

# Elektronik

---

## Basic Components and Circuit Theory 3

EITA10


Iman Ghotbi

Mars 2025




# We learned


## KVL

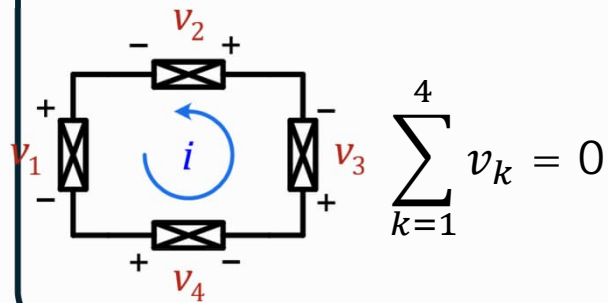


## Series Coupling

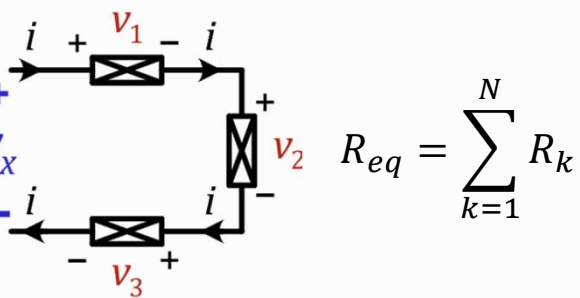


## Thevenin's/Norton's

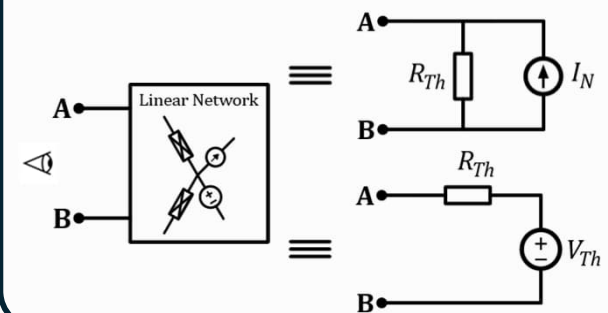


## KCL

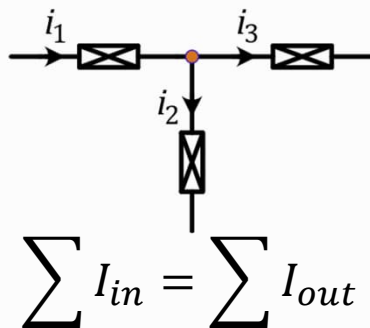

## Parallel Coupling

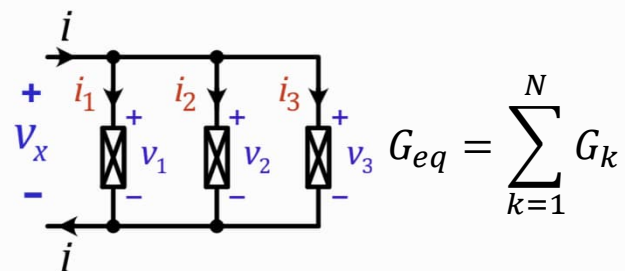

## Superposition

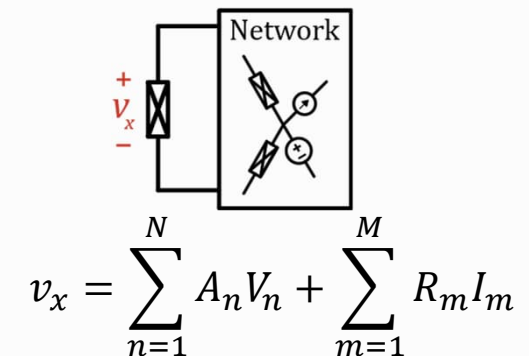

# Today we learn


---

- Circuit analysis – an example
- Measurement techniques
- Capacitance
- Capacitors
- First-order (RC) circuits




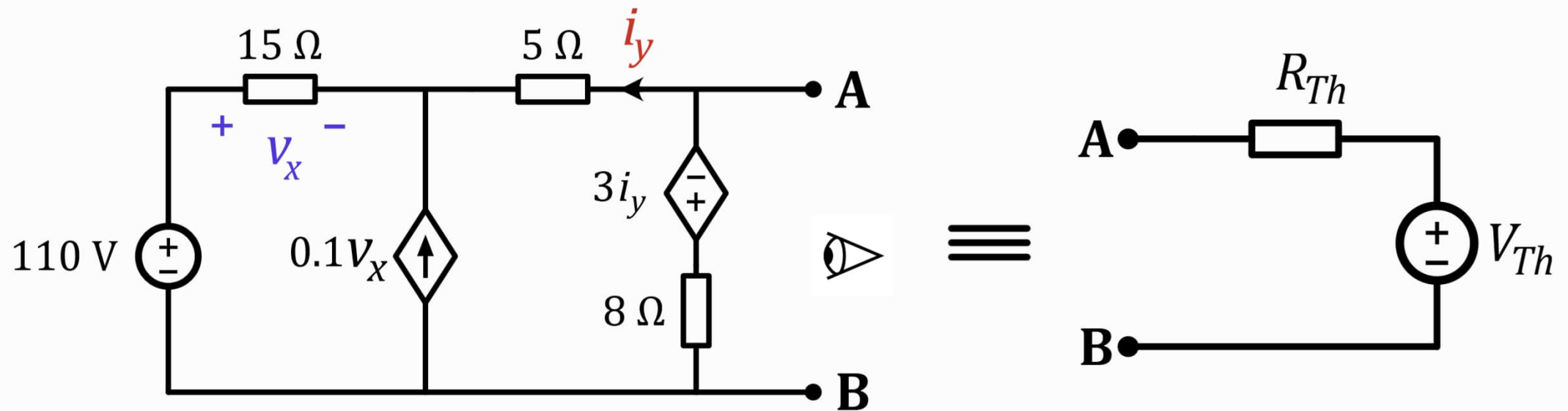
# Example

- Determine the Thevenin's equivalent circuit seen from A-B port.


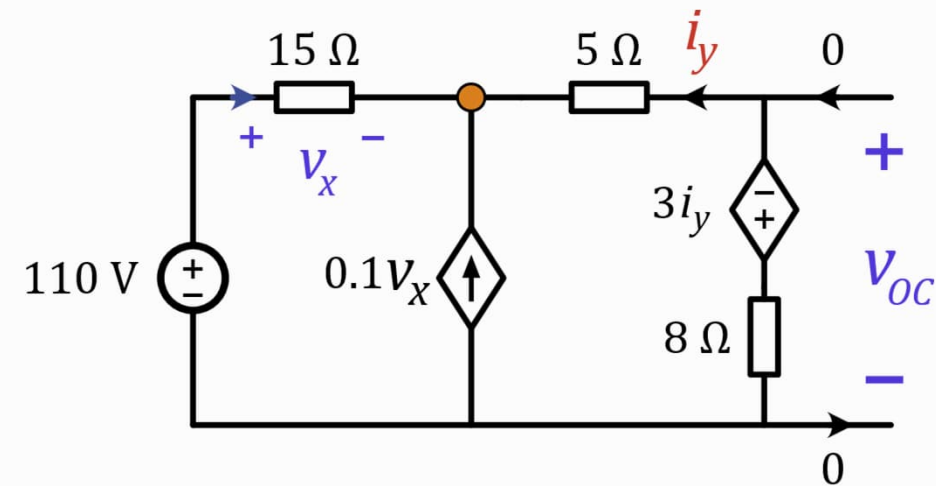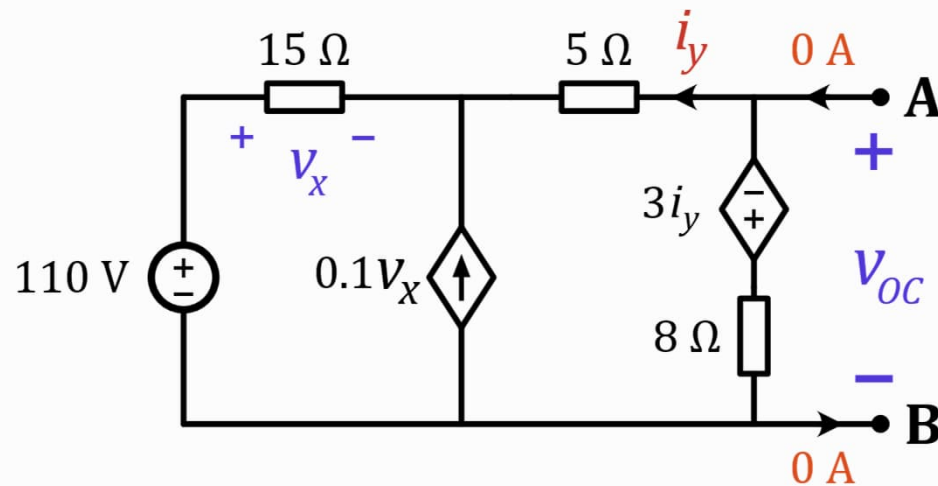
# Nodal Analysis – Example

- Determine the Thevenin's equivalent circuit seen from A-B port.
- **Open-circuit voltage ( $V_{Th} = V_{OC}$ )**




$$\text{KCL: } i_y + 0.1v_x + \frac{1}{15}v_x = 0$$


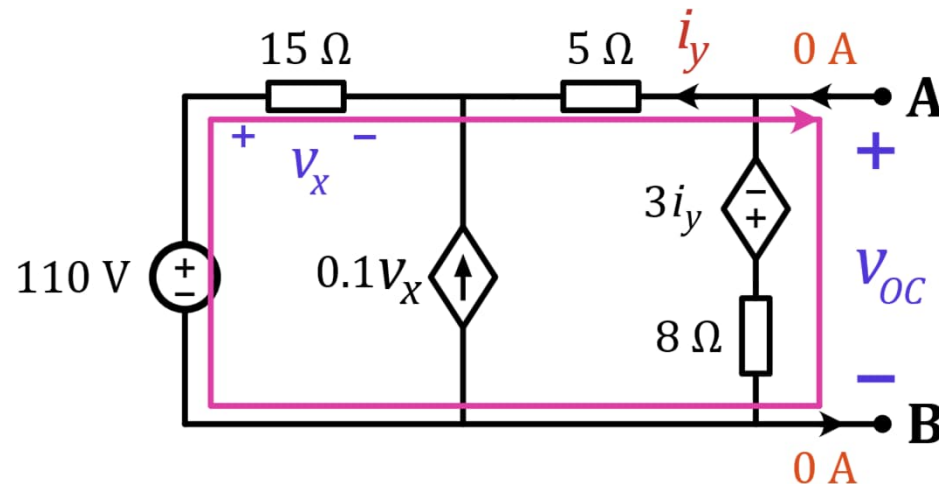
# Nodal Analysis – Example

- Determine the Thevenin's equivalent circuit seen from A-B port.
- Open-circuit voltage ( $V_{Th} = V_{OC}$ )**



$$\begin{cases} \text{KCL: } i_y + \frac{1}{6} v_x = 0 \\ \text{KVL: } v_x - 16i_y = 110 \end{cases} \quad \begin{cases} i_y = -5 \text{ A} \\ v_x = 30 \text{ V} \end{cases}$$

$$V_{OC} = -3i_y - 8i_y = -11i_y$$

$$\Rightarrow \boxed{V_{OC} = 55 \text{ V}}$$


$$\text{KVL: } -110 + v_x - 5i_y - 3i_y - 8i_y = 0$$


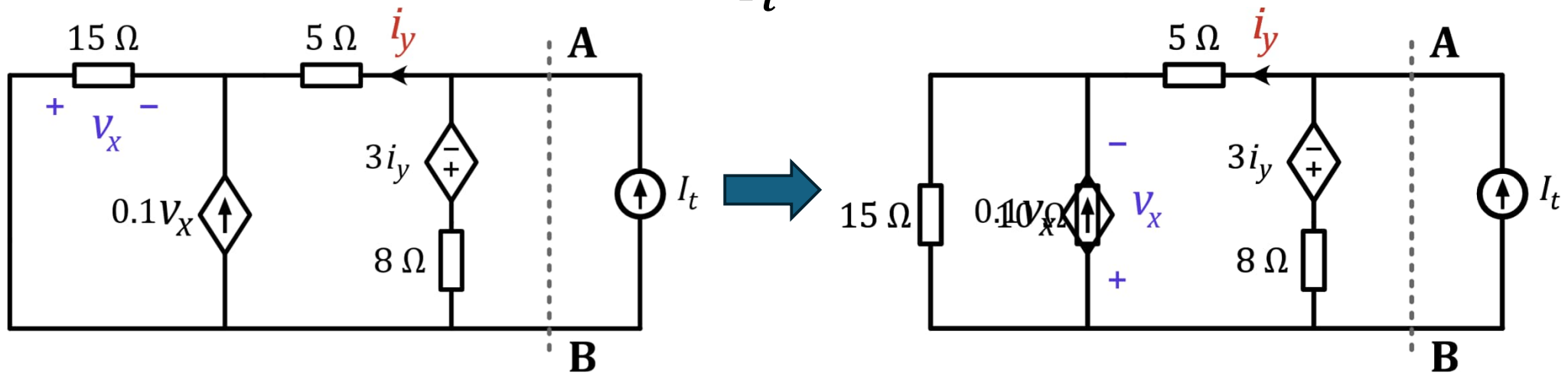
# Nodal Analysis – Example

- Determine the Thevenin's equivalent circuit seen from A-B port.

- Thevenin's resistance (  $R_{Th} = \frac{V_{AB}}{I_t}$  )



$$R_x = \frac{v_x}{0.1v_x} = 10 \Omega$$





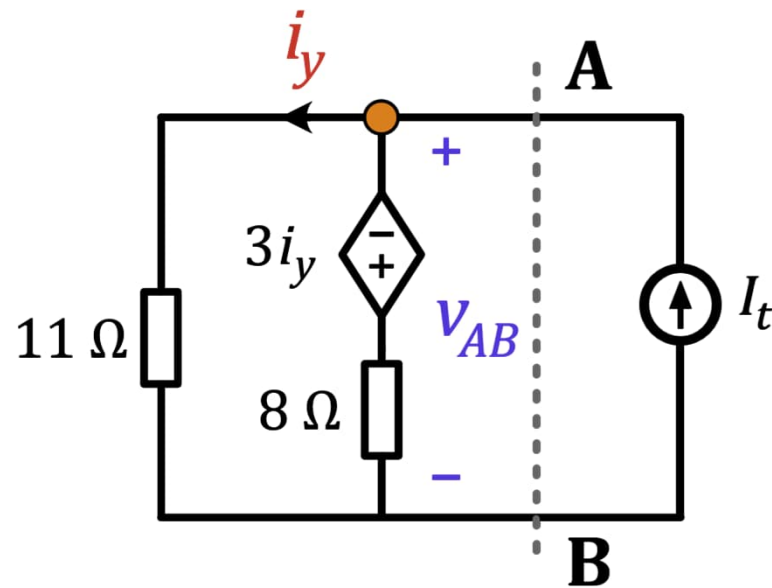
# Nodal Analysis – Example

- Determine the Thevenin's equivalent circuit seen from A-B port.

- Thevenin's resistance (  $R_{Th} = \frac{V_{AB}}{I_t}$  )



$$\begin{cases} \text{KVL: } -v_{AB} + 11i_y = 0 \\ \text{KCL: } -v_{AB} - 3i_y + 8(I_t - i_y) = 0 \end{cases}$$


$$v_{AB} = 4I_t \Rightarrow \boxed{R_{Th} = 4\ \Omega}$$





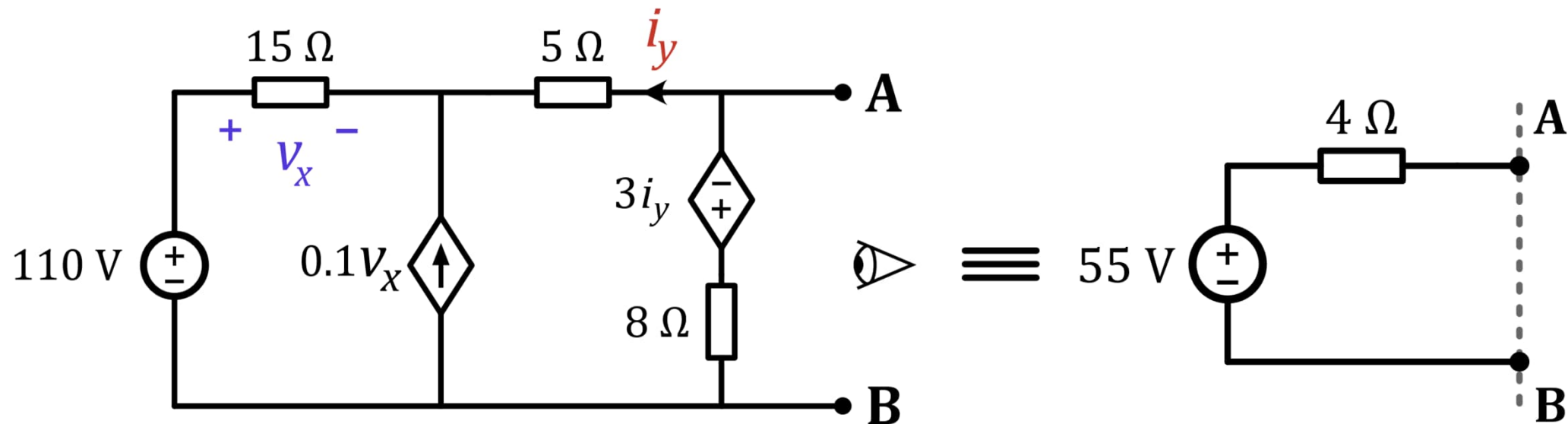
# Example

- Determine the Thevenin's equivalent circuit seen from A-B port.


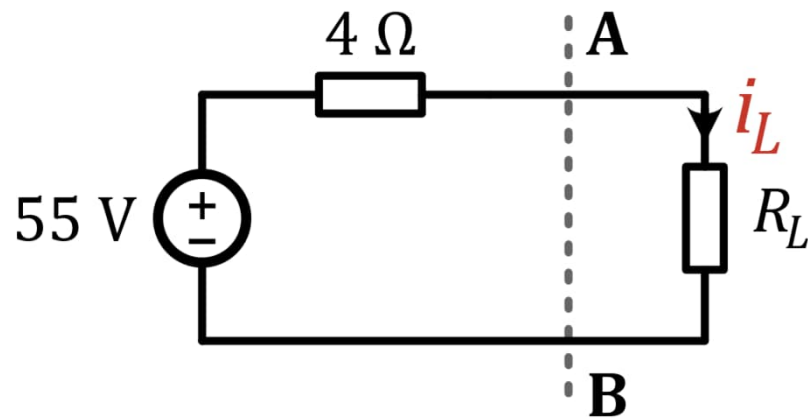
# Pause and Ponder 1

- We aim to supply power to a resistive load using the circuit we've just analyzed. What is the **optimal value for the load resistance** to absorb the **maximum power** available?




$$i_L = \frac{55}{4 + R_L} \quad , \quad v_L = \frac{R_L}{4 + R_L} \times 55$$

$$P_L = v_L i_L \quad \Rightarrow \quad P_L = \frac{R_L}{(4 + R_L)^2} \times 55^2$$


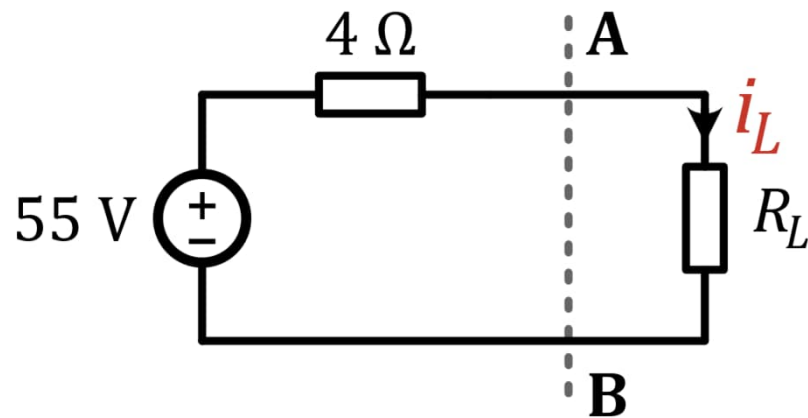
# Pause and Ponder 1

- We aim to supply power to a resistive load using the circuit we've just analyzed. What is the **optimal value for the load resistance** to absorb the **maximum power** available?





$$\frac{dP_L}{dR_L} = 0 \Rightarrow R_{L,opt} = R_{Th} \Rightarrow \boxed{R_{L,opt} = 4 \Omega}$$

$$P_{L,max} = \frac{v_{Th}^2}{4R_{Th}} = 189 \text{ W}$$



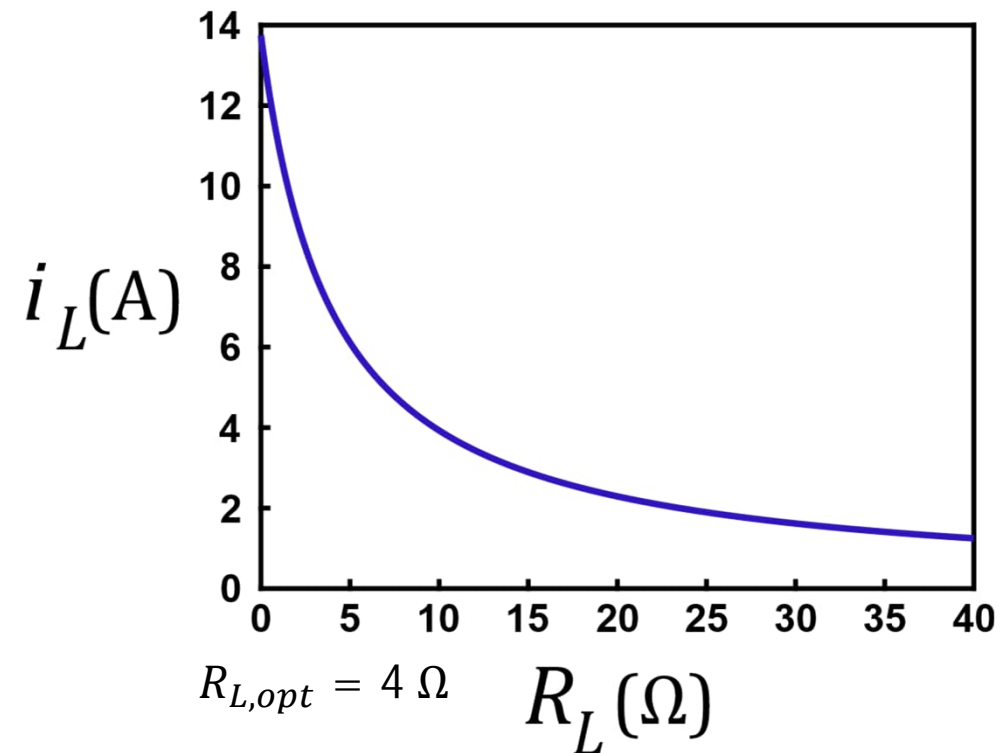
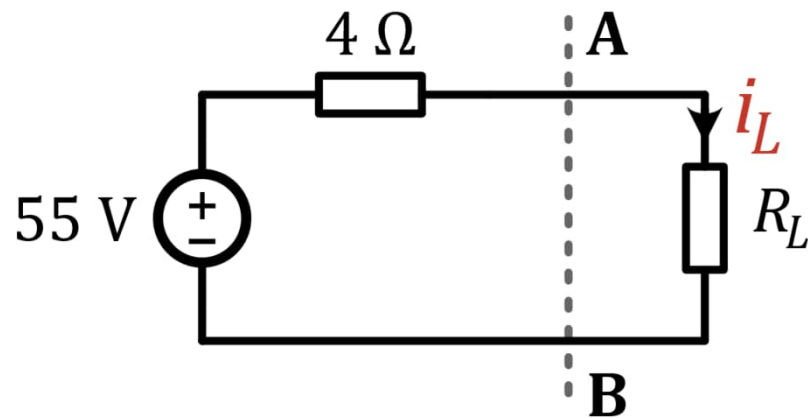
# Pause and Ponder 1

- We aim to supply power to a resistive load using the circuit we've just analyzed. What is the **optimal value for the load resistance** to absorb the **maximum power** available?



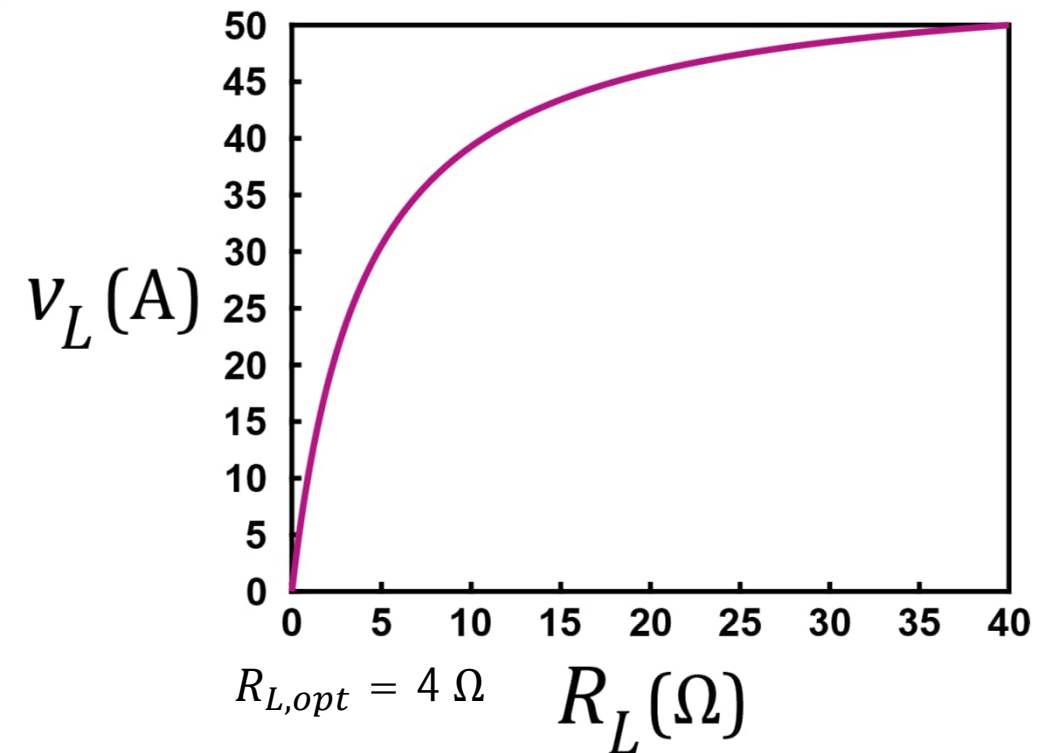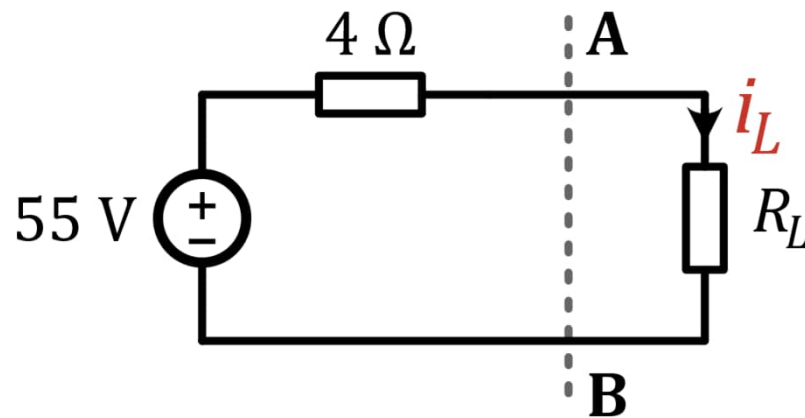
# Pause and Ponder 1

- We aim to supply power to a resistive load using the circuit we've just analyzed. What is the **optimal value for the load resistance** to absorb the **maximum power** available?



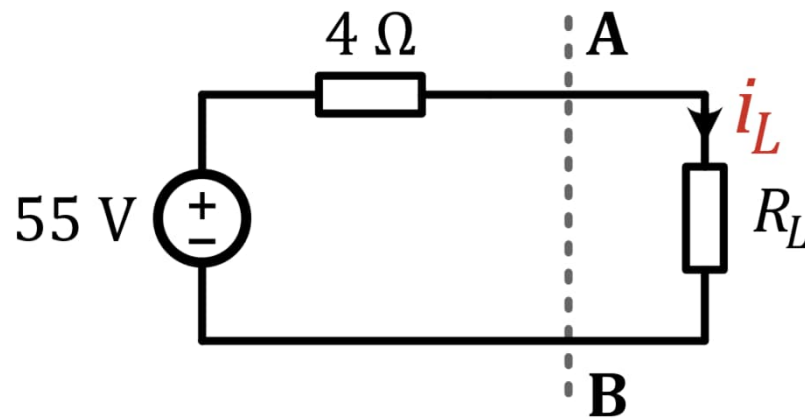
# Pause and Ponder 1

- We aim to supply power to a resistive load using the circuit we've just analyzed. What is the **optimal value for the load resistance** to absorb the **maximum power** available?




$P_L$  (W)

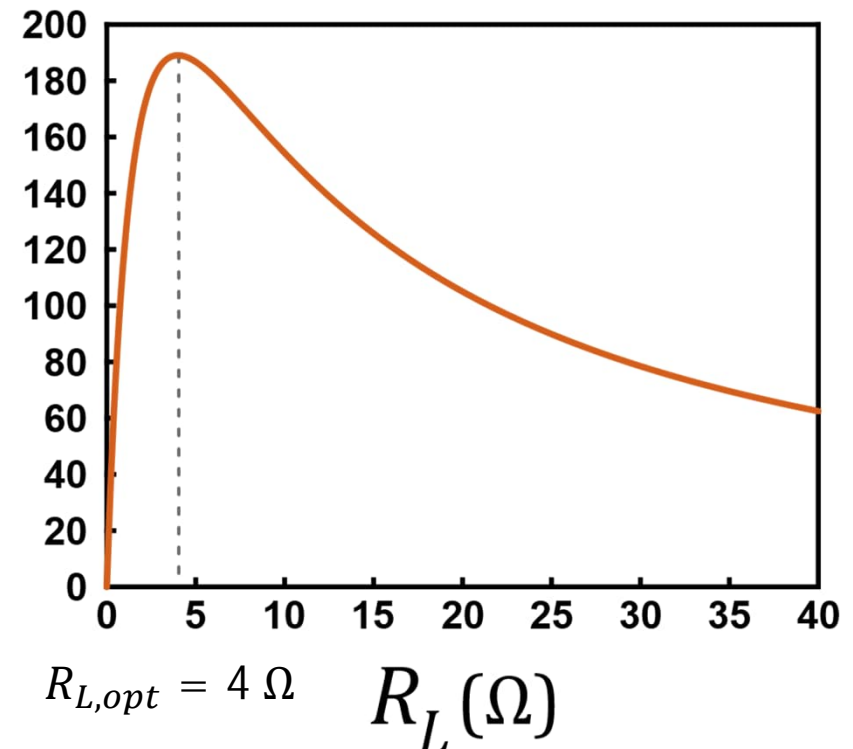
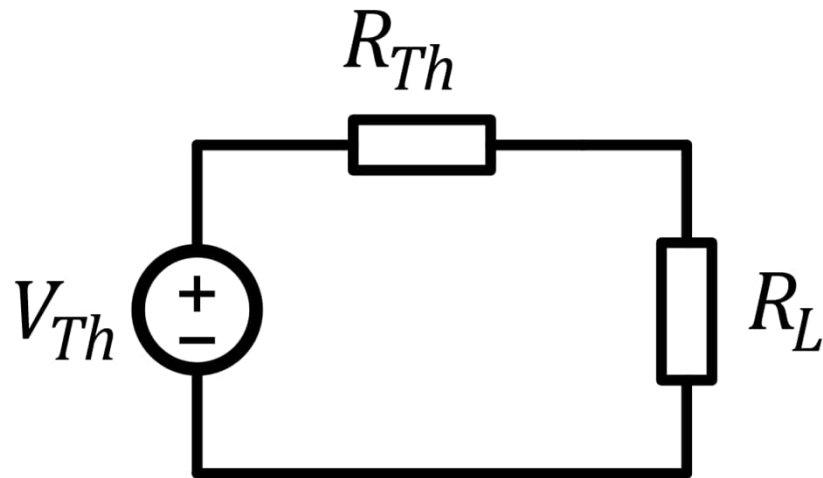
# Pause and Ponder 2

---

- Calculate the power efficiency when the optimal load is connected.



$$P_{in} = v_{th} \times i_L = \frac{v_{Th}^2}{2R_{Th}}$$

$$P_{L,max} = \frac{v_{Th}^2}{4R_{Th}}$$


$$\eta\% = \frac{P_L}{P_{in}} \times 100 = 50\%$$






# Measurement Techniques

- A typical multimeter

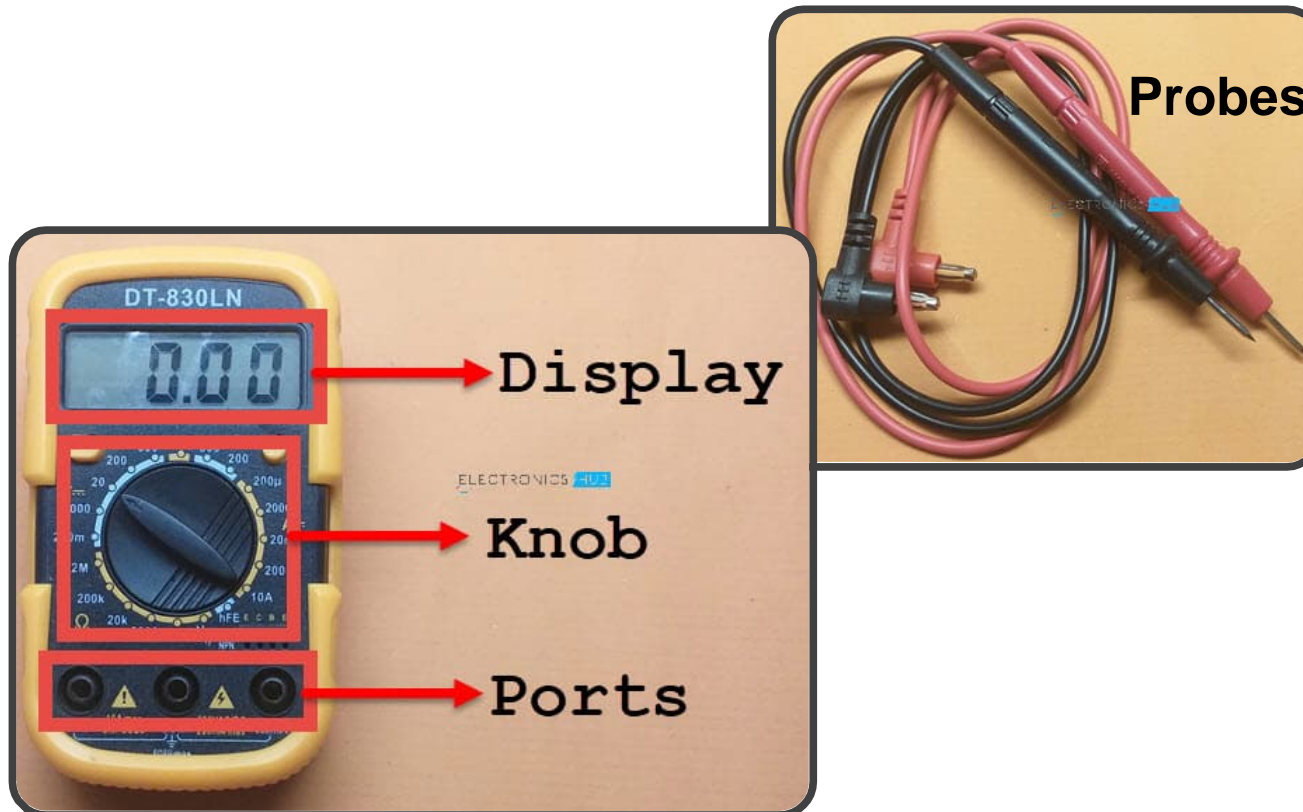

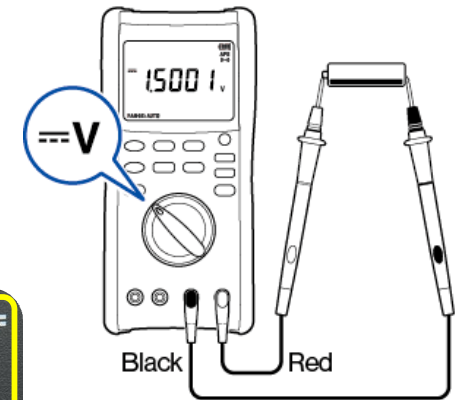
# Measurement Techniques

- A typical multimeter
- DC voltage measurement
  - The **black probe** is connected between the **COM** jack and **GND** of the circuit.
  - The **red probe** is connected to the **node-of-interest**.
  - Differential measurement: **parallel connection**  
(positive → red, negative → black)



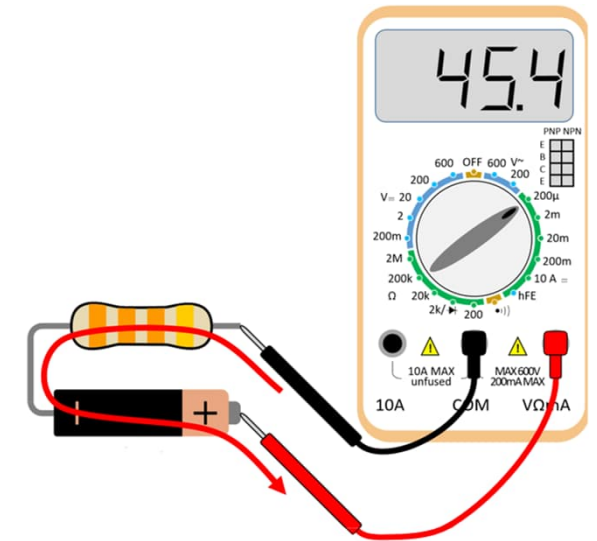
# Measurement Techniques

- A typical multimeter
- DC voltage measurement
- **DC current measurement**
  - **Series** connection
  - The probes are placed on the way of the current of interest.


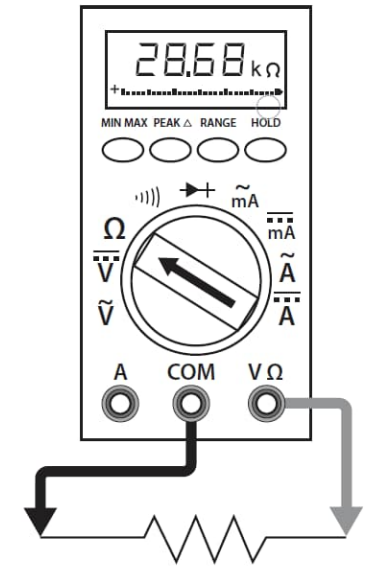
# Measurement Techniques

- A typical multimeter
- DC voltage measurement
- DC current measurement
- **Resistance measurement**
  - Connect the probes to the two sides of the resistor.





# Measurement Techniques

- A typical multimeter
- DC voltage measurement
- DC current measurement
- Resistance measurement
- **Short-circuit test**
  - Kind of resistance measurement
  - Continuity Beeper





Don't forget to **turn it off**  
before leaving the lab!


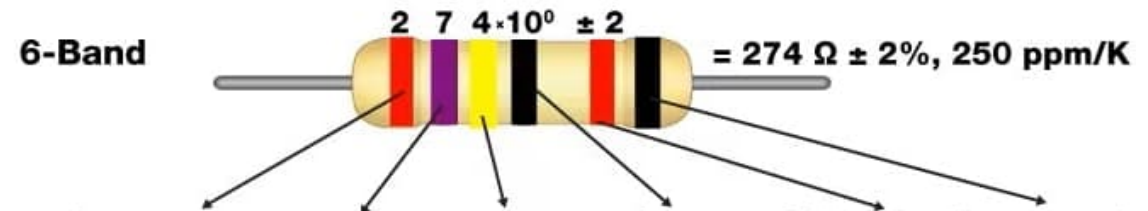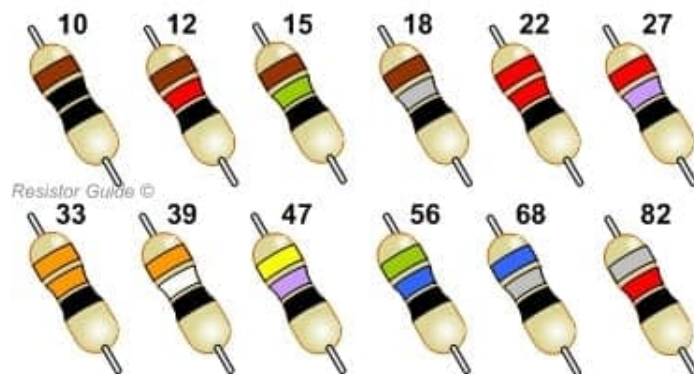
# Standard Resistors and Color Code

- Resistors are manufactured in a variety of shapes and sizes.
- Commercially available resistors are typically **limited to standard values**.
- Non-standard resistor values are implemented by **creating series and parallel combinations**.



Color	1st Digit	2nd Digit	3rd Digit	Multiplier	Tolerance	Temperature Coefficient
Black	0	0	0	1 $\Omega$		250 ppm/K
Brown	1	1	1	10 $\Omega$	$\pm 1\%$	100 ppm/K
Red	2	2	2	100 $\Omega$	$\pm 2\%$	50 ppm/K
Orange	3	3	3	1k $\Omega$		15 ppm/K
Yellow	4	4	4	10k $\Omega$		25 ppm/K
Green	5	5	5	100k $\Omega$	$\pm 0.5\%$	20 ppm/K
Blue	6	6	6	1M $\Omega$	$\pm 0.25\%$	10 ppm/K
Violet	7	7	7		$\pm 0.1\%$	5 ppm/K
Grey	8	8	8			1 ppm/K
White	9	9	9			
Gold				0.1 $\Omega$	$\pm 5\%$	
Silver				0.01 $\Omega$	$\pm 10\%$	




# Capacitance

- The capability of a device (material) to **store electric charge** in response to an **electric potential**.

$$C \triangleq \frac{q}{v}$$

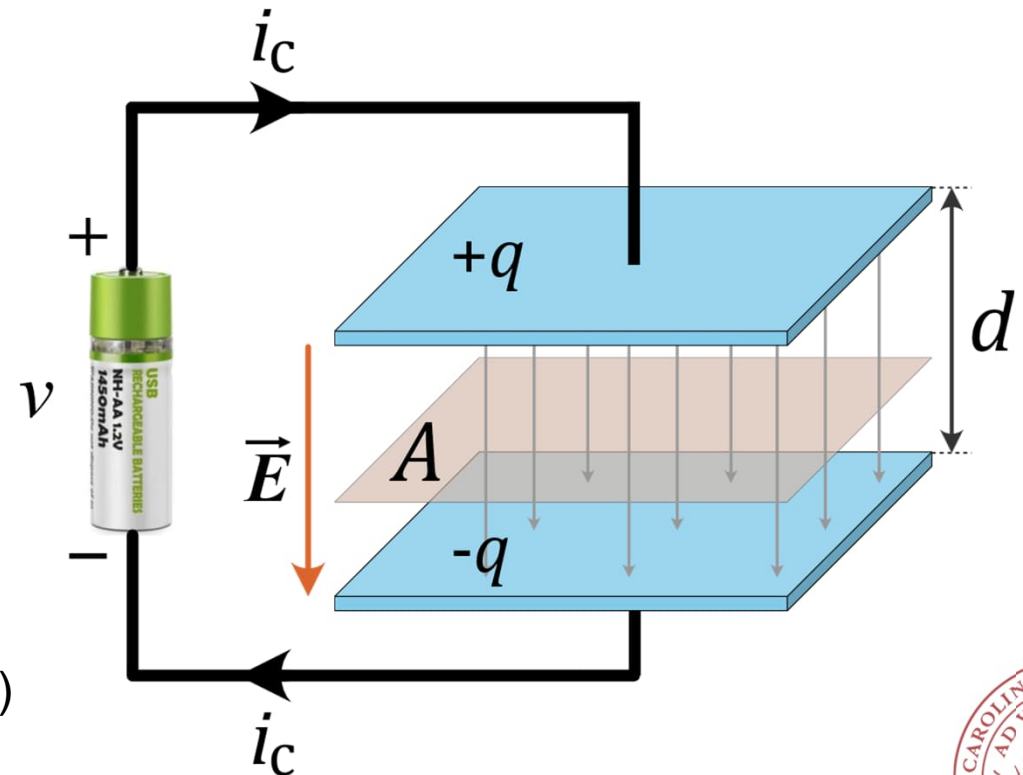- Measured in Farad (F).
  - 1 F is a huge capacitance.
  - Normal range of capacitance in circuits:  
 $\mu\text{F}$ ,  $\text{nF}$ , and  $\text{pF}$ .
  - Unwanted (parasitic) capacitances:  $\text{fF}$  ( $10^{-15} \text{ F}$ )






# Relative Permittivity (Dielectric constant)

- Permittivity of a dielectric (insulator) measures its **capability to store electric energy** in an electric field.

$$\epsilon = \epsilon_r \epsilon_0$$

$$\epsilon_0 \approx 8.85 \times 10^{-12} \left[ \frac{C^2}{N.m^2} \right]$$

Material	$\epsilon_r$
Paper	1.4
Mica	3 to 6
Silicon dioxide (SiO <sub>2</sub> )	3.9
Graphite	10 to 15
Silicon (Si)	11.68
Water (room temperature)	80
Titanium dioxide (TiO <sub>2</sub> )	86 to 173

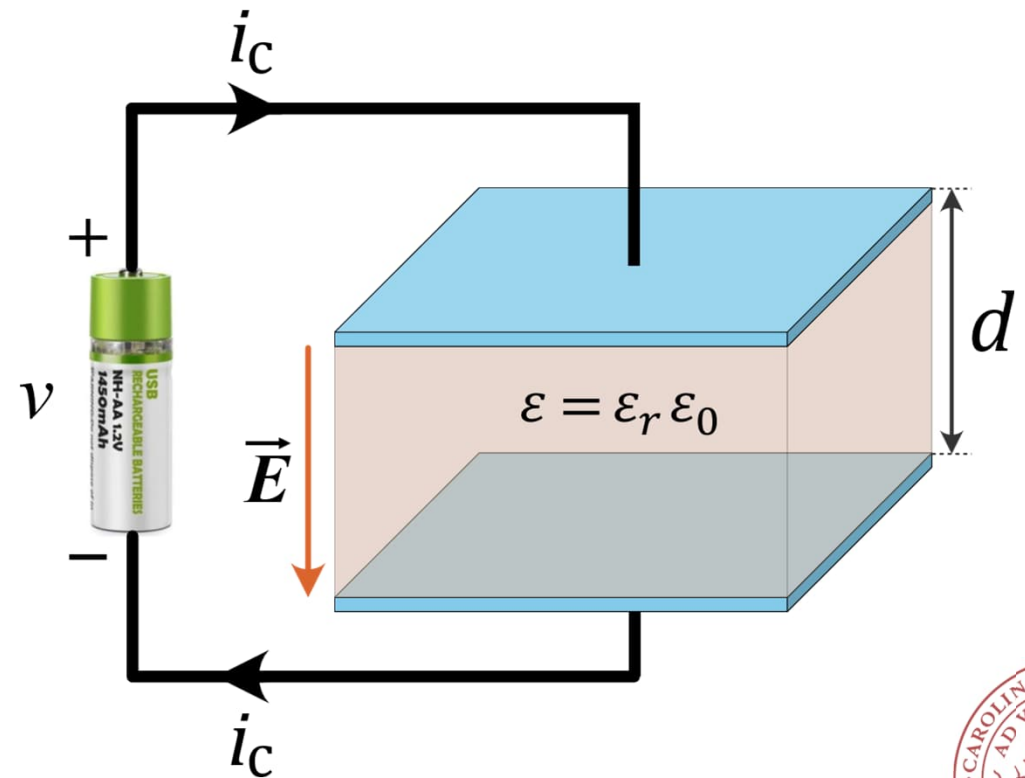


# Parallel-Plate Capacitor

---

- An insulator is sandwiched between two conductor plates.
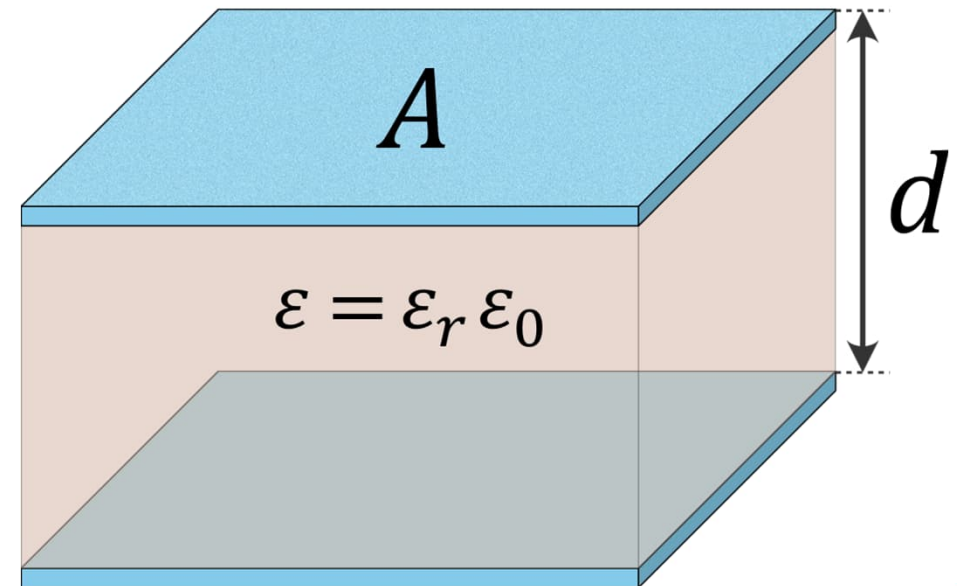
$$C = \epsilon_r \epsilon_0 \frac{A}{d}$$



# Practical Capacitors


---

- To create sufficiently large capacitance:

- Thin insulator
- High  $\epsilon_r$
- Large area


→ Roll up!

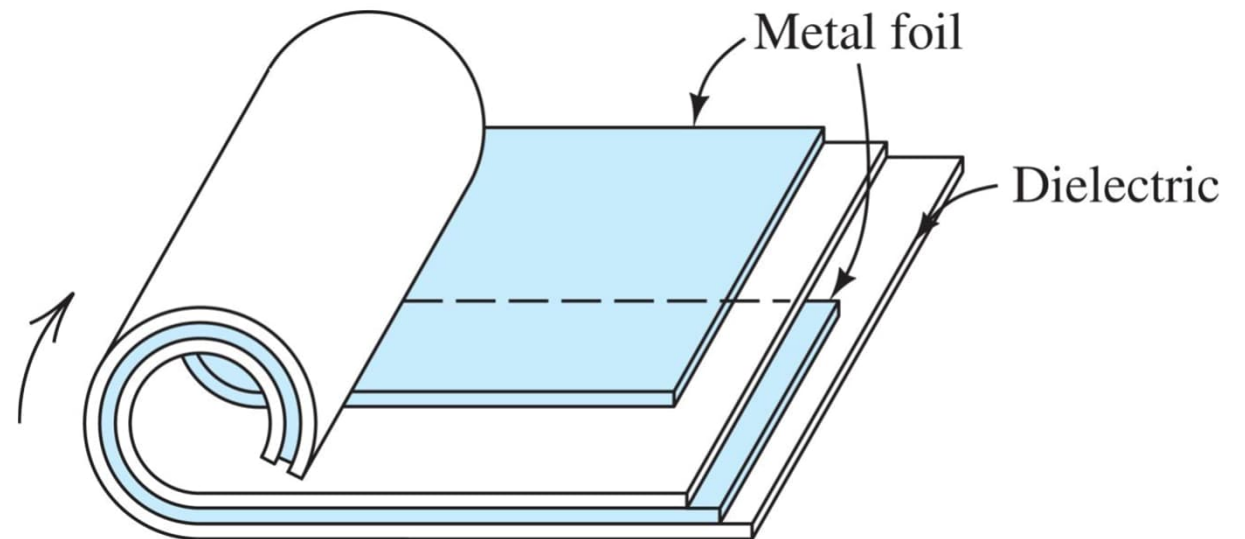- We need them for:
  - **Filtering** out interference
  - **Isolating** DC voltages (AC-Coupling)
  - **Bypassing** some components at high frequencies
  - **Compensating** inductances


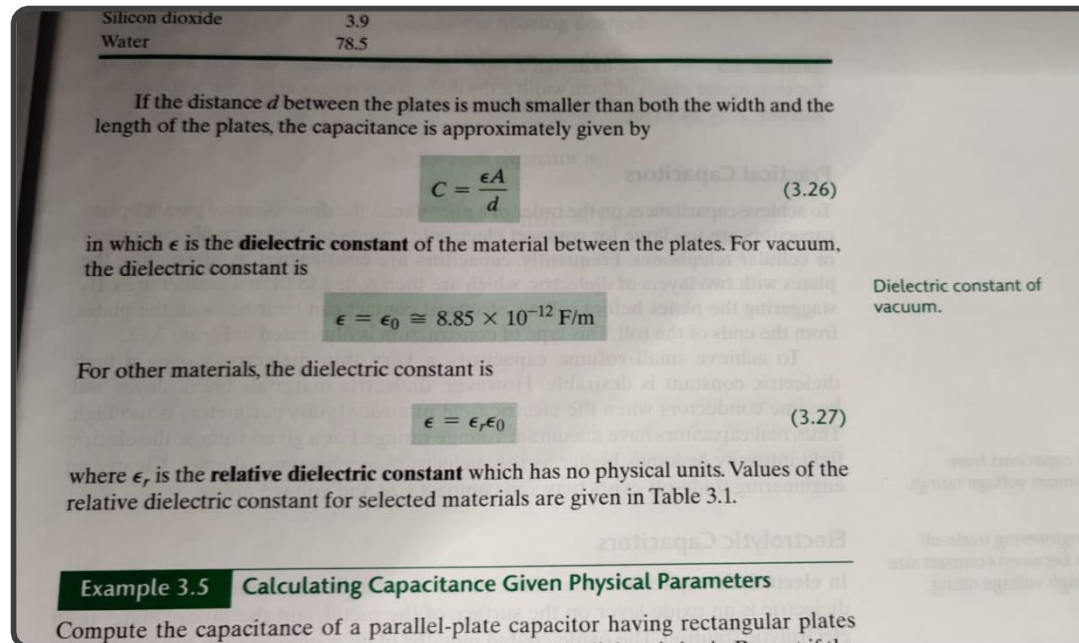
# Coursebook's Capacitance!

- Coursebook roll!
- Where PDF doesn't work!



# Coursebook's Capacitance!

- Metal plates:

- Area:

$$A = 16 \times 5 \text{ cm}^2 = 80 \text{ cm}^2$$

- Page thickness:

$$d = 50 \text{ }\mu\text{m}$$


- Permittivity:

$$\epsilon_r \approx 1.4$$

Theory:


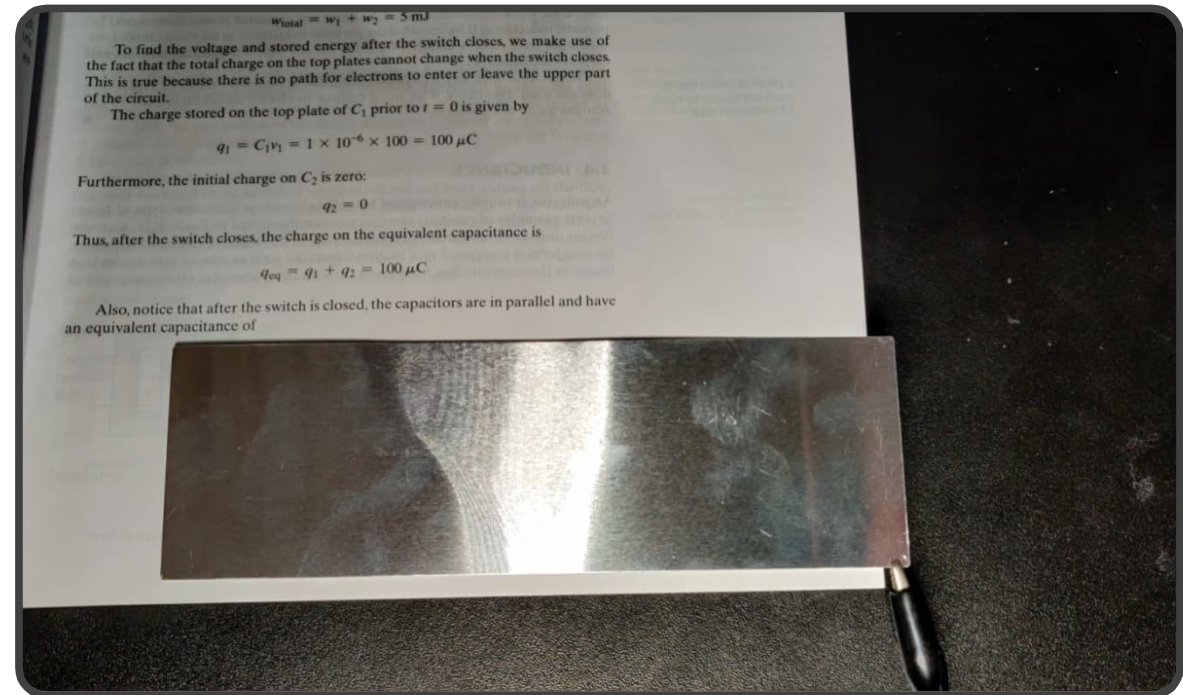
$$C = \epsilon_r \epsilon_0 \frac{A}{d} \approx 2 \text{ nF}$$





# Coursebook's Capacitance!

- First measurement:

$$C_{meas1} = 1.4 \text{ nF}$$

- Slightly uneven plates, air gap → (inconsistent  $d$ )



- Press it down!

$$C_{meas2} = 2.2 \text{ nF}$$

- The theory is correct!




# $i - v$ relationship of a Capacitor

- Time domain:

$$q_c = C v_c \Rightarrow \frac{dq_c}{dt} = \frac{dC}{dt} v_c + C \frac{dv_c}{dt}$$
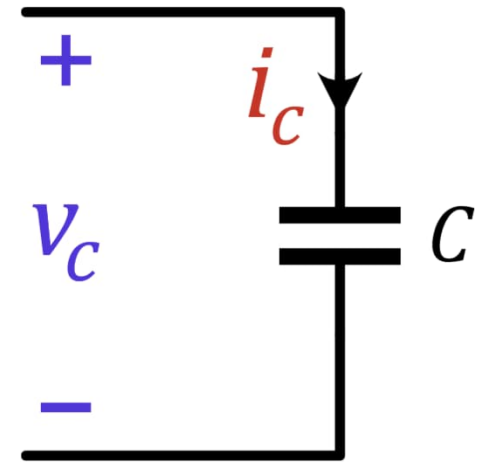
$$i_c = \frac{dC}{dt} v_c + C \frac{dv_c}{dt}$$



For a **time-invariant** (constant) capacitor:

$$i_c = C \frac{dv_c}{dt}$$






# $I(s) - V(s)$ relationship of a Capacitor

- Frequency domain:

$$i_c = C \frac{dv_c}{dt} \xrightarrow{\mathcal{L}} I_c(s) = C(sV_c(s) - \overbrace{v_c(t_0^-)}^{\text{Initial condition}})$$

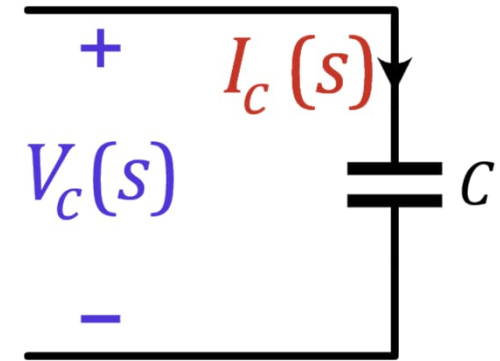
$t_0$ : The time of change in the circuit's state (switching)



$$\Rightarrow I_C = (Cs)V_C - Cv_c(t_0^-)$$

Impedance

$$Z_C = \frac{V_C(s)}{I_C(s)} \Big|_{v_c(t_0^-)=0} = \frac{1}{Cs}$$

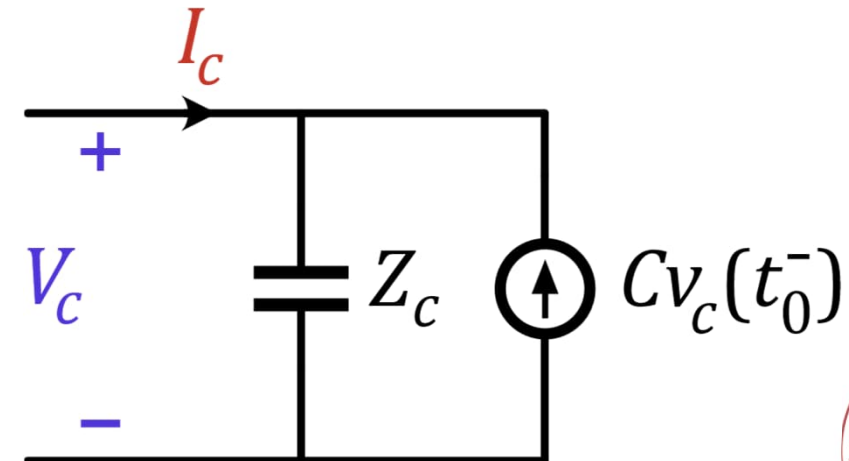


# Impedance ( $Z$ ) and Admittance ( $Y$ )

- Ohm's law in frequency domain
- Useful for dynamic circuits

Static circuit	$V = RI$	$I = GV$
Dynamic circuit	$V(s) = Z(s)I(s)$	$I(s) = Y(s)V(s)$

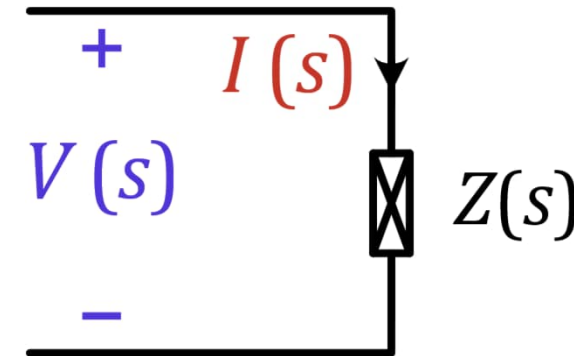- The same techniques can be applied:
  - Series/parallel combination
  - Voltage/current division, superposition
  - Thevenin's equivalent circuit



$$V(s) = Z(s)I(s)$$

$$I(s) = Y(s)V(s)$$



# Laplace Transform and S-Plane


Laplace  
transform

$$F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

$$s = \frac{1}{\tau} + j\omega$$

$$\Rightarrow e^{-st} = \exp\left(-\frac{t}{\tau}\right) (\cos(\omega t) - j\sin(\omega t))$$
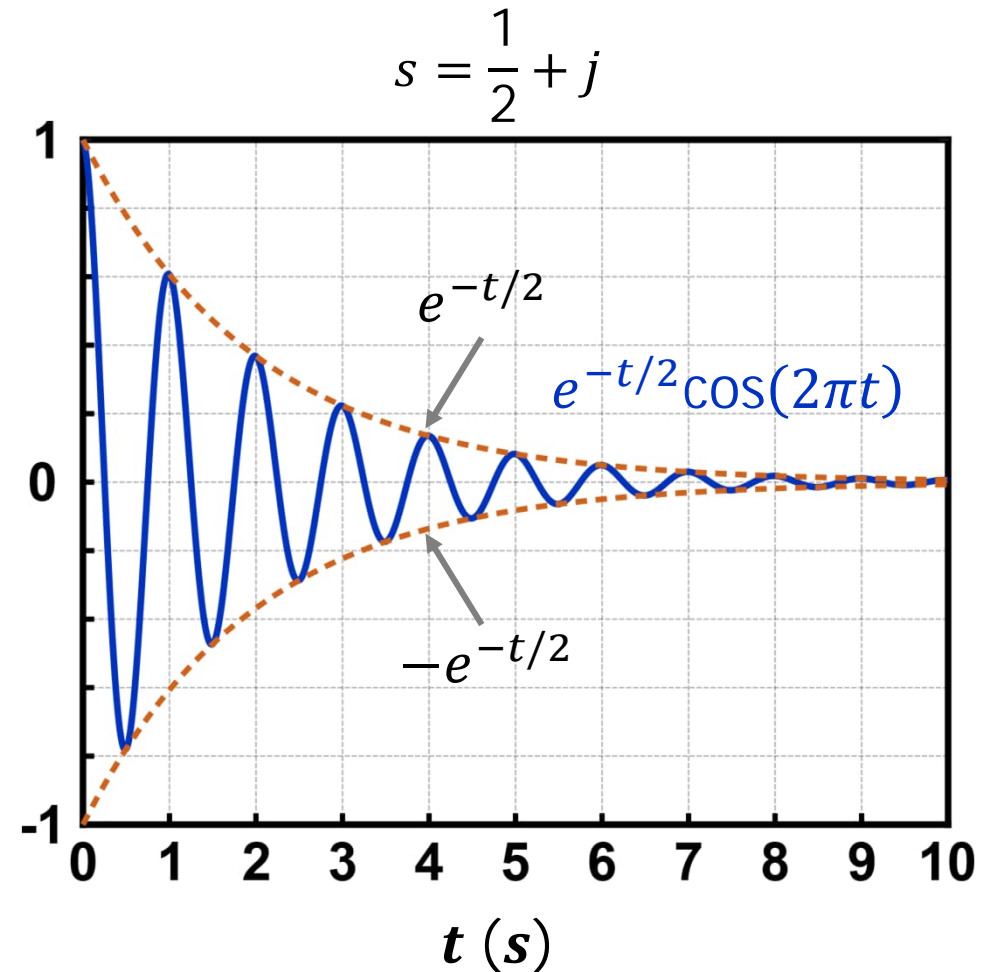
$$\Rightarrow \text{Re}\{e^{-st}\} = \exp\left(-\frac{t}{\tau}\right) \cos(\omega t)$$



# Laplace Transform and S-Plane

**Laplace transform**

$$F(s) = \int_0^{\infty} f(t) e^{-st} dt$$

**Derivative**


$$\mathcal{L}\{f'(t)\} = sF(s) - f(0^-)$$

**Integration**

$$\mathcal{L}\left\{\int_0^t f(\tau) d\tau\right\} = \frac{1}{s} F(s)$$

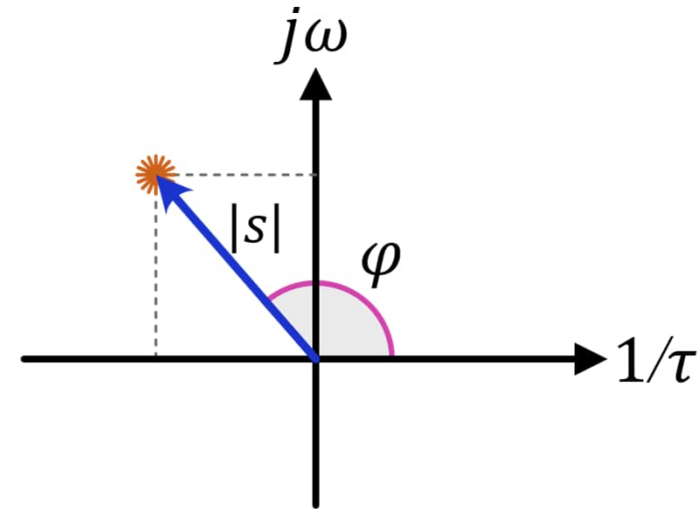**Convolution**

$$\mathcal{L}\{f(t) * g(t)\} = F(s) \cdot G(s)$$



$$|s| = \sqrt{\left(\frac{1}{\tau}\right)^2 + \omega^2}$$

$$\varphi = \arctan(\omega\tau)$$





# Steady-state vs. Transient Response

- If we give enough time to a circuit, the effect of **the exponential response** becomes negligible:

$$t \gg \tau \Rightarrow \exp\left(-\frac{t}{\tau}\right) \approx 0$$


- In the frequency domain, we limit  $s$  to the **imaginary axis**:

$$s = j\omega \Rightarrow F(s)|_{s=j\omega} = F(j\omega)$$

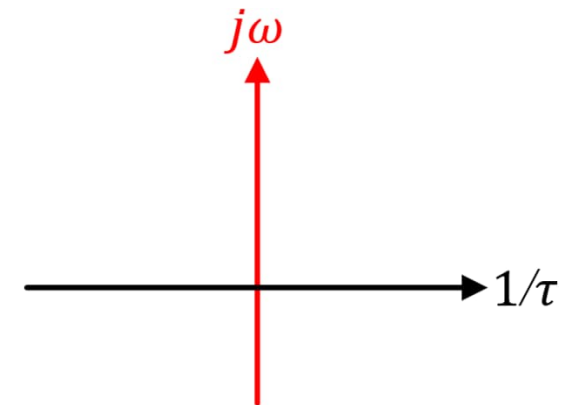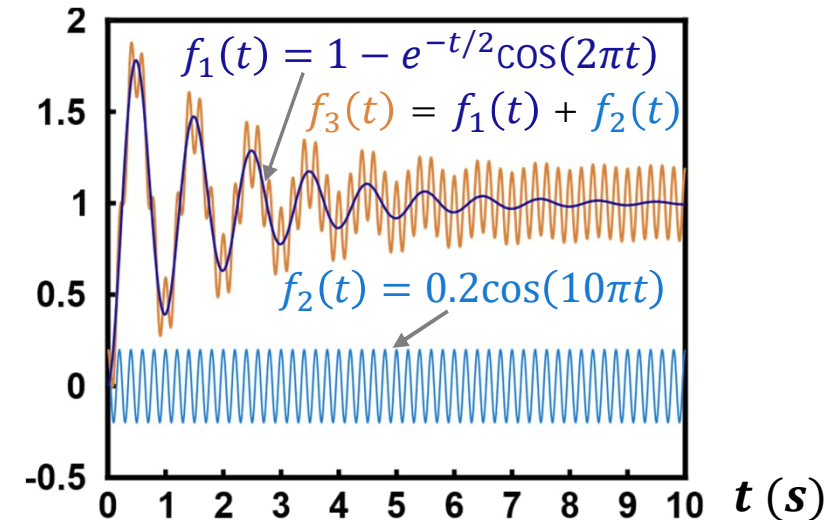

# Impedance ( $Z$ ) and Admittance ( $Y$ )

## Resistor

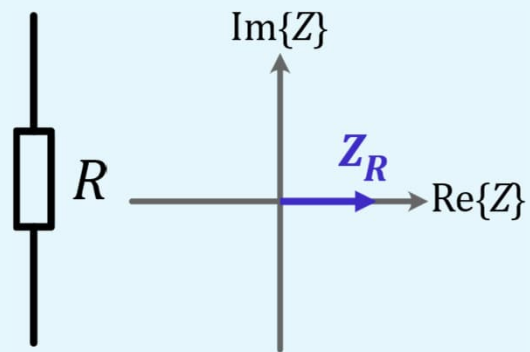


$$Z_R = R \quad Y_R = \frac{1}{R} = G$$

$$|Z_R(j\omega)| = R$$

$$\angle Z_R(j\omega) = 0$$

## Capacitor

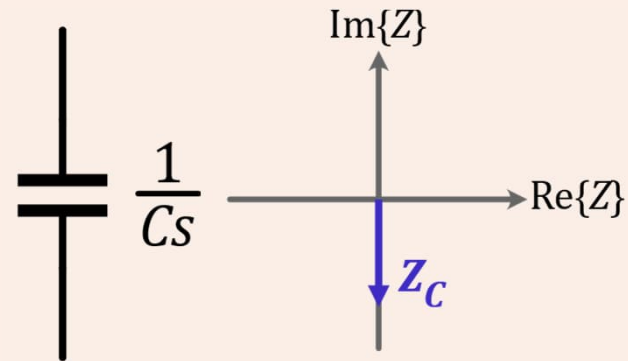


$$Z_C = \frac{1}{Cs} \quad Y_C = Cs$$

$$|Z_C(j\omega)| = \frac{1}{\omega C}$$

$$\angle Z_C(j\omega) = -\frac{\pi}{2}$$

## Inductor

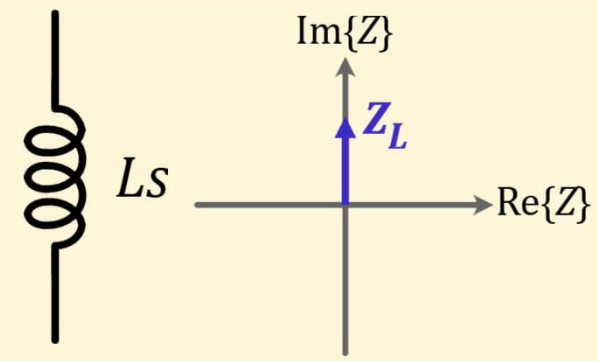


$$Z_L = Ls \quad Y_L = \frac{1}{Ls}$$

$$|Z_L(j\omega)| = \omega L$$

$$\angle Z_L(j\omega) = +\frac{\pi}{2}$$



# Series Capacitors

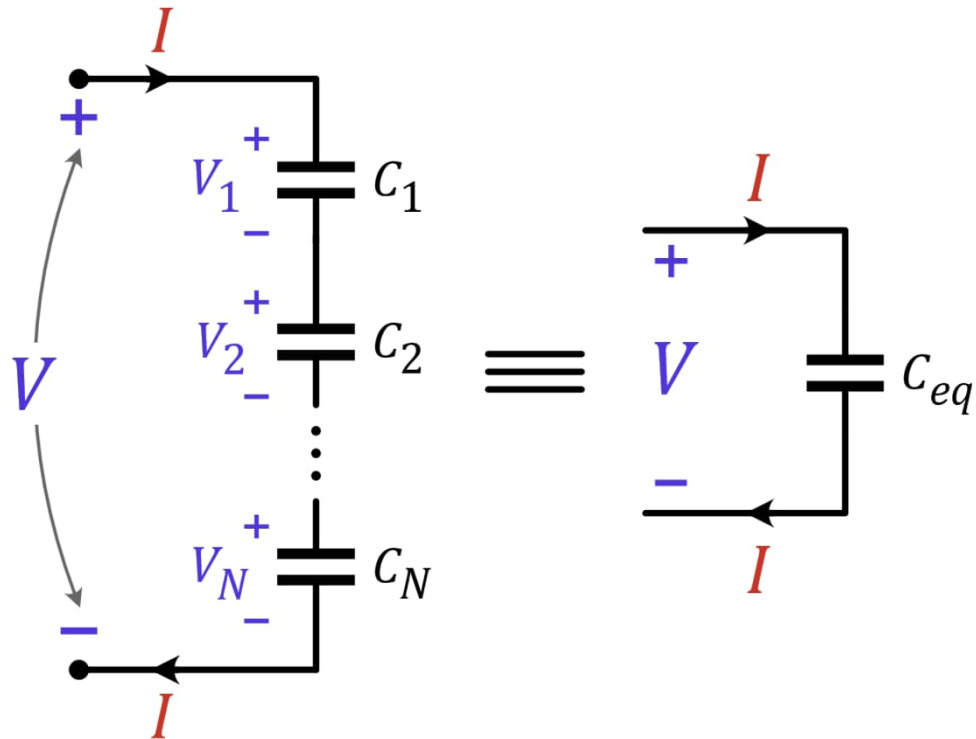


$$\begin{cases} V_k = Z_{Ck} I = \frac{1}{C_k s} I \\ V = \sum_{k=1}^N V_k = \sum_{k=1}^N Z_{Ck} I \\ \Rightarrow V = \frac{I}{s} \sum_{k=1}^N \frac{1}{C_k} = \frac{I}{C_{eq} s} \end{cases}$$
$$\Rightarrow C_{eq} = \frac{1}{\sum_{k=1}^N \frac{1}{C_k}}$$





# Parallel Capacitors

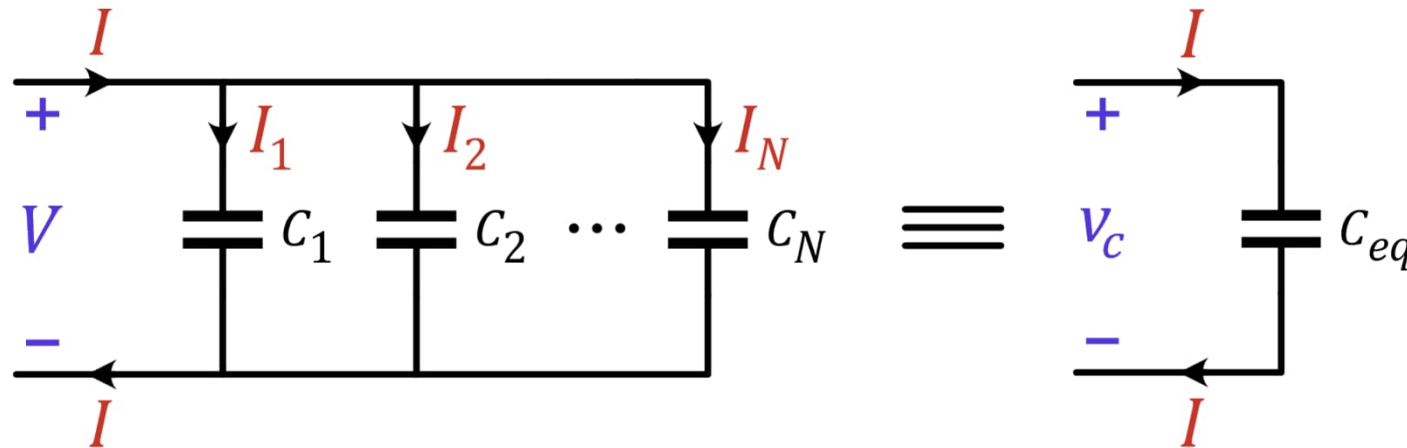


$$\left\{ \begin{array}{l} I_k = \frac{V}{Z_{Ck}} = C_k s V \\ I = \sum_{k=1}^N I_k = \sum_{k=1}^N C_k s V \end{array} \right. \Rightarrow I = s V \sum_{k=1}^N C_k = C_{eq} s V \Rightarrow \boxed{C_{eq} = \sum_{k=1}^N C_k}$$


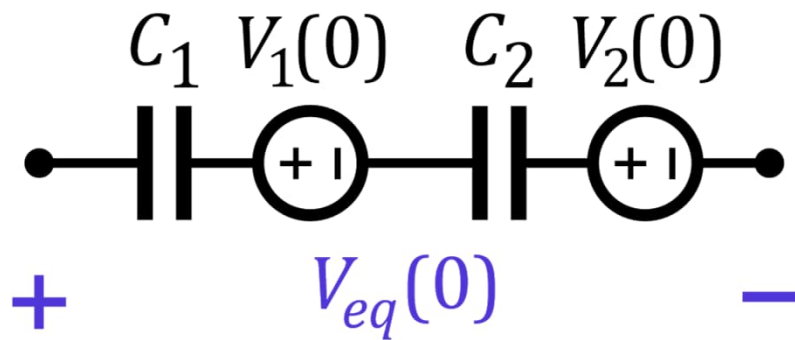
# Pause and Ponder 3

- In a **series connection** of  $N$  capacitors, assume they have initial voltages as  $V_1(0), V_2(0), \dots, V_N(0)$ . What initial condition should we consider for the equivalent capacitor?




$$V_{eq}(0) = \sum_{k=1}^N V_k(0)$$


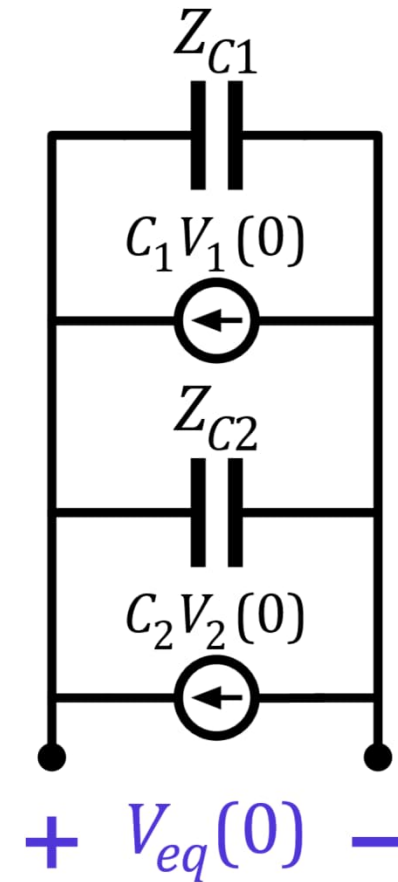
# Pause and Ponder 4

- In a **parallel connection** of  $N$  capacitors, assume they have initial voltages as  $V_1(0), V_2(0), \dots, V_N(0)$ .  
What initial condition should we consider for the equivalent capacitor?

$$V_{eq}(0) = \frac{\sum_{k=1}^N C_k V_k(0)}{\sum_{k=1}^N C_k} = \frac{\sum_{k=1}^N q_k(0)}{C_{eq}}$$




# Example: Equivalent Impedance

- Find the equivalent impedance of the following circuit.
- $C_1$  parallel with  $R$ :

$$Z_1 = \frac{1}{\frac{1}{R} + C_1 s} = \frac{R}{1 + RC_1 s}$$

- $Z_1$  series with  $C_2$ :
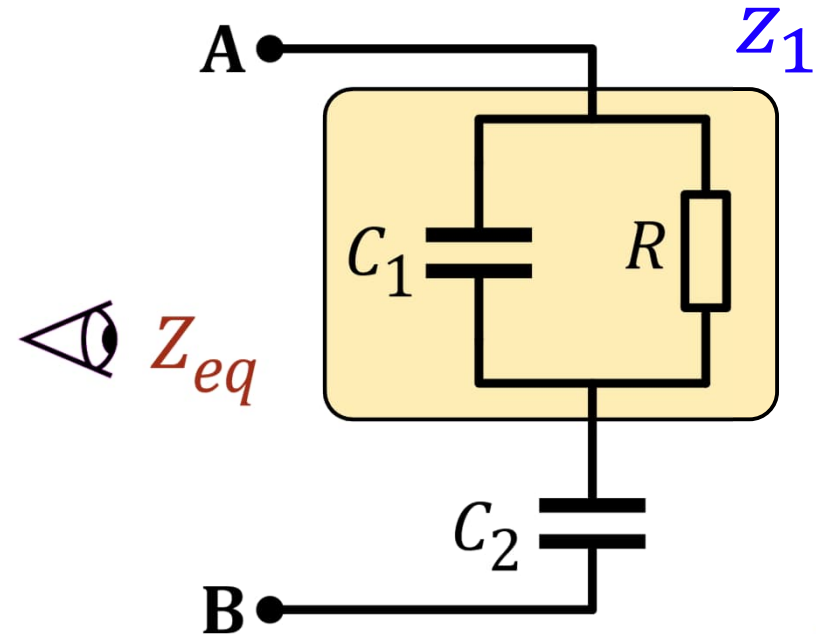
$$Z_{eq} = Z_1 + \frac{1}{C_2 s} = \frac{1 + R(C_1 + C_2)s}{C_2 s(1 + RC_1 s)}$$



# Capacitors: Energy and Power

- We have learned so far:


$$i_c(t) = C \frac{dv_c(t)}{dt} \quad p(t) = v(t)i(t)$$

- Power:

$$p_c(t) = v_c(t)i_c(t) = C v_c(t) \frac{dv_c(t)}{dt}$$

- Energy consumed to charge  $C$  from 0 V at  $t = 0$  to  $V_1$  at  $t = t_1$ :
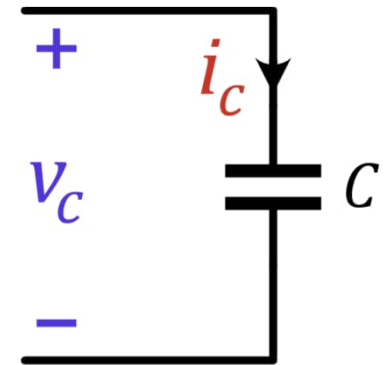
$$W(t_1) = \int_0^{t_1} p_c(t) dt = \int_0^{t_1} C v_c(t) \frac{dv_c(t)}{dt} dt = C \int_0^{V_1} v_c(t) dv_c(t) = \frac{1}{2} C V_1^2$$



# Capacitors: Average Power

- **Energy:**



$$W(t_1) = \frac{1}{2} C V_1^2$$

- **Average Power:**

$$P_{avg} = \frac{W(t_1)}{t_1} = \frac{1}{2t_1} C V_1^2$$

- **Periodic charge/discharge with a clock frequency ( $f_{clk}$ ):**

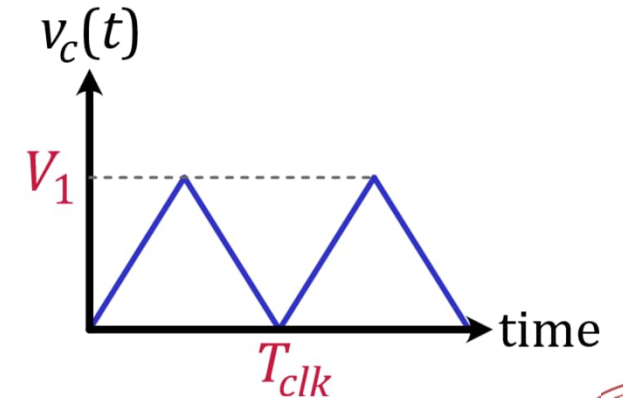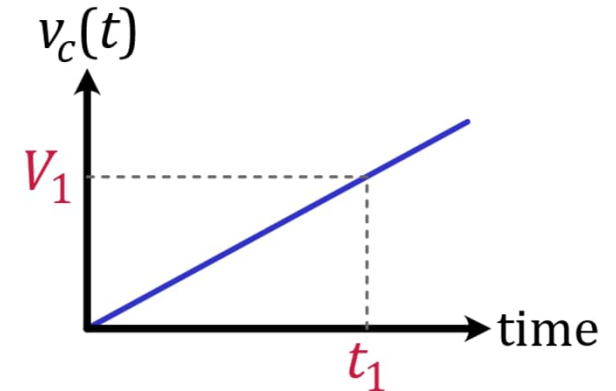
$$P_{avg} = \frac{1}{2 \frac{T_{clk}}{2}} C V_1^2 = f_{clk} C V_1^2$$




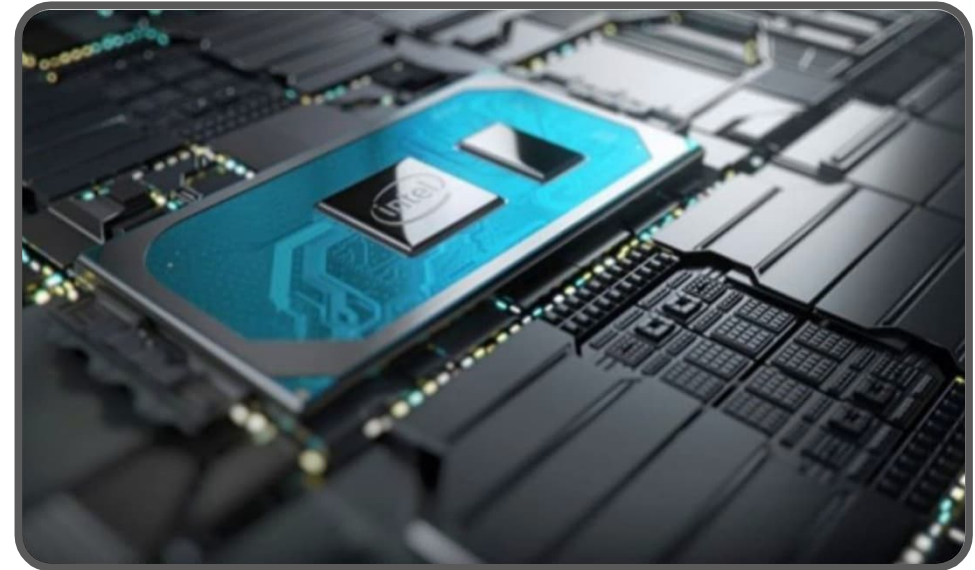
# Pause and Ponder 5

- A real-world example:
  - 10 Billion transistors
  - 10 fF capacitance per transistor
  - Total capacitance:  $C = 100 \mu\text{F}$
  - Power supply:  $V_{DD} = 1 \text{ V}$
  - Clock frequency:  $f_{clk} = 2 \text{ GHz}$
  - Dynamic power:  $P_{avg} = f_{clk} C V_C^2 = 200 \text{ kW}$
  - How could it be possible? What's wrong?!



$$P_{avg} = \alpha f_{clk} C V_C^2$$



# Pause and Ponder 6

- How long does it take to charge a Tesla's battery from 20% to 90% of its full capacity?

$$I = \frac{\Delta Q}{\Delta t} \Rightarrow \Delta t = \frac{\Delta Q}{I} = \frac{(0.9 - 0.2)Q_{max}}{I_{ch}}$$

$$\Rightarrow T_{ch} = \frac{(0.9 - 0.2)Q_{max}}{I_{ch}} = \frac{0.7 \times 230}{20} = 8 \text{ hr} + 3 \text{ min}$$

- How much capacitance does this battery have?

$$C = \frac{Q_{max}}{V_{max}} = \frac{230 \times 3600}{22.5} = 36.8 \text{ kF} \quad \textbf{Tremendous!}$$



Specification	Value
Capacity	230 Ah
Max. voltage	22.5 V
Charger current	20 A



# Pause and Ponder 6

- How much energy is consumed in this process?

$$W_1 = \frac{1}{2} C V_1^2 = \frac{1}{2} C \times (0.2 V_{max})^2$$

$$W_2 = \frac{1}{2} C V_2^2 = \frac{1}{2} C \times (0.9 V_{max})^2$$

$$\Rightarrow \Delta W = \frac{1}{2} C (V_2^2 - V_1^2) = \frac{1}{2} C V_{max}^2 \times (0.9^2 - 0.2^2)$$

$$\Rightarrow \Delta W \approx 7.2 \text{ MJ} = 2 \text{ kWh}$$



Specification	Value
Capacity	230 Ah
Max. voltage	22.5 V
Charger current	20 A



# First-order RC Circuits


- Time-domain analysis

- Initial condition (IC):  $v_c(0^-) = V_0$

**KVL:**  $Ri_c + v_c = v_s \Rightarrow RC \frac{dv_c}{dt} + v_c = v_s$

$$\mathcal{L} \left\{ RC \frac{dv_c}{dt} + v_c \right\} = \mathcal{L}\{v_s\}$$

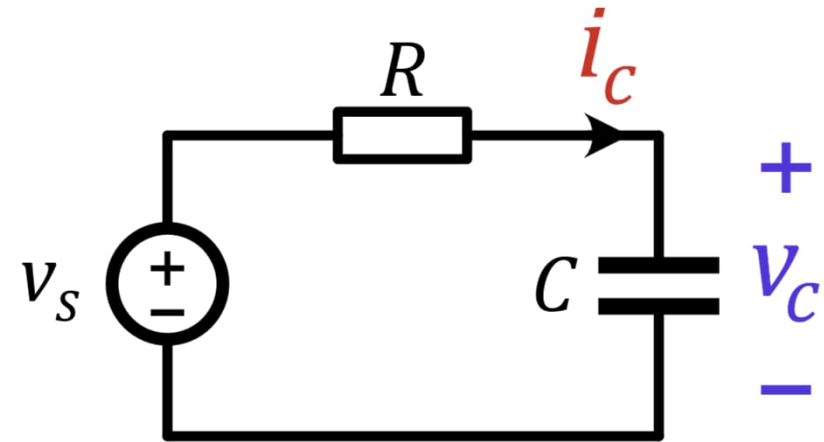
$$RCsV_c + V_c = V_s + RCv_c(0^-) \Rightarrow V_c = \underbrace{\frac{1}{RCs + 1} V_s}_{\text{Source-dependent response}} + \underbrace{\frac{RC}{RCs + 1} V_0}_{\text{IC-dependent response}}$$


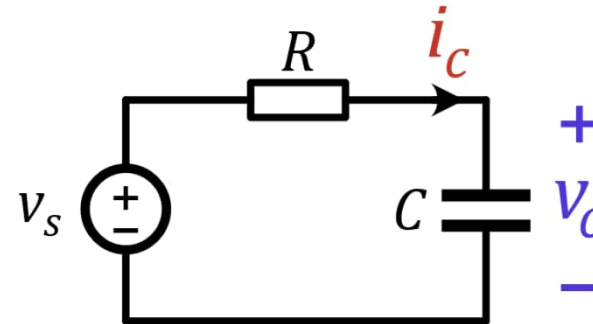
# First-order RC Circuits

- impulse response ( $h(t)$ )

$$v_s(t) = \delta(t) \Rightarrow V_s = 1$$




$x(t)$	$X(s)$
$e^{-at}u(t)$	$\frac{1}{s+a}$

Transfer function:

$$V_c = H(s) = \frac{1}{RCs + 1} = \frac{1}{RC} \cdot \frac{1}{s + \frac{1}{RC}}$$

$$h(t) = \frac{1}{RC} \exp\left(-\frac{t}{RC}\right) u(t)$$

Time constant:  $\tau = RC$

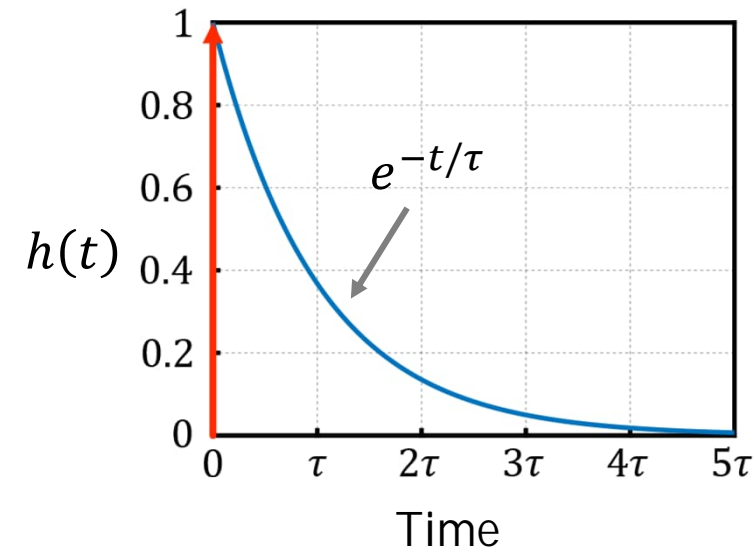

# First-order RC Circuits



- IC-dependent response

$$V_{c,IC} = \frac{RC}{RCs + 1} V_0$$

$$V_{c,IC} = \frac{1}{s + \frac{1}{RC}} V_0$$

$$v_{c,IC}(t) = V_0 \exp\left(-\frac{t}{RC}\right) u(t)$$

**Time constant:**  $\tau = RC$

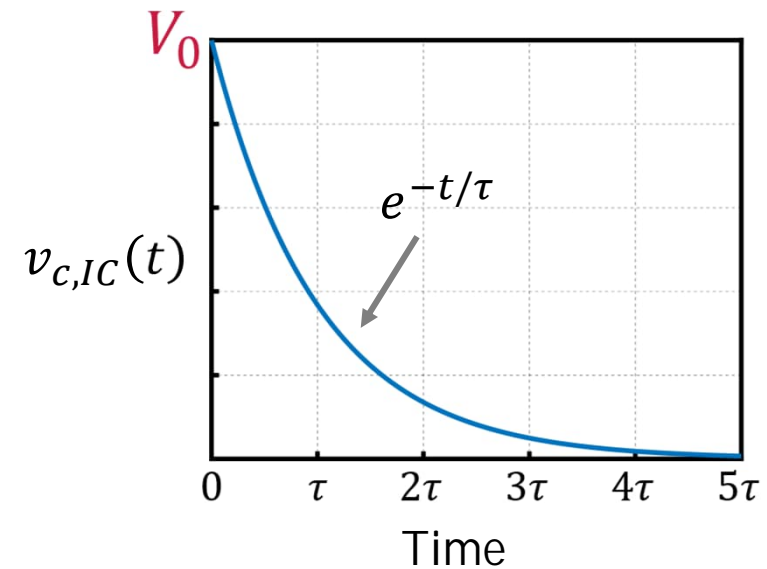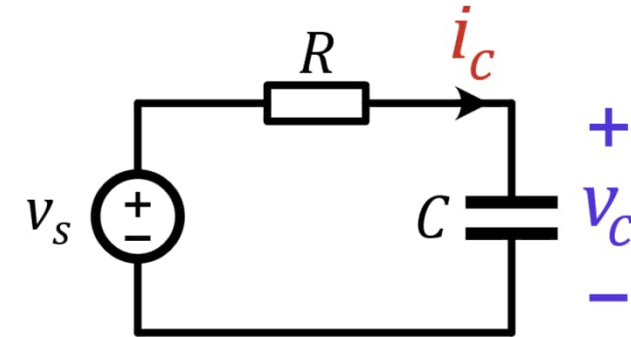





# First-order RC Circuits

- Total response

$$v_c(t) = h(t) + v_{c,IC}(t)$$

$$v_c(t) = \frac{1}{\tau} \exp\left(-\frac{t}{\tau}\right) u(t) + V_0 \exp\left(-\frac{t}{\tau}\right) u(t)$$
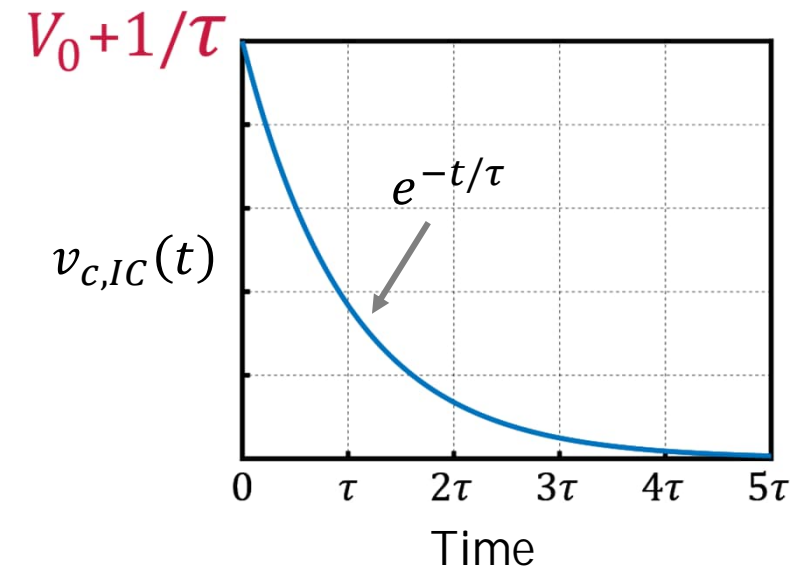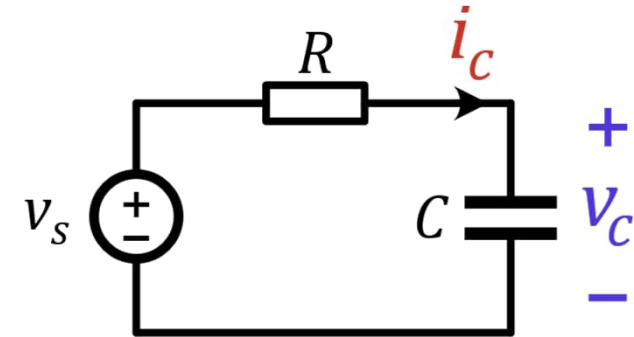
$$v_c(t) = \left(\frac{1}{\tau} + V_0\right) \exp\left(-\frac{t}{\tau}\right) u(t)$$



# First-order RC Circuits

- **Frequency-domain analysis**


- Simple voltage division if we consider impedances:

$$V_C(s) = \frac{Z_C}{Z_C + Z_R} V_S(s) = \frac{\frac{1}{Cs}}{\frac{1}{Cs} + R} V_S(s) = \frac{1}{1 + RCs} V_S(s)$$

- Impulse response ( $V_S(s) = 1$ ):

$$H(s) = \frac{1}{1 + \tau s}$$


The same result

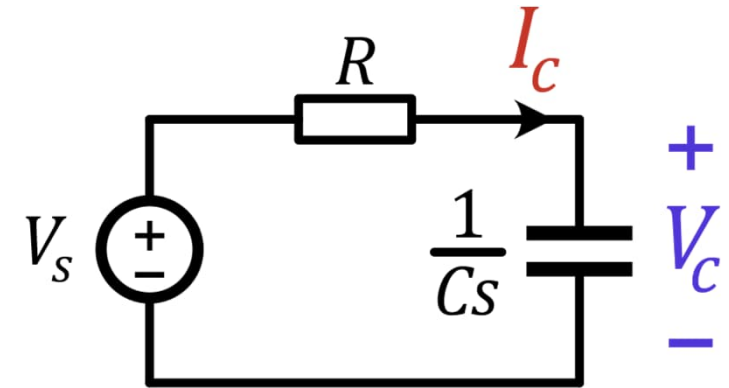
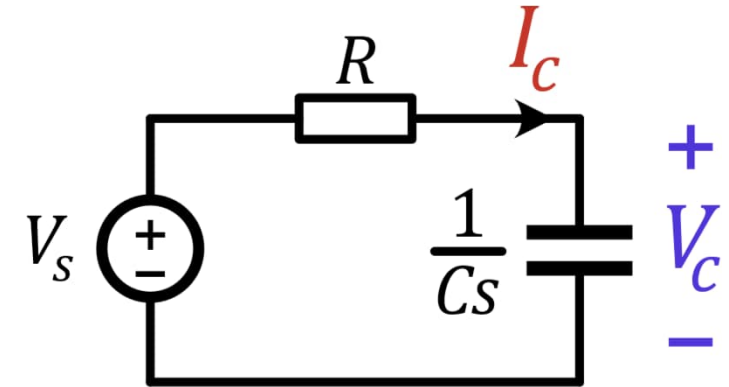
# Pause and Ponder 7

- Find a transfer function for  $I_c(s)$ .

$$I_c(s) = \frac{1}{Z_c} V_c(s) = \frac{1}{\frac{1}{Cs}} V_c(s) = \frac{Cs}{1 + RCs}$$



- Find the impulse response of  $v_R(t)$ .

$$V_R(s) = RI_c(s) = \frac{RCs}{1 + RCs}$$

$$v_R(t) = \mathcal{L}^{-1}\{V_R(s)\} = (RC) \frac{d}{dt} \left( \mathcal{L}^{-1} \left\{ \frac{1}{1 + RCs} \right\} \right) = \delta(t) - \frac{1}{\tau} \exp\left(-\frac{t}{\tau}\right) u(t)$$



# First-order RC Circuits


- Step Response

$$v_s(t) = u(t) \Rightarrow V_s(s) = \frac{1}{s}$$

$$V_c(s) = H(s) \cdot V_s(s) = \frac{1}{1 + \tau s} \cdot \frac{1}{s}$$

$$\Rightarrow V_c(s) = \frac{1}{\tau} \cdot \frac{1}{s \left( s + \frac{1}{\tau} \right)} = \frac{1}{s} - \frac{1}{s + \frac{1}{\tau}}$$
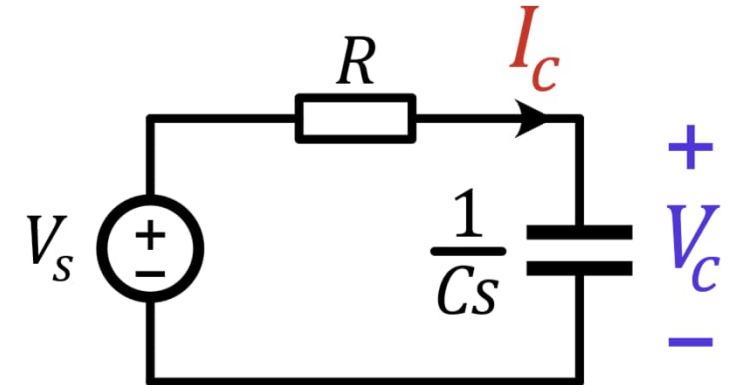
$$\Rightarrow v_c(t) = u(t) - \exp\left(-\frac{t}{\tau}\right) u(t) = \left(1 - \exp\left(-\frac{t}{\tau}\right)\right) u(t)$$




# First-order RC Circuits

- Step Response

$$v_c(t) = \left(1 - \exp\left(-\frac{t}{\tau}\right)\right) u(t)$$

**Initial value:**  $v_c(0) = 0$

**Final value:**  $v_c(\infty) = 1$

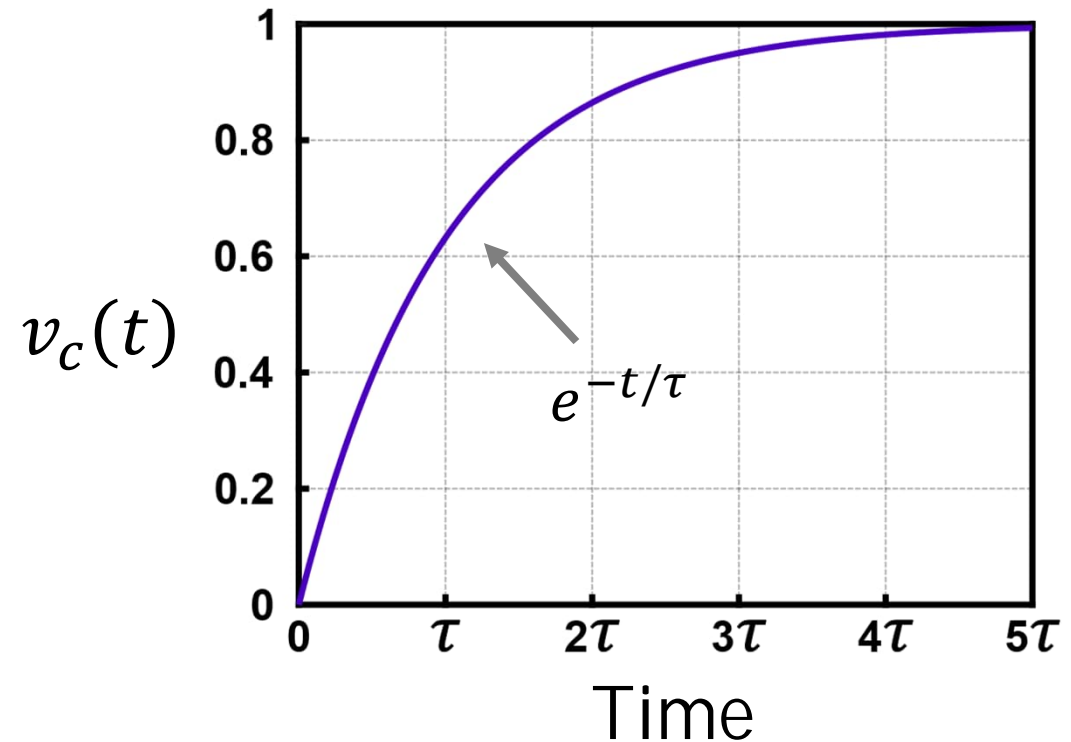

# First-order RC Circuits


- Current's Step Response

$$i_c(t) = c \frac{dv_c}{dt}$$

$$i_c(t) = \frac{1}{R} \exp\left(-\frac{t}{\tau}\right) u(t)$$

**Initial value:**  $i_c(0) = \frac{1}{R}$

**Final value:**  $i_c(\infty) = 0$

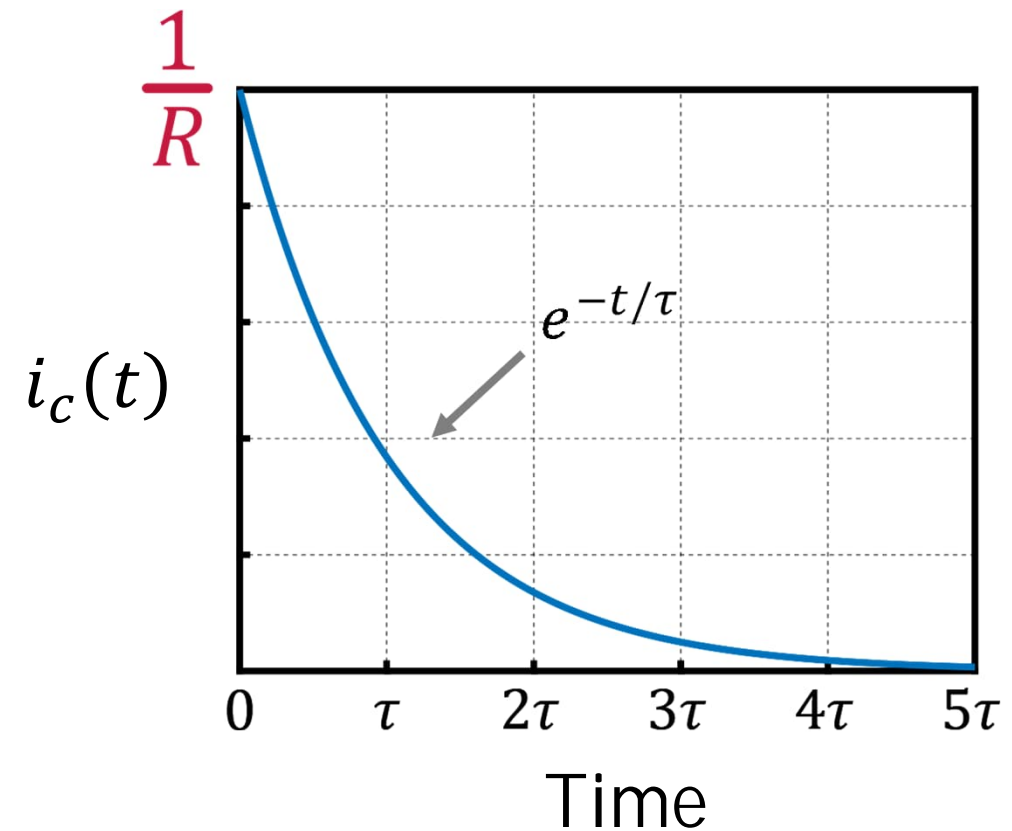

# Capacitor's Model when $t \rightarrow 0^+$

- Capacitor's **voltage** must be **continuous**.

$$i_c(t) = C \frac{dv_c}{dt} \Rightarrow \text{if } v_c = \Delta V u(t): i_c(t) \rightarrow \infty$$



Physically  
Impossible

$$\Rightarrow v_c(0^+) = v_c(0^-) = V_0$$

- What about current?

$$i_c(0^+) = \frac{V_s - V_0}{R}$$

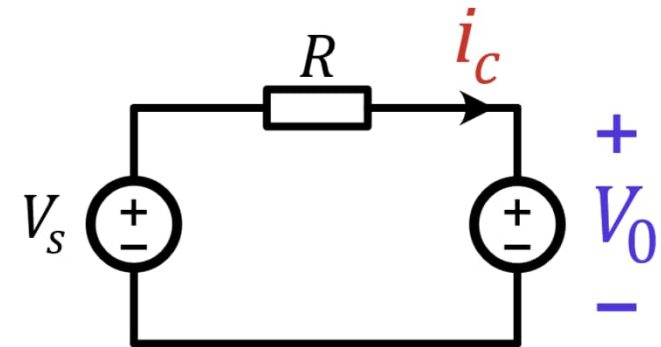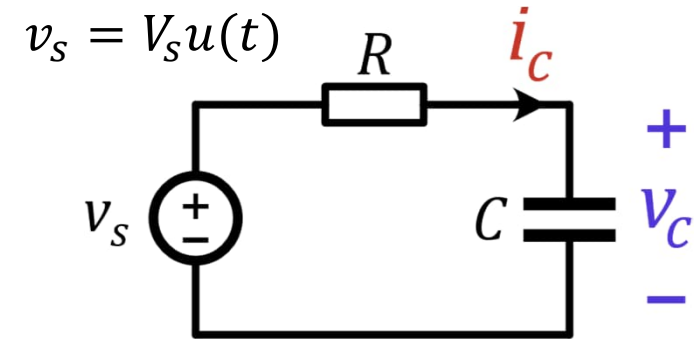Capacitor acts like a **voltage source**, showing **zero impedance**





# Capacitor's Model when $t \rightarrow \infty$

- After a sufficiently long time ( $t > 5\tau$ ), the voltage across the capacitor reaches a stable states.
- This duration is called **settling time**.
- **No current** flows into the circuit anymore.

$$\left. \frac{dv_c}{dt} \right|_{t \rightarrow \infty} = 0 \Rightarrow i_c(\infty) = 0, v_c(\infty) = V_s$$

Capacitor acts like **an open-circuit**,  
showing **infinite impedance**

