

Elektronik

Basic Components and Circuit Theory

EITA10


Iman Ghotbi

Mars 2025



We learned


Voltage Source

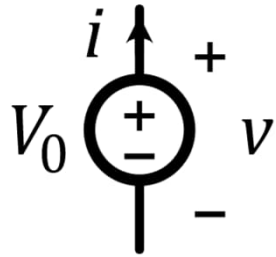


$$v_{BA} = - \int_A^B \vec{E} \cdot d\vec{l}$$




Current Source

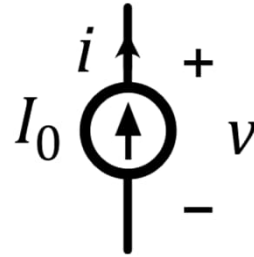


$$i = \frac{dq}{dt}$$

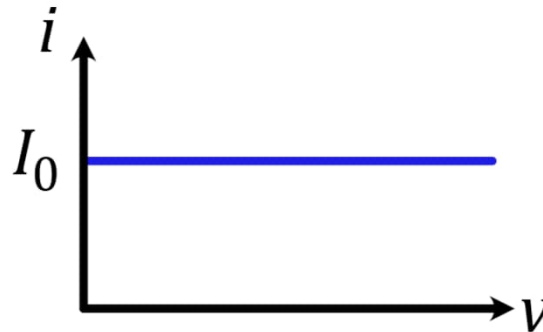

Resistor

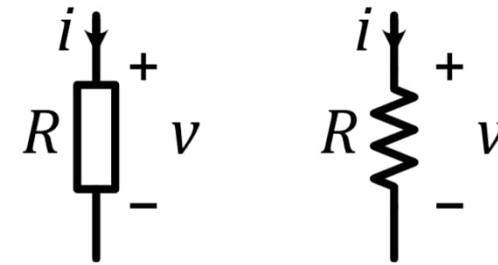

$$v = Ri \quad i = Gv$$

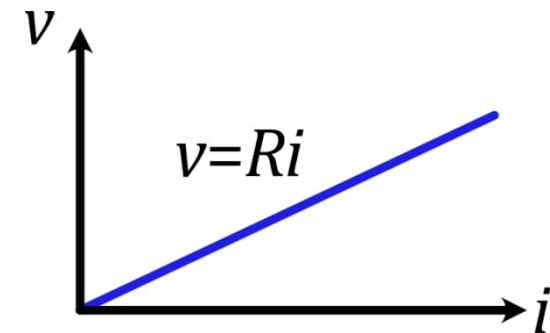

Today we learn


- Resistive circuits
- Kirchhoff's voltage and current laws (KVL and KCL)
- Parallel and Series combination
- Voltage and current division
- Superposition
- Thevenin's and Norton's theorems
- Nodal analysis



Circuit Theory


Physical Reality

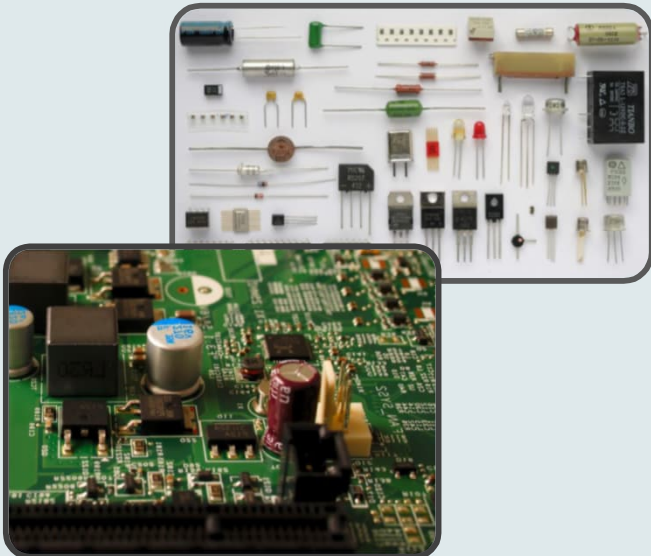- Fields
- Flows
- Charges
- Material
- Particles



Circuit Models

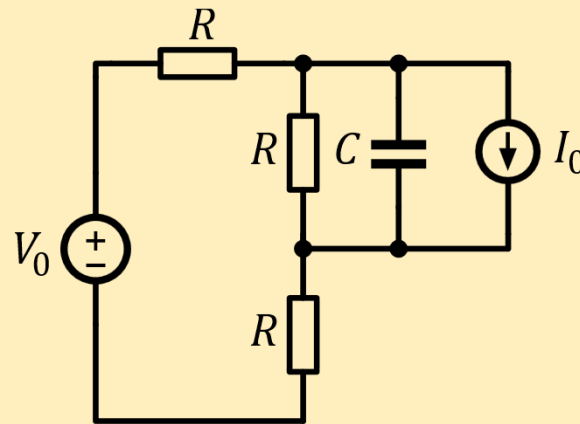- Abstracts
- Behavioral models
- Linear/non-linear
- Sources
- Passive/active components




Mathematical Calculations

- Matrices
- Algebraic equations
- Partial differential equations
- System of linear/non-linear equations
- Graphical methods
- Numerical methods

$$\mathbf{V} = \mathbf{Z}\mathbf{I}$$

$$\mathbf{V} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} \quad \mathbf{I} = \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$
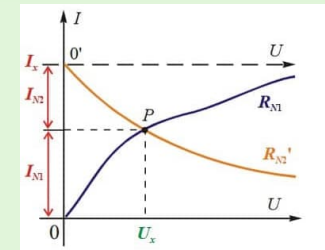
$$\mathbf{Z} = \begin{pmatrix} Z_{11} & 0 & Z_{13} \\ 0 & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{pmatrix}$$



Electric Circuit Essentials

- **Wire**


- ideal conductor
- No voltage difference
- Can handle any current level

- **Circuit element**

- Sources
- Passives: Resistors, capacitors, inductors
- Actives: Transistors, diodes, ...

- **Node**

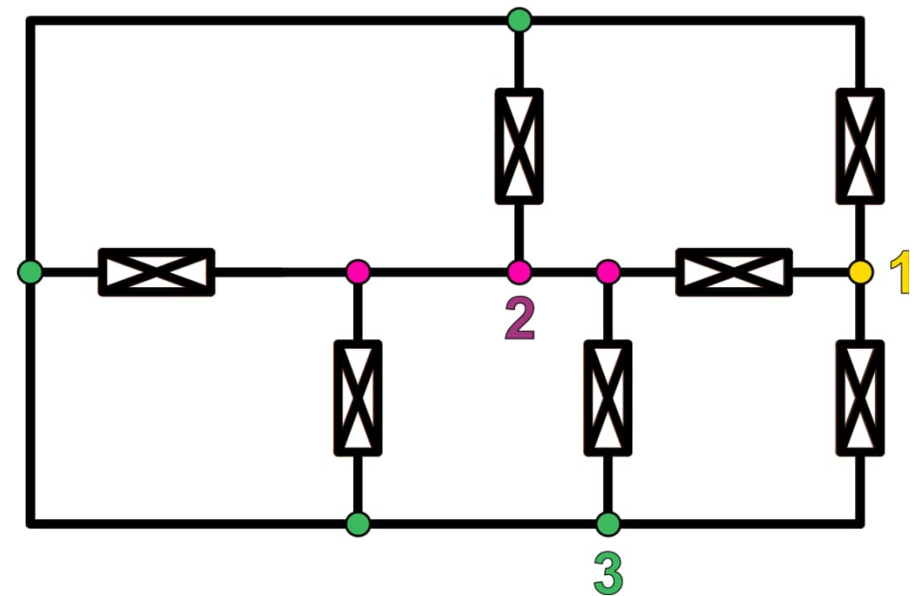- A junction where two or more branches intersect
- Two nodes must have different voltages (no wire connecting them directly)




Electric Circuit Essentials

- **Loop**

- A subset of branches forming a closed path
- Might pass by several nodes (at least two)


- **Ground Node**

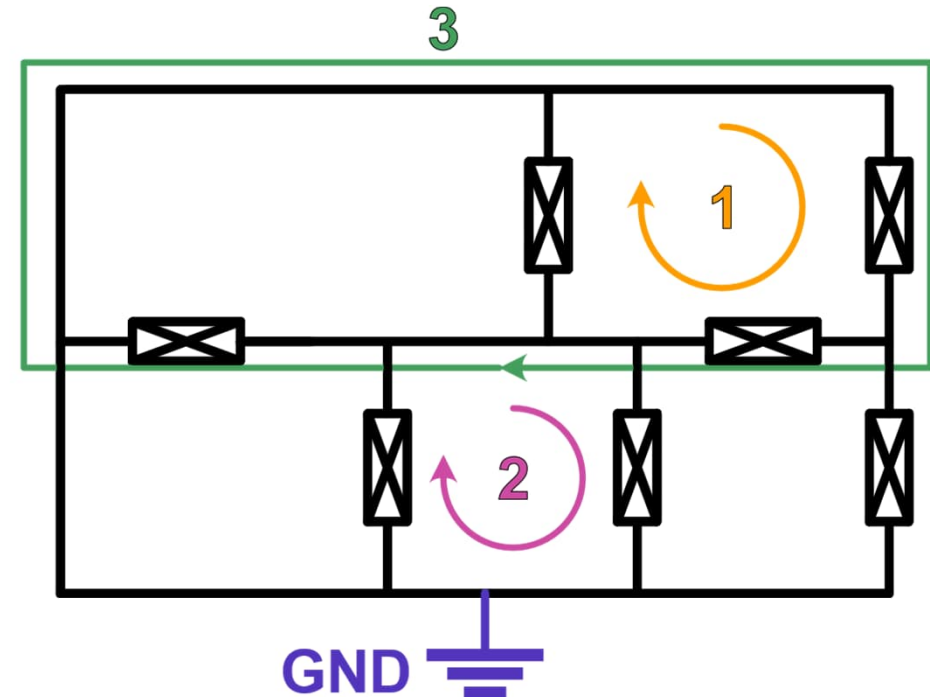- The node with the maximum connected branches
- Voltage reference for our calculations and measurements
- Denoted by GND
- $V(\text{GND})=0 \text{ V}$




Kirchhoff's Voltage Law (KVL)

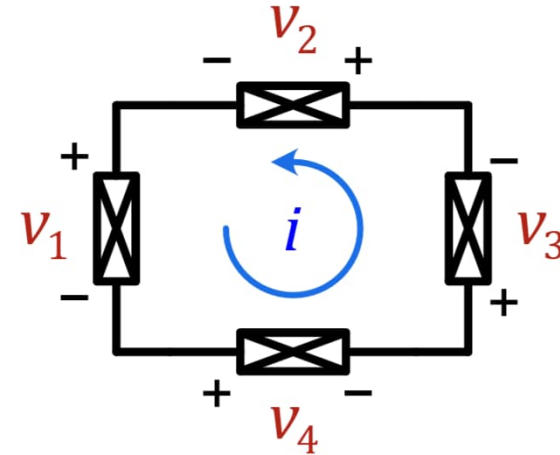- The algebraic **sum of the voltage** drops or rises around **any loop** in a circuit is always equal to **zero**.
- Current-voltage direction
 - current flows across an element from + to -
- Voltage sources (pumps of charge)
 - Follow the polarity of the source in the direction of circulating around the loop



$$\sum_{k=1}^4 v_k = 0$$

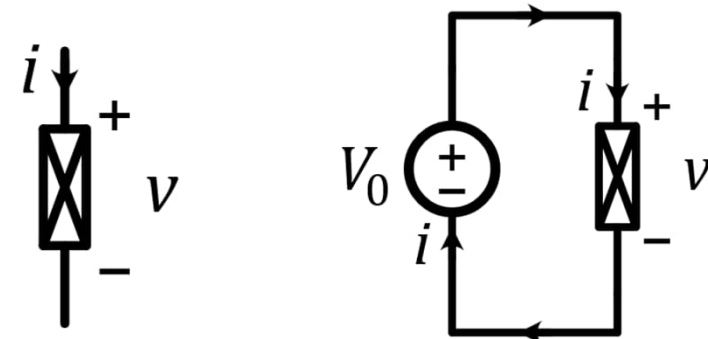


$$+v - V_0 = 0$$



KVL– Example

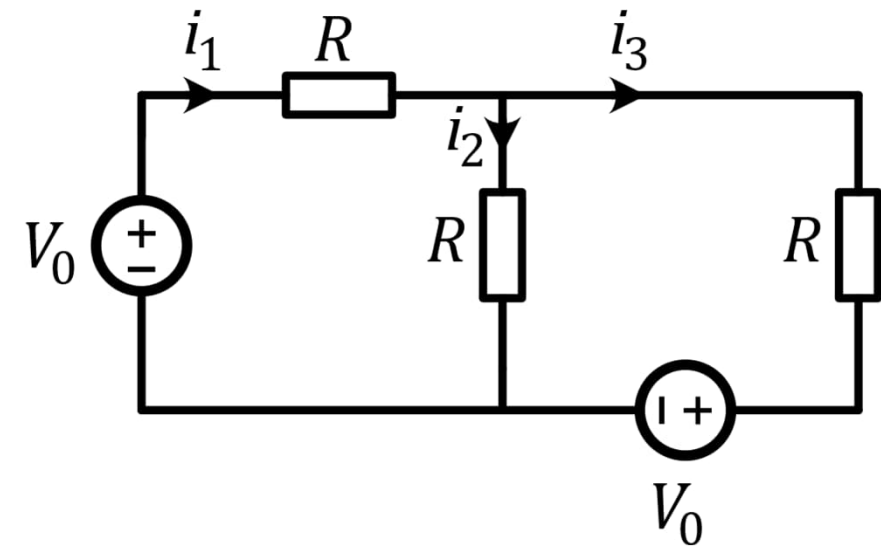- Write all KVLs in terms of i_1 , i_2 and i_3 .



KVL– Example

- Write all KVLs in terms of i_1 , i_2 and i_3 .

$$\text{KVL 1: } Ri_1 + Ri_2 - V_0 = 0$$


$$\text{KVL 2: } Ri_3 + V_0 - Ri_2 = 0$$

$$\text{KVL 3: } Ri_1 + Ri_3 + V_0 - V_0 = 0$$

Therefore:


$$i_1 = -i_3$$

$$i_1 + i_2 = \frac{V_0}{R}$$

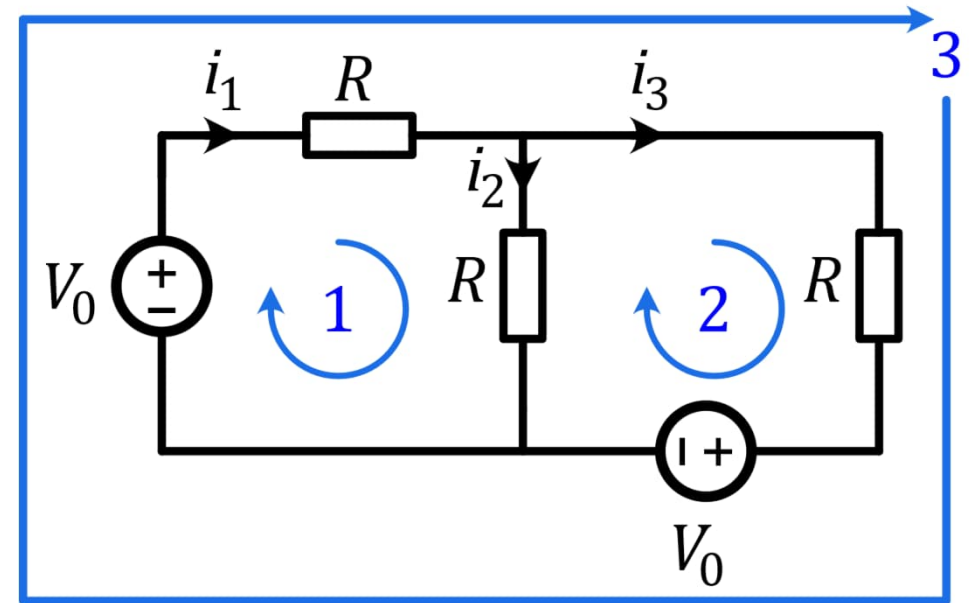

Kirchhoff's Current Law (KCL)

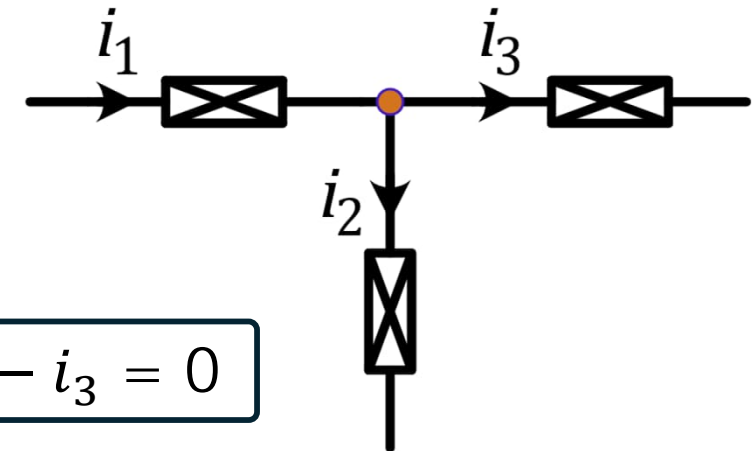- The algebraic **sum of the currents** entering/leaving **a node** is always equal to **zero**.
- Current direction
 - Entering \rightarrow positive
 - Leaving \rightarrow negative




$$i_1 - i_2 - i_3 = 0$$

$$\sum I_{in} = \sum I_{out}$$



KCL– Example

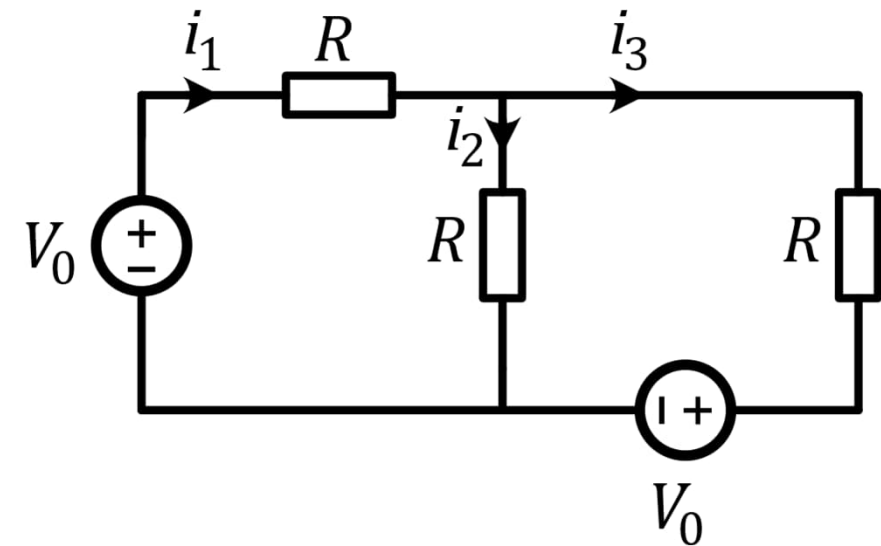- Write all KCLs in terms of i_1 , i_2 and i_3 .



KCL– Example

- Write all KVLs in terms of i_1 , i_2 and i_3 .


$$\text{KCL @ } \mathbf{n}_1: i_1 - i_2 - i_3 = 0$$

$$\text{KCL @ } \mathbf{n}_2: i_3 + i_2 - i_1 = 0$$

Therefore:

$$i_1 = i_2 + i_3$$


One of KCLs seems redundant!

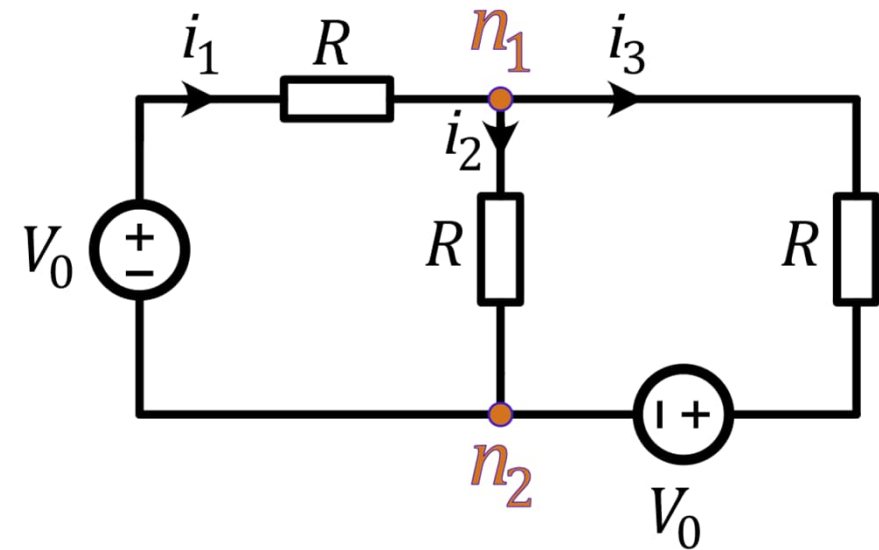

Pause and Ponder 1

- In a circuit with n_t nodes, how many **independent KCLs** can be written?

$$n = n_t - 1$$

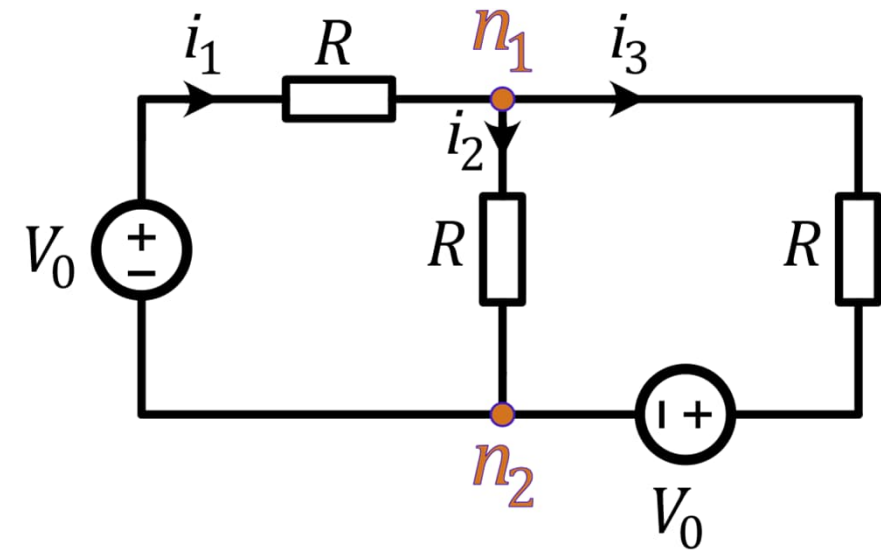

KVL+KCL → System of Equations

- Express i_1 , i_2 and i_3 in terms of V_0 .

From KVL:


$$i_1 = -i_3 \quad i_1 + i_2 = \frac{V_0}{R}$$

From KCL:

$$i_1 = i_2 + i_3$$

Therefore:
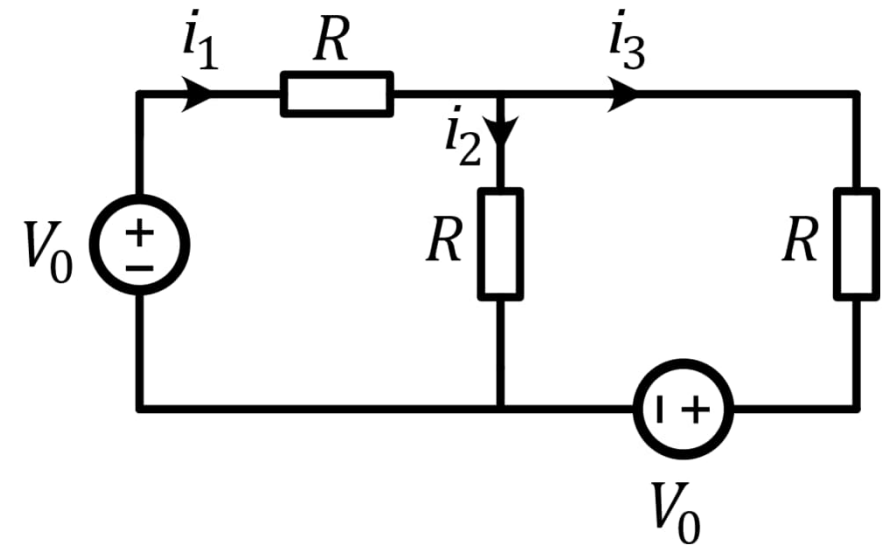
$$i_2 = 2i_1 \Rightarrow i_1 = \frac{V_0}{3R}, \quad i_2 = \frac{2V_0}{3R}, \quad i_3 = -\frac{V_0}{3R}$$



KVL+KCL → System of Equations


- Write a system of equation in matrix format.

KVL: $i_1 + i_3 = 0$

KVL: $i_1 + i_2 = \frac{V_0}{R}$

KCL: $i_1 - i_2 - i_3 = 0$
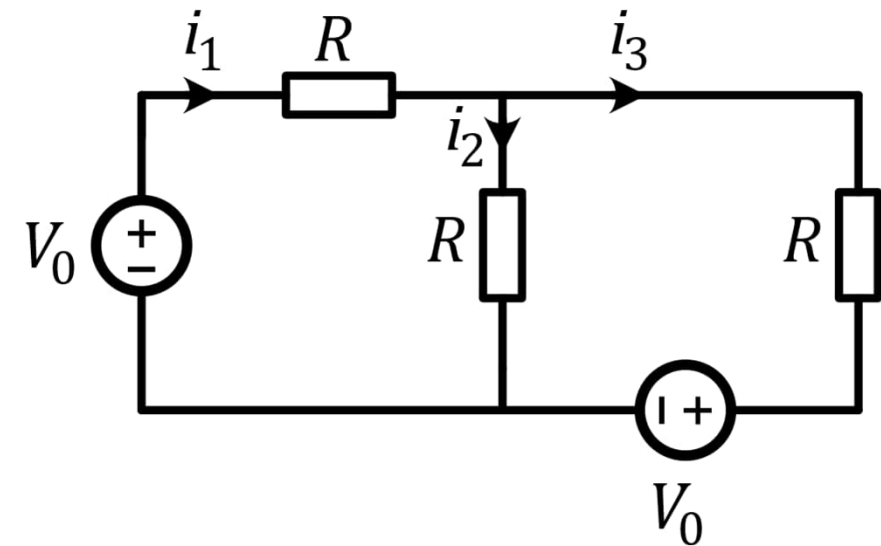
$$\begin{pmatrix} 1 & 0 & 1 \\ 1 & 1 & 0 \\ 1 & -1 & -1 \end{pmatrix} \begin{pmatrix} i_1 \\ i_2 \\ i_3 \end{pmatrix} = \begin{pmatrix} 0 \\ \frac{V_0}{R} \\ 0 \end{pmatrix}$$




Series Coupling

- Two or more elements are connected in series if **the same current** flows through them.

$$i_1 = i_2 = i_3 = i$$

$$v_1 + v_2 + v_3 = v_x$$

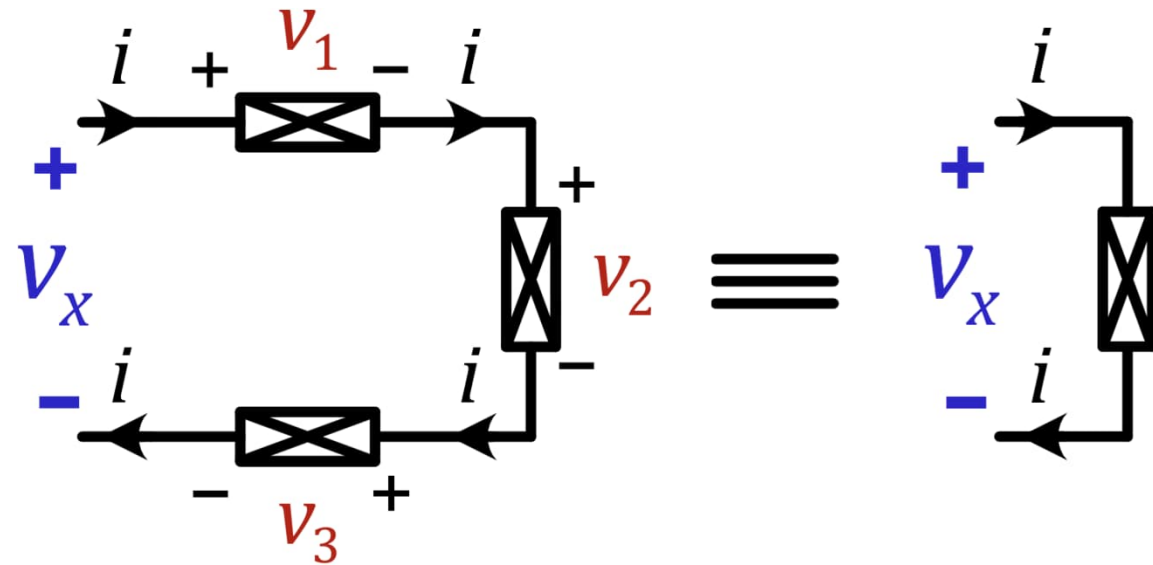


Series Voltage Sources

- The total voltage difference equals **the sum of voltage sources** according to their **polarity**.

$$V_{BA} = V_1 + V_2 + V_3 - V_4$$

$$V_{BA} = \sum_{k=1}^N V_k$$

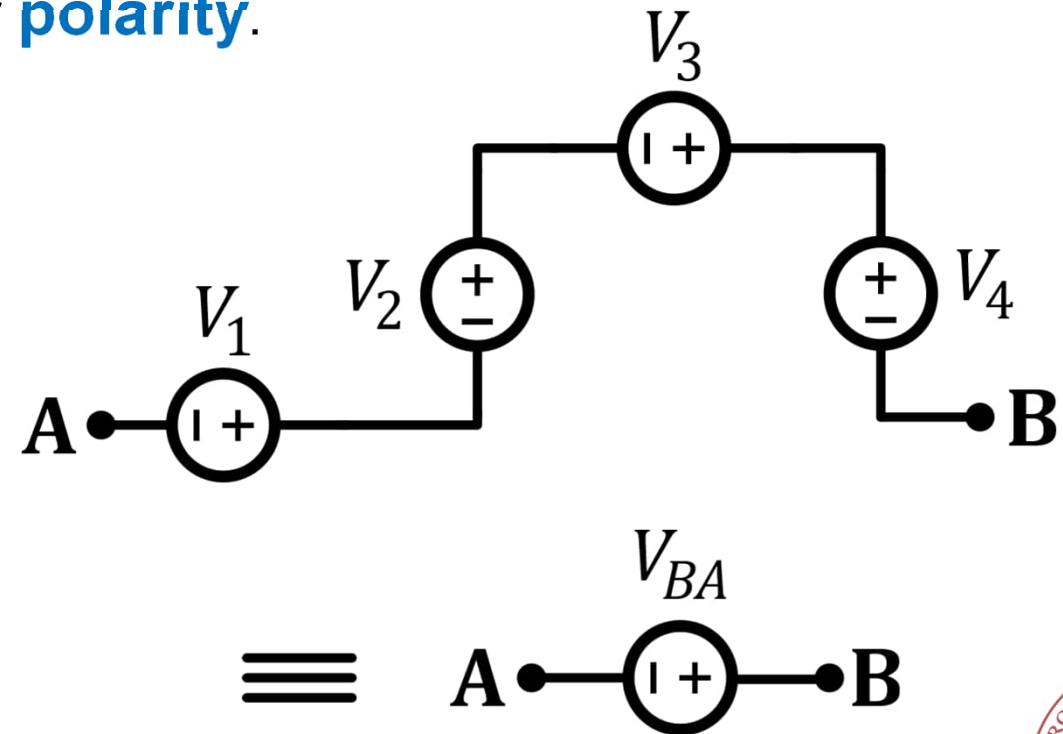


Series Resistors

- Series resistors can be replaced by an equivalent resistor whose value is equal to the **sum of their individual resistances**.

$$V_x = R_1 i + R_2 i + R_3 i + R_4 i$$


$$V_x = \left(\sum_{k=1}^4 R_k \right) i$$

$$R_{eq} = \sum_{k=1}^N R_k$$

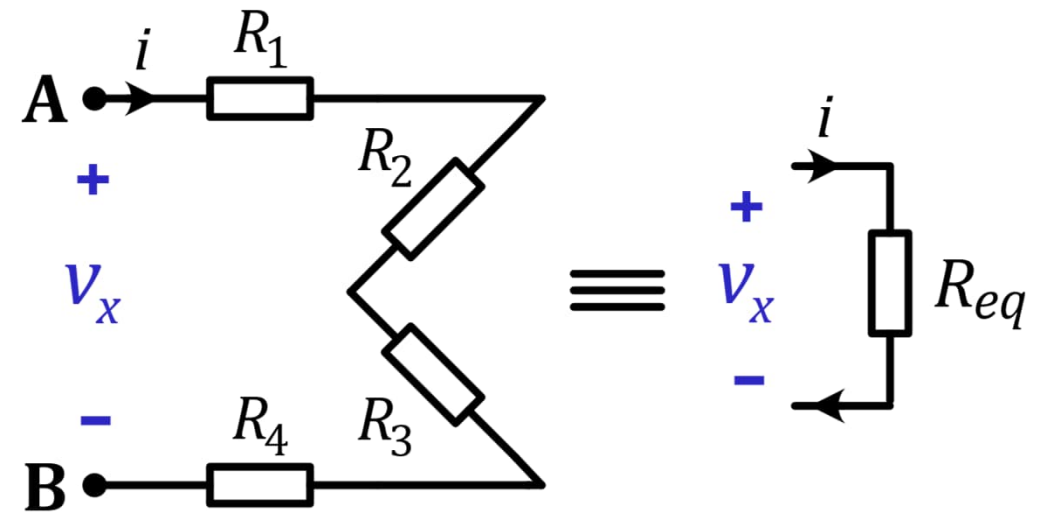


Pause and Ponder 2

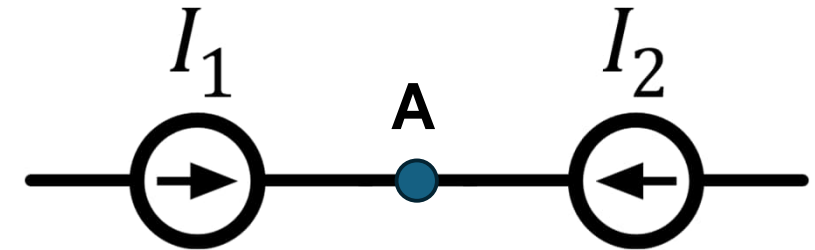- What would happen if a student were to connect two ideal independent current sources in series?
- Does connecting any circuit element in series with an ideal independent current source make any difference to the rest of the circuit?



$$\text{KCL: } I_1 = -I_2$$

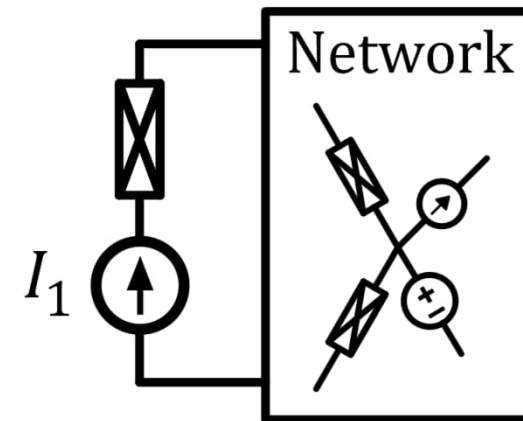


Parallel Coupling

- Two or more components are connected **across the same two nodes**.

$$v_1 = v_2 = v_3 = v_x$$

$$i_1 + i_2 + i_3 = i$$

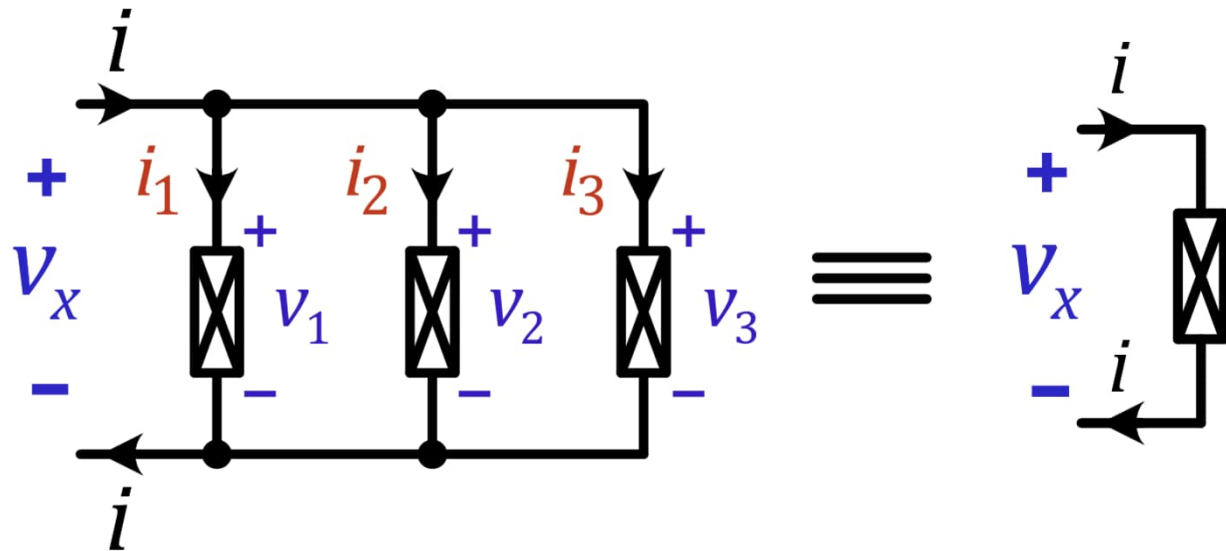


Parallel Current Sources

- Parallel current sources can be replaced by an equivalent current source whose value is equal to **the sum of their individual currents, according their direction.**

$$I_{eq} = I_1 + I_2 - I_3$$

$$I_{eq} = \sum_{k=1}^N I_k$$

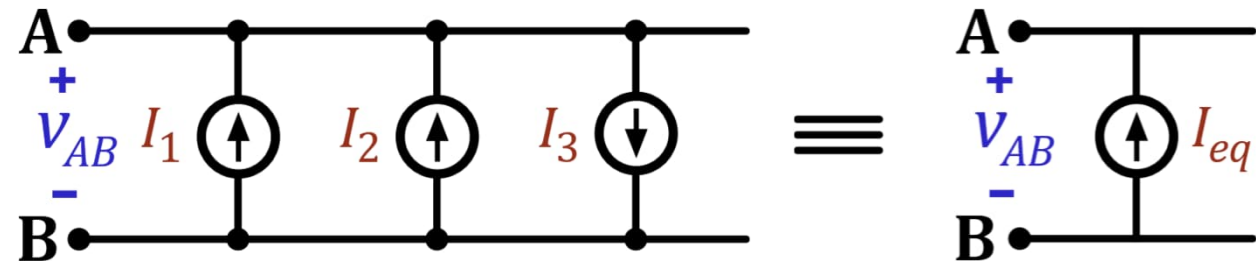

Parallel Resistors


- Parallel resistors can be replaced by an equivalent resistor whose conductance (G_{eq}) is equal to the **sum of their individual conductances**.

$$i_x = \frac{V_{AB}}{R_1} + \frac{V_{AB}}{R_2} + \frac{V_{AB}}{R_3} \quad \& \quad G_k = \frac{1}{R_k}$$

$$i_x = (G_1 + G_2 + G_3) \cdot V_{AB}$$


$$G_{eq} = \sum_{k=1}^N G_k$$

$$R_{eq} = \frac{1}{G_{eq}}$$

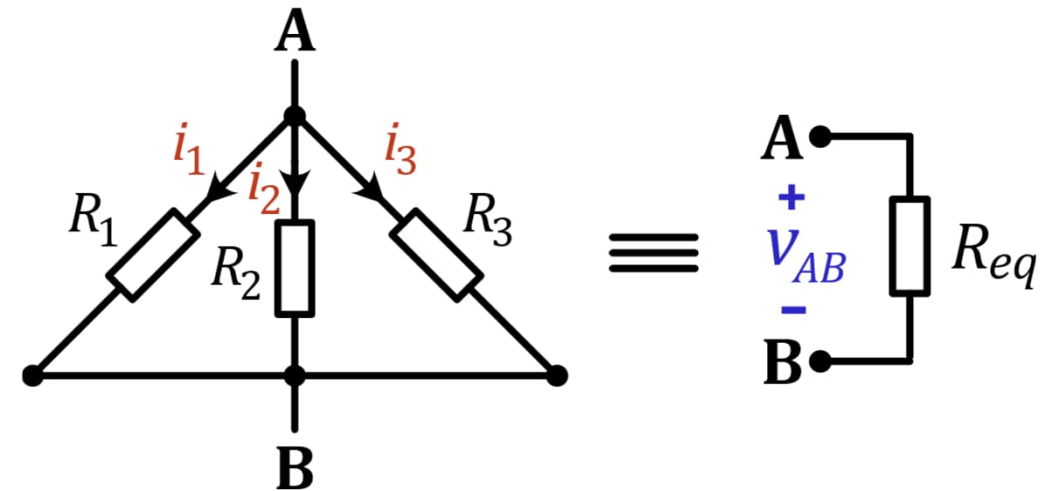


Pause and Ponder 3

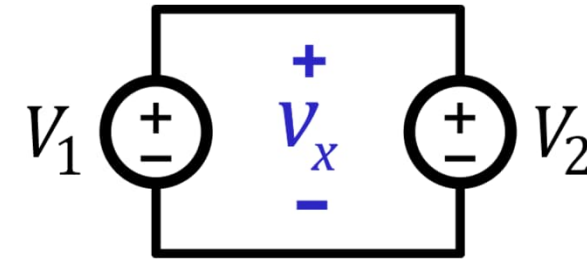- What would happen if a student were to connect two ideal independent voltage sources in parallel?
- Does connecting any circuit element in parallel with an ideal independent voltage source make any difference to the rest of the circuit?




$$\text{KVL: } V_1 = V_2$$

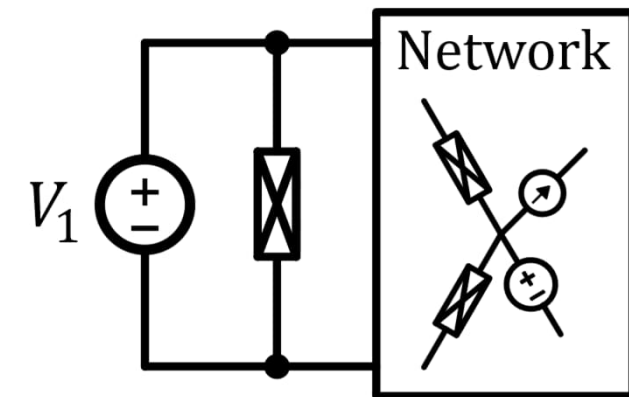

Example of Equivalent Resistance

- Find the equivalent resistance.

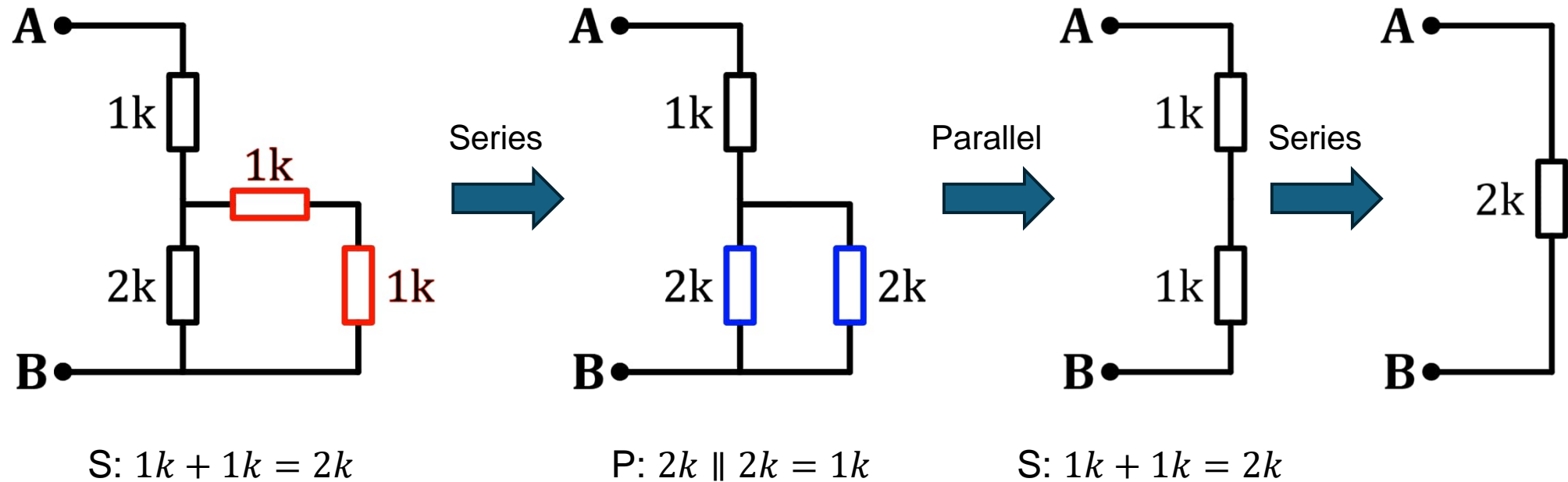


Voltage Division

- Within a **series combination**, the voltage is distributed among the individual elements according to **their respective resistances**.

$$v_{AB} = \sum_{n=1}^N v_n = i \cdot \sum_{n=1}^N R_n = i \cdot R_{tot}$$

$$v_k = R_k i = \frac{R_k}{R_{tot}} v_{AB}$$
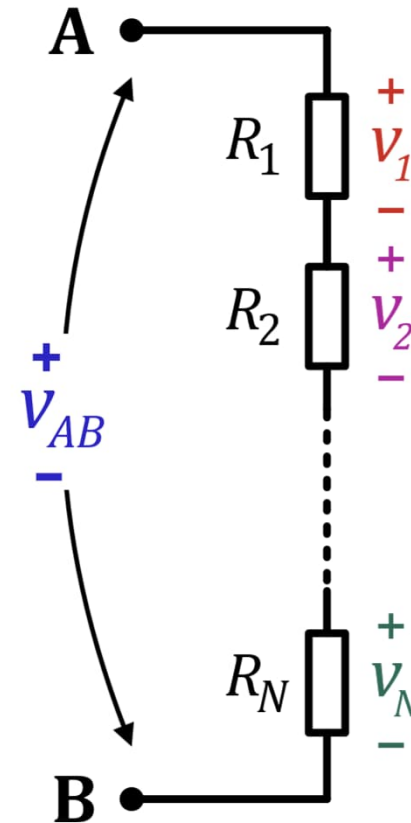
$$v_k = \frac{R_k}{\sum_{n=1}^N R_n} v_{AB}$$




Current Division

- Within a **parallel combination**, the current is distributed among the individual elements according to **their respective conductances**.

$$i_{tot} = \sum_{n=1}^N G_n \cdot v_{AB}$$


$$i_k = G_k v_{AB}$$
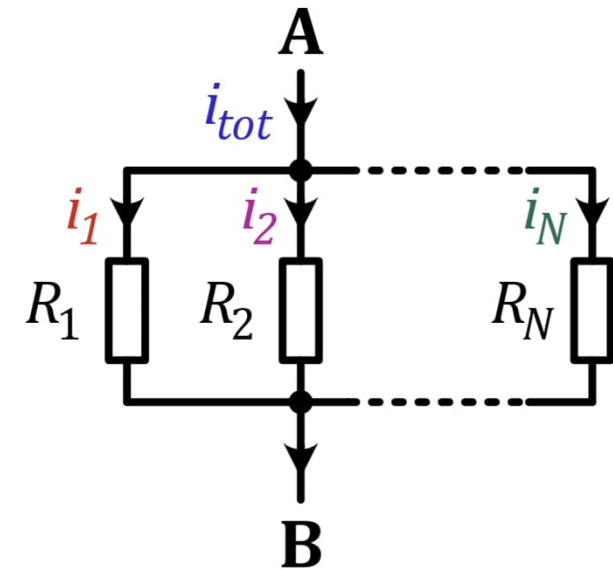
$$i_k = \frac{G_k}{\sum_{n=1}^N G_n} i_{tot}$$





Example

- Find the value of i_x .

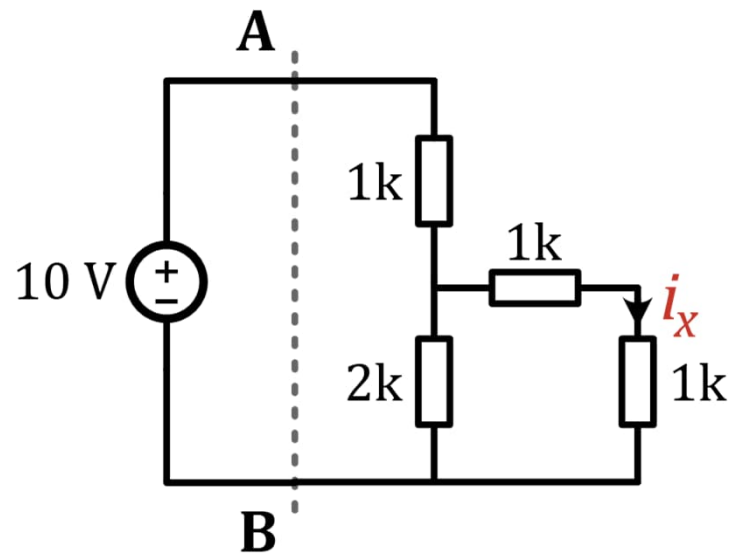

Example

- Find the value of i_x .

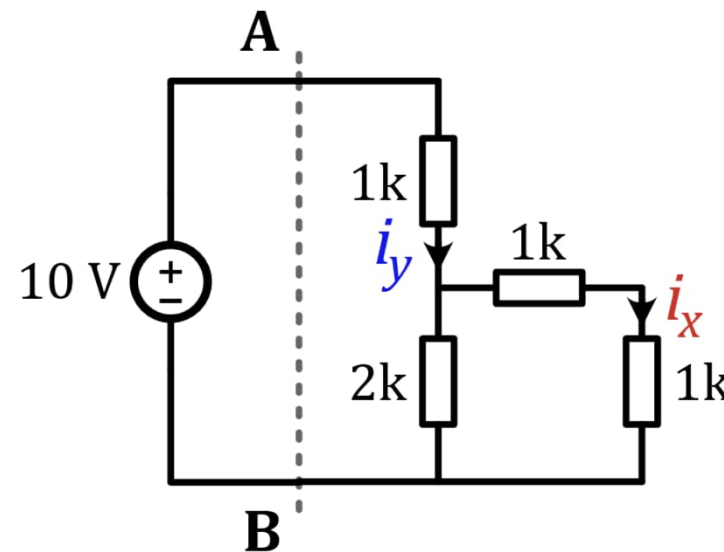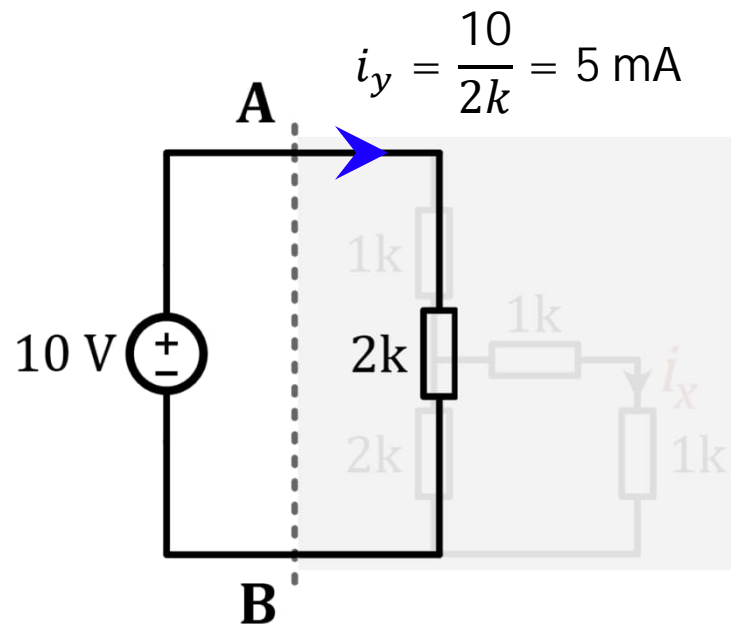


$$i_x = \frac{G_{(1k+1k)}}{G_{(1k+1k)} + G_{2k}} i_y$$
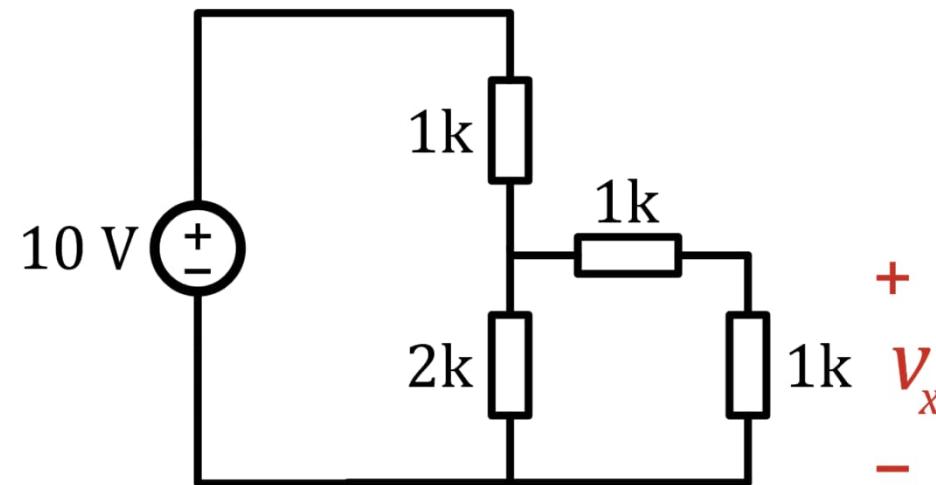
$$i_x = \frac{\frac{1}{1k + 1k}}{\frac{1}{1k + 1k} + \frac{1}{2k}} i_y = 2.5 \text{ mA}$$







Pause and Ponder 4

- In the previous example, find v_x by using voltage division.







Dependent Sources

	Voltage Source	Current Source
Voltage-Controlled	$v = A_v (v_x)$ VCVS 	$i = G_m (v_x)$ VCCS 
Current-Controlled	$v = R_m (i_x)$ CCVS 	$i = A_i (i_x)$ CCCS 



Linear Dependent Sources

	Voltage Source	Current Source
Voltage-Controlled	$v = A_v v_x$  <p>VCVS</p>	$i = G_m v_x$  <p>VCCS</p>
Current-Controlled	$v = R_m i_x$  <p>CCVS</p>	$i = A_i i_x$  <p>CCCS</p>




Superposition

- In a linear circuit, the response (such as voltage or current) due to **multiple sources** can be determined by considering **the effects of each independent source individually** and then **summing up** these individual responses.

$$v_x = \sum_{n=1}^N A_n V_n + \sum_{m=1}^M R_m I_m$$

N : number of independent voltage sources

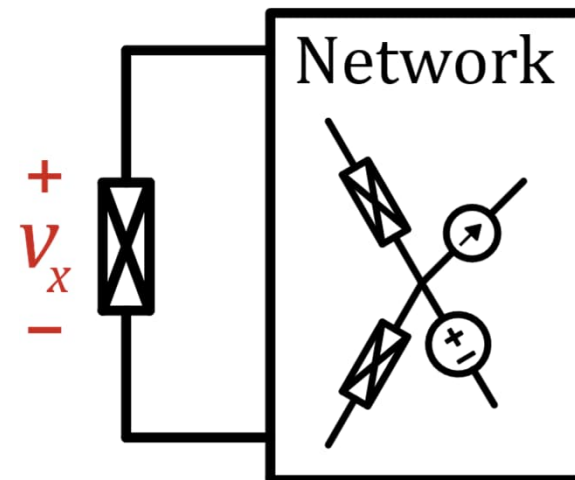M : number of independent current sources




Using Superposition in Circuit Analysis

Step 1: Calculate the contribution of each independent source, one by one.

- Turn off all other independent sources.
 - **Voltage sources** → **Short-circuit** (a wire)
 - **Current source** → **Open-circuit** (remove it)
- Use nodal analysis, current/voltage division, etc.

Step 2: Sum up individual responses.

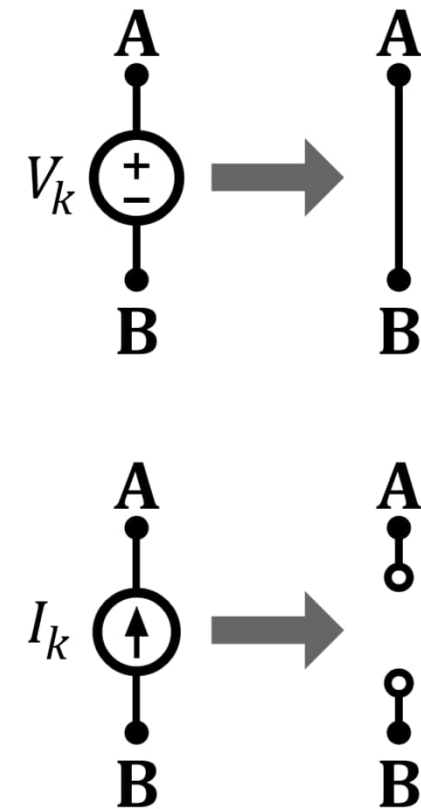

Example of Superposition

- Find the value of i_x .




- Effect of 10 V source (already calculated):

$$i_{x_{10V}} = 2.5 \text{ mA}$$

- Effect of 2 mA source:

- Short-circuit 10 V source
- Use of current division and parallel/series connections


$$i_{x_{4mA}} = 2.5 \text{ mA}$$

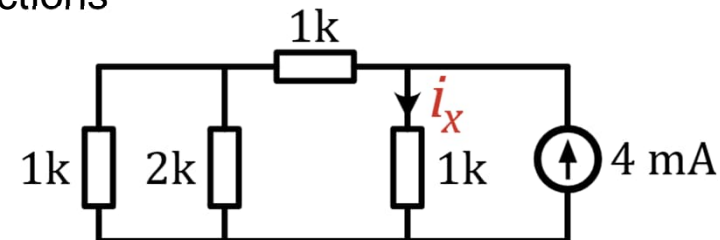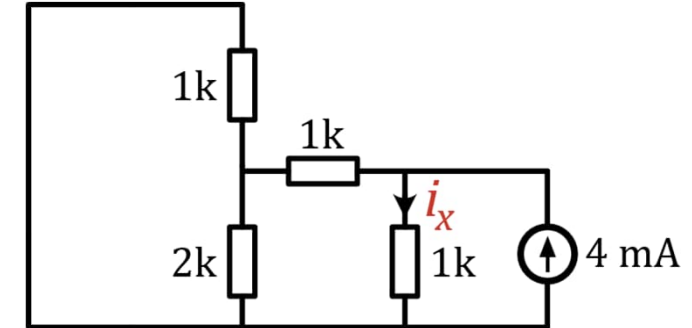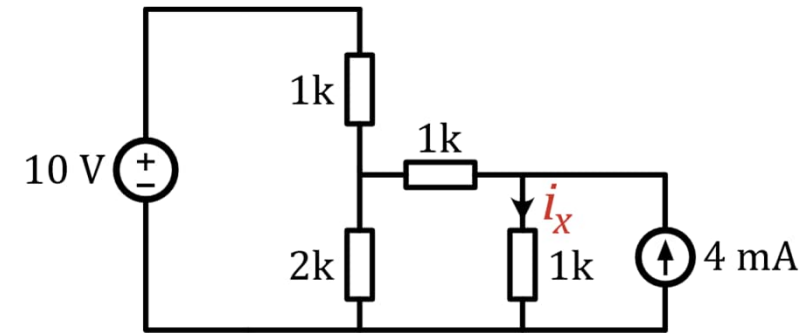

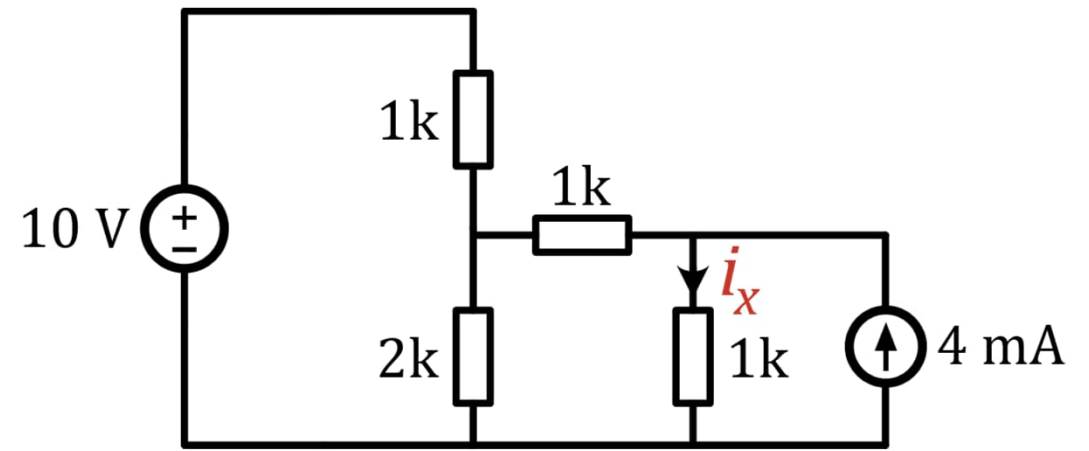Example of Superposition

- Find the value of i_x .
 - Summing them up:

$$i_x = i_{x_{10V}} + i_{x_{4m}} = 5 \text{ mA}$$




Thevenin's Theorem

- Any linear circuit can be modeled as **a voltage source** (V_{Th}) in series with **a resistor** (R_{Th}).
 - Simplifies circuit analysis.
 - Useful in time-constant calculations and circuit with only one nonlinear component (like a diode).




Leon Charles Thévenin
(1857-1926)

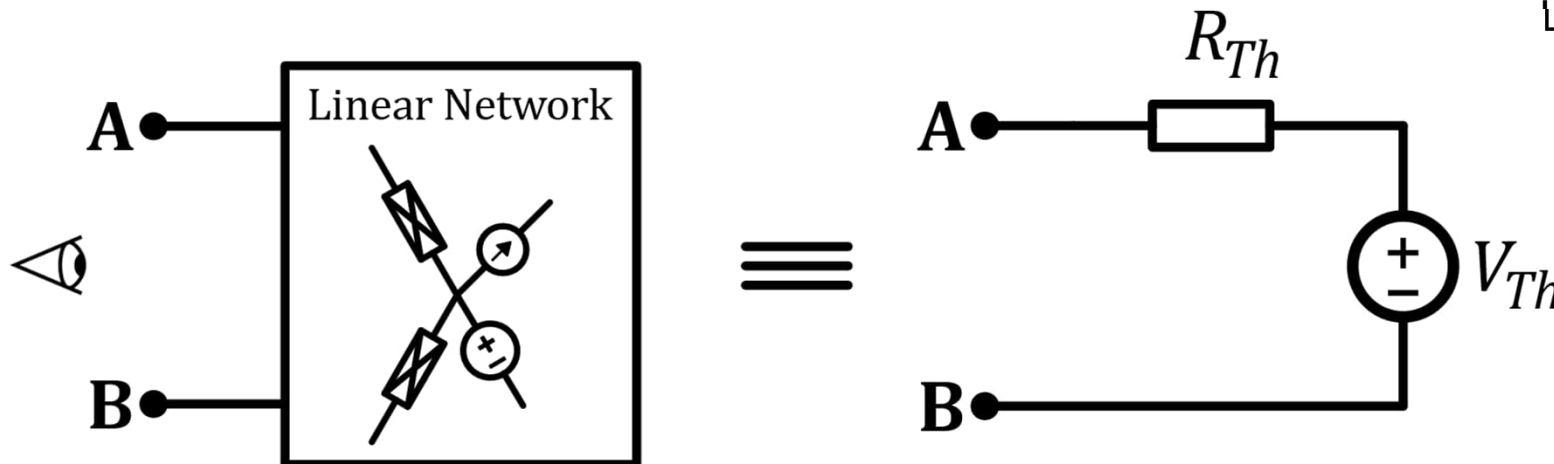

How to determine V_{Th} and R_{Th} ?

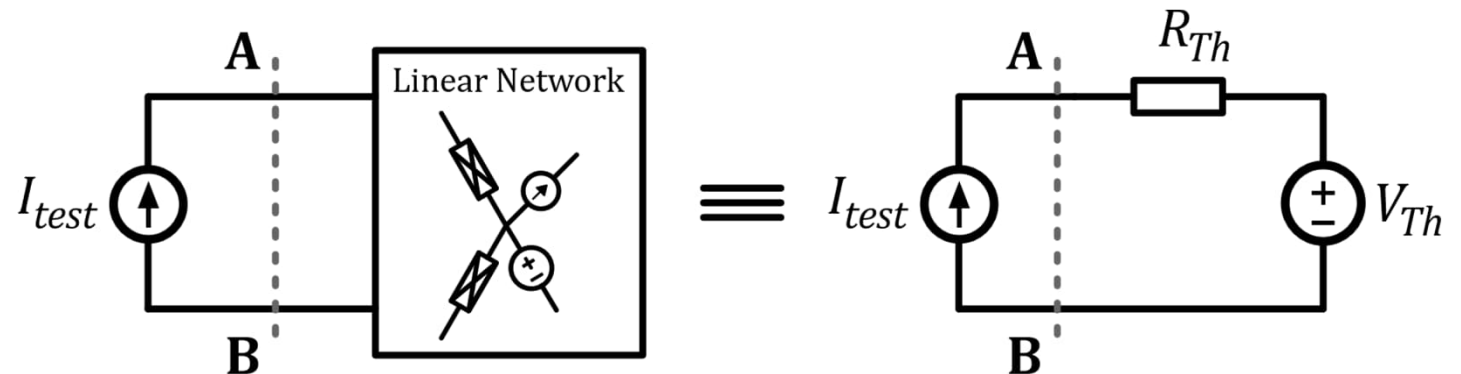- When applying a **test current**, the response of the model must match the network's response.



$$V_{AB} = R_{Th}I_{test} + V_{Th}$$

- When $I_{test} = 0$, meaning open-circuit:

$$V_{AB} = V_{Th} \Rightarrow \boxed{V_{Th} = V_{oc}}$$

- When all independent sources are off:

$$V_{AB} = R_{Th}I_{test} \Rightarrow \boxed{R_{Th} = \frac{V_{AB}}{I_{test}}}$$





Example of Thevenin's Theorem

- Draw an equivalent circuit seen between A and B.
 - Open circuit voltage: (from KVL in the loops)

$$\begin{cases} v_x = -20i_y \times 25 = -500i_y \\ 2000i_y + 3v_x - 5 = 0 \end{cases}$$

$$i_y = 10 \text{ mA}$$



$$V_{OC} = v_x = -5 \text{ V}$$

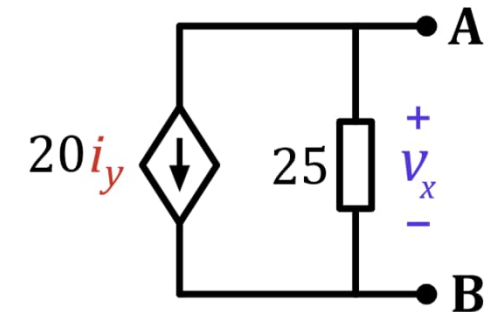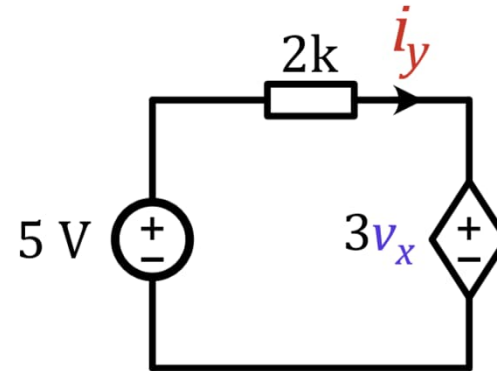

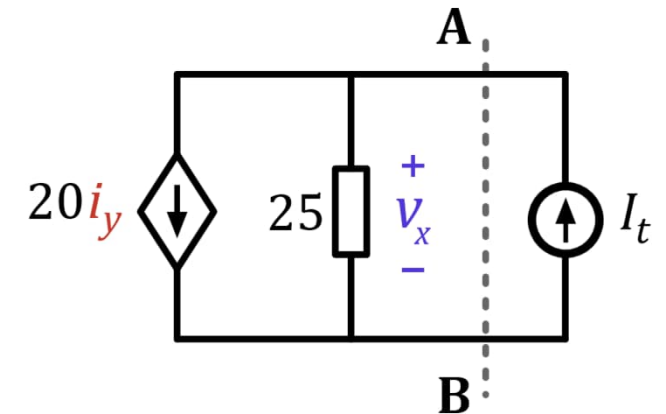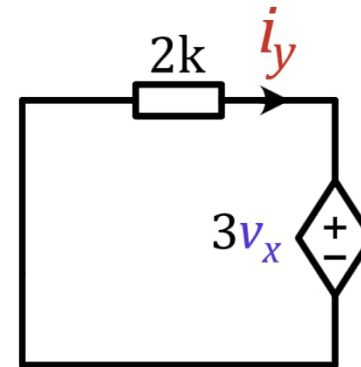Example of Thevenin's Theorem

- Draw an equivalent circuit seen between A and B.
 - Equivalent Resistance: (5 V source off)

$$\begin{cases} 20i_y + \frac{v_x}{25} = I_t \\ 2000i_y + 3v_x = 0 \end{cases}$$




$$v_{AB} = v_x = 100I_t$$

$$R_{Th} = \frac{V_{AB}}{I_{test}} = 100 \Omega$$



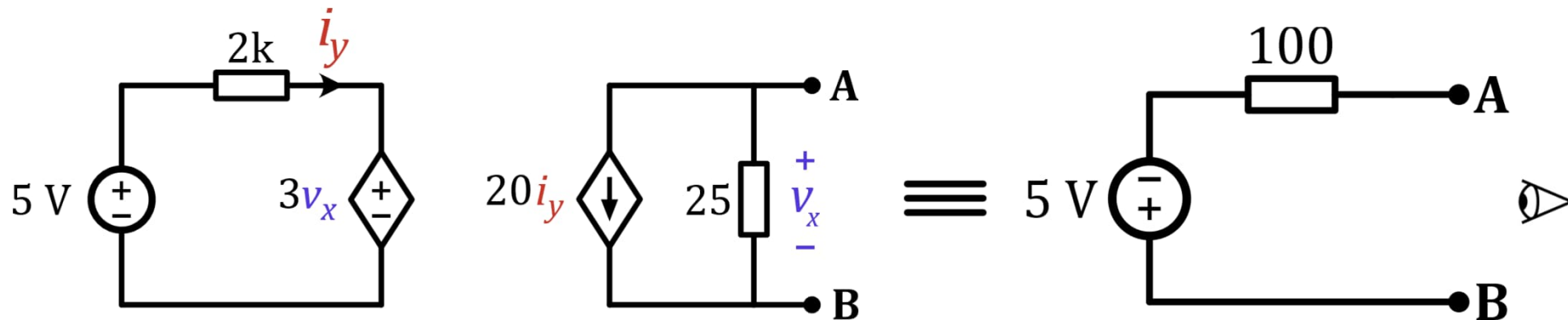Example of Thevenin's Theorem


- Draw an equivalent circuit seen between A and B.



Norton's Equivalent Circuit

- The same concept, but this time we model a linear network with **a current source** (I_N) **in parallel with a resistor** (R_{Th}).

$$I_N = \frac{V_{Th}}{R_{Th}}$$

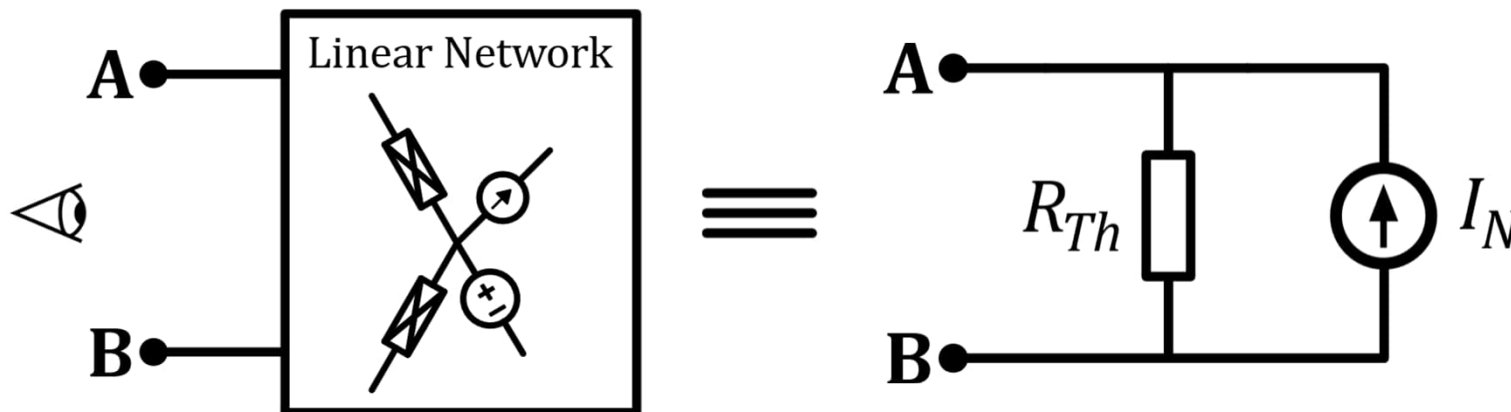

Edward Lawry Norton
(1898-1983)




Nodal Analysis

- Systematic approach to derive a system of equations for any circuit.
- Powerful tool for algorithmic simulators.
- Only relies on KCL!



Nodal Analysis, step by step

- Find the values of V_1 , V_2 and V_3 .

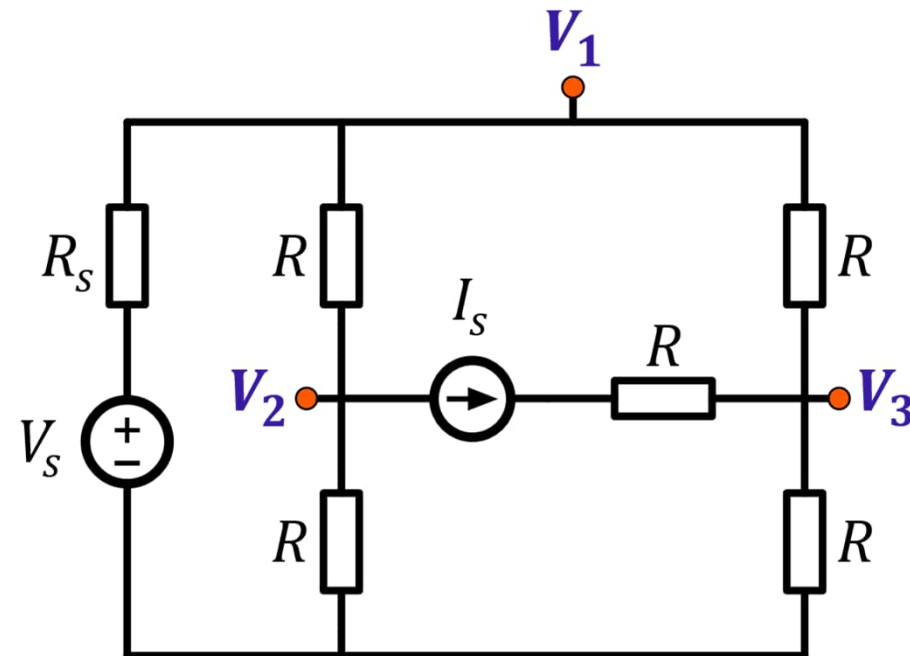

Nodal Analysis, step by step

1- Simplify your circuit.

- Remove anything in **series with current sources** or in **parallel with voltage sources**.
- Turn all voltage source into their **Norton equivalent**.
- Series/parallel combinations
- Short-circuits → remove excess wires.


2- Determine the Ground (GND).

- Node with maximum connected branches




Nodal Analysis, step by step

- Remove R in series with I_s .

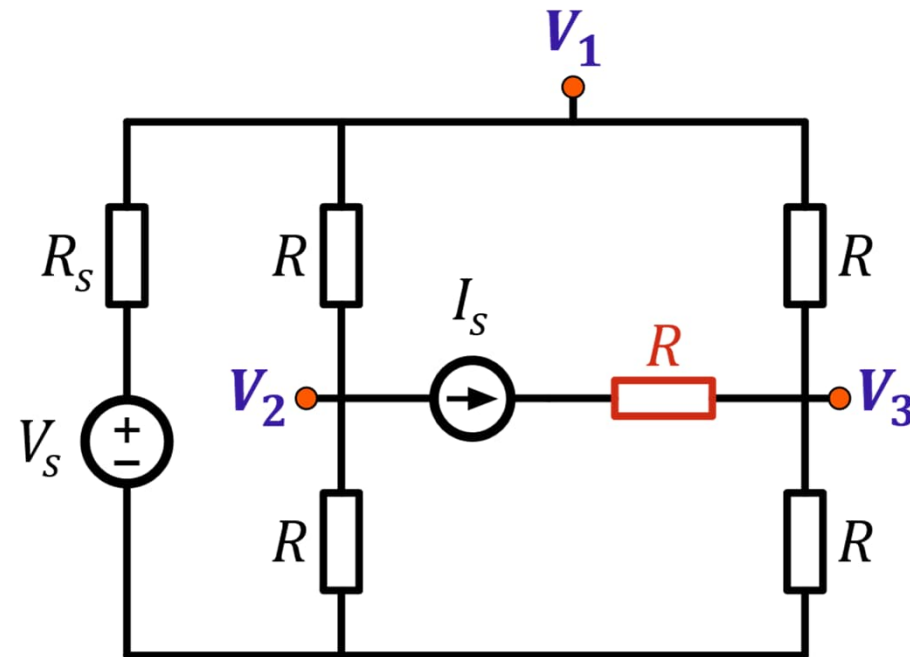


Nodal Analysis, step by step

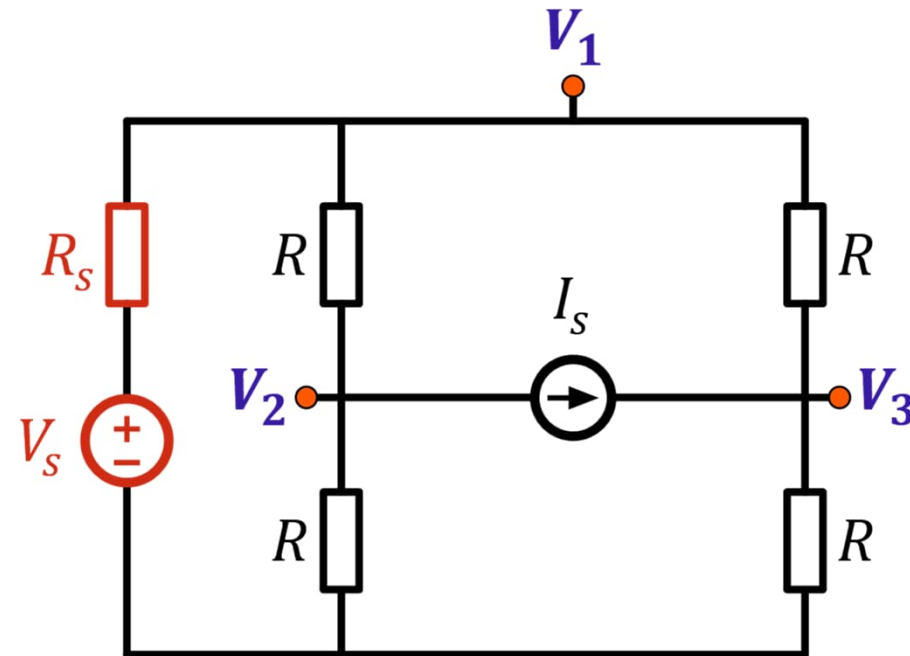- Remove R in series with I_s .
- Norton equivalent of V_s



Nodal Analysis, step by step

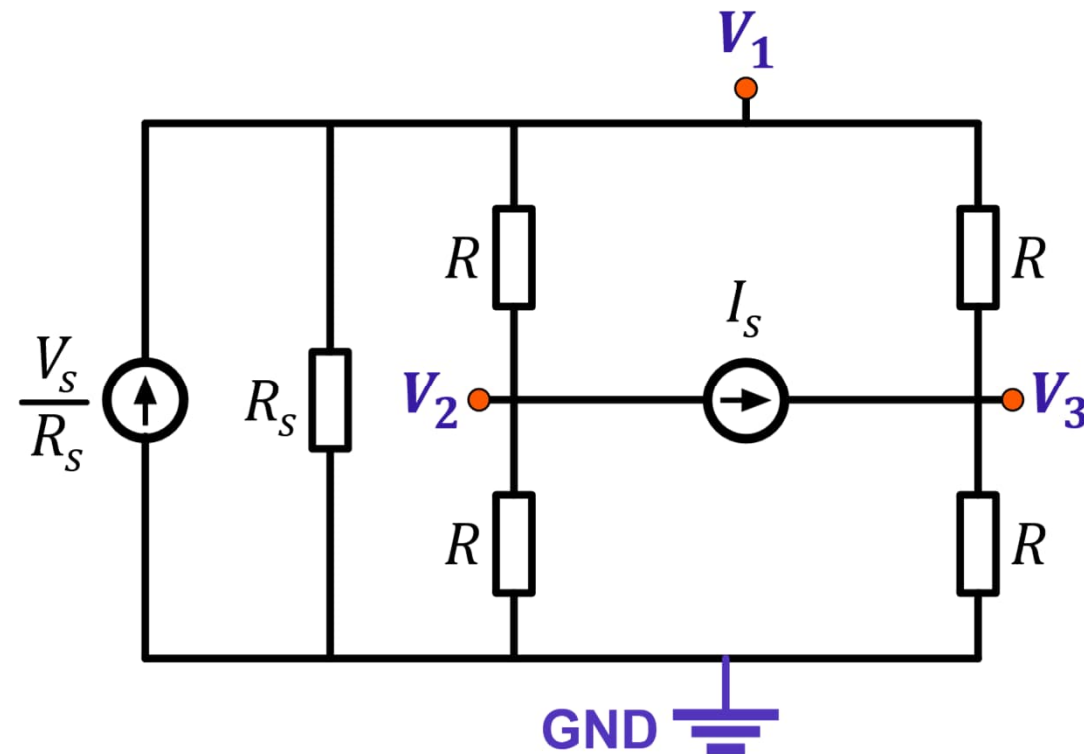- Remove R in series with I_s .
- Norton equivalent of V_s .
- Ground node



Nodal Analysis, step by step

3- Write a system of equation in matrix form $GV = I$

- In a circuit with N nodes, the number of equations and **independent voltages equals** $N_t = N - 1$. (In our example $N = 4$, meaning 3 independent voltages)
- Vector of unknown variables (node voltages):
 - Its size: $N_t \times 1$

$$V = \begin{pmatrix} V_1 \\ V_2 \\ \vdots \\ V_{N_t} \end{pmatrix}$$



Nodal Analysis, step by step

3- Write a system of equation in matrix format $\mathbf{GV} = \mathbf{I}$


- Coefficient matrix (conductance matrix, \mathbf{G})

KCL@ n_1 :

$$\frac{V_1}{R_s} + \frac{V_1 - V_2}{R} + \frac{V_1 - V_3}{R} = 0$$

$$G = \frac{1}{R}, G_s = \frac{1}{R_s}$$

$$(G_s + 2G)V_1 - GV_2 - GV_3 = 0$$

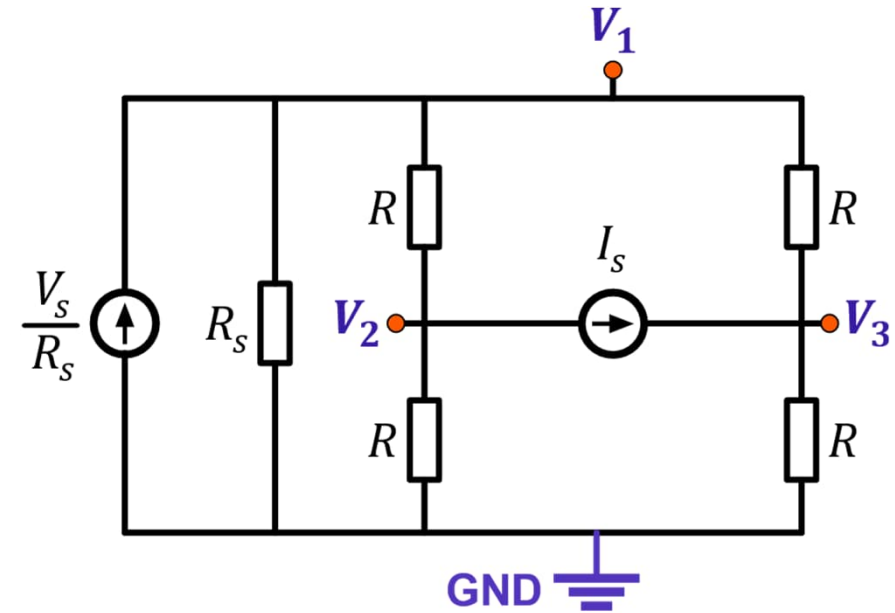

Nodal Analysis, step by step


3- Write a system of equation in matrix format $\mathbf{GV} = \mathbf{I}$

- Coefficient matrix (conductance matrix, \mathbf{G})

KCL@ n_1 :

$$(G_s + 2G)V_1 - GV_2 - GV_3 = 0$$
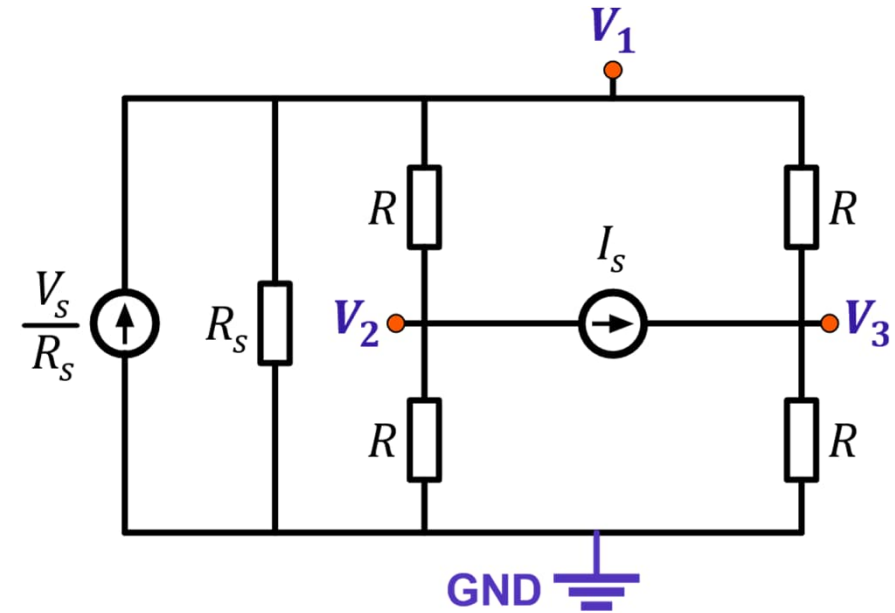
$$\begin{pmatrix} G_s + 2G & -G & -G \\ ? & ? & ? \\ ? & ? & ? \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 0 \\ ? \\ ? \end{pmatrix}$$



Nodal Analysis, step by step

3- Write a system of equation in matrix format $\mathbf{G}\mathbf{V} = \mathbf{I}$

- Coefficient matrix (conductance matrix, \mathbf{G})

$$\begin{pmatrix} G_s + 2G & -G & -G \\ ? & ? & ? \\ ? & ? & ? \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} 0 \\ ? \\ ? \end{pmatrix}$$

$$\mathbf{G} = \begin{pmatrix} G_{11} & G_{12} & G_{13} \\ G_{21} & G_{22} & G_{23} \\ G_{31} & G_{32} & G_{33} \end{pmatrix}$$

$$G_{kk} = \sum (\text{all connected conductances to node } \mathbf{n}_k)$$

$$G_{jk} (j \neq k) = - \sum (\text{all connected conductances between nodes } \mathbf{n}_j \text{ and } \mathbf{n}_k)$$




Nodal Analysis, step by step

3- Write a system of equation in matrix format $\mathbf{GV} = \mathbf{I}$

$$\begin{pmatrix} G_s + 2G & ? & ? \\ ? & 2G & ? \\ ? & ? & 2G \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} ? \\ ? \\ ? \end{pmatrix}$$
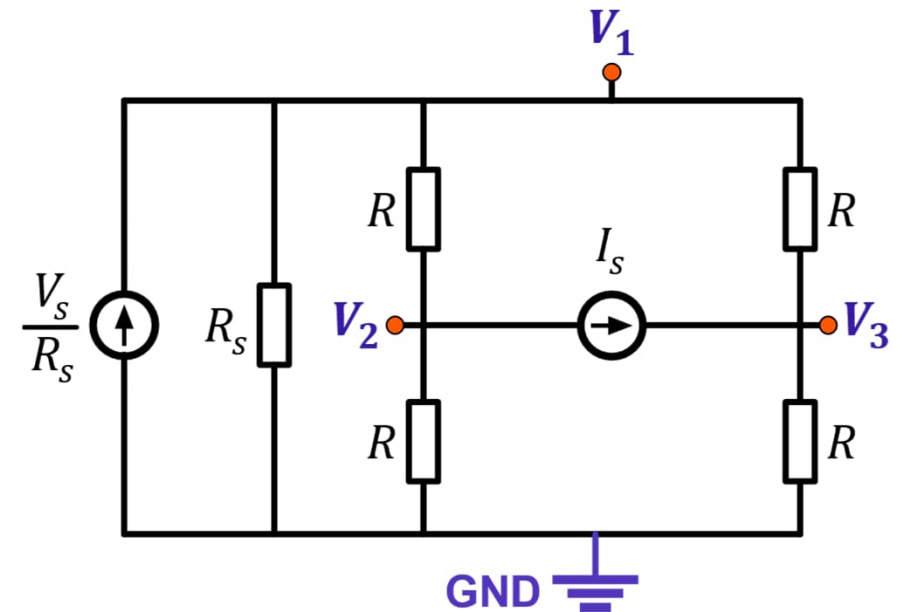
$$G_{kk} = \sum (\text{all connected conductances to node } \mathbf{n}_k)$$




Nodal Analysis, step by step

3- Write a system of equation in matrix format $\mathbf{GV} = \mathbf{I}$

$$\begin{pmatrix} G_s + 2G & -G & -G \\ -G & 2G & 0 \\ -G & 0 & 2G \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} ? \\ ? \\ ? \end{pmatrix}$$
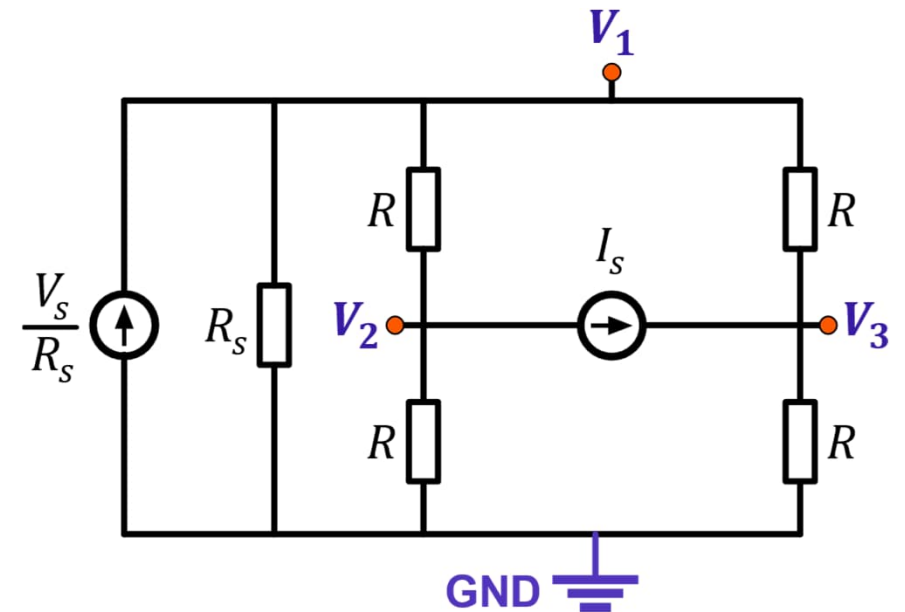
$$G_{jk} \ (j \neq k) = - \sum (\text{all connected conductances between nodes } \mathbf{n}_j \text{ and } \mathbf{n}_k)$$



Nodal Analysis, step by step

3- Write a system of equation in matrix format

$$GV = \mathbf{I}$$

- Constants matrix (current matrix, \mathbf{I})

$$I_k = \sum (\text{all connected current sources entering node } n_k)$$

$$\mathbf{I} = \begin{pmatrix} I_1 \\ I_2 \\ \vdots \\ I_{N_t} \end{pmatrix}$$




Nodal Analysis, step by step

3- Write a system of equation in matrix format $GV = I$

- Constants matrix (current matrix, I)
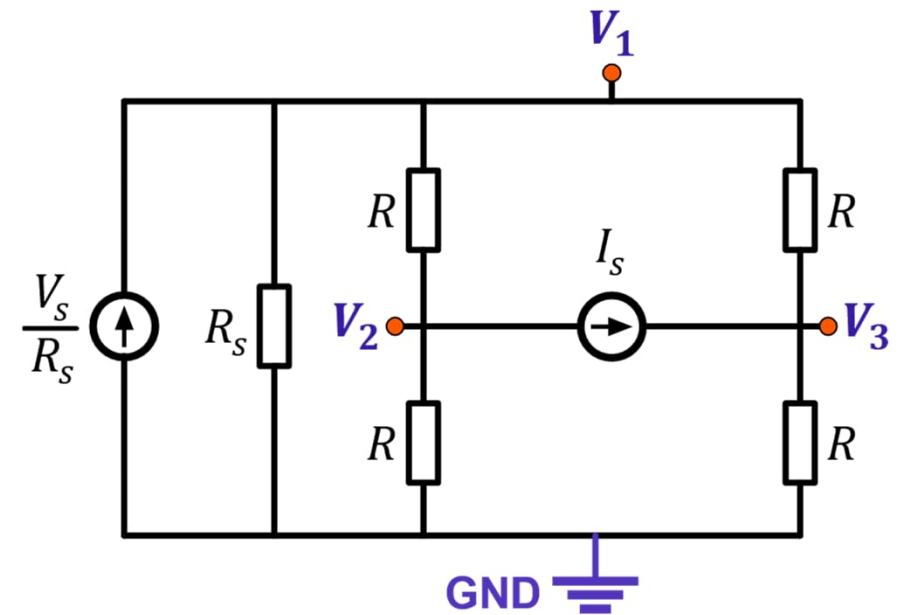
$$\begin{pmatrix} G_s + 2G & -G & -G \\ -G & 2G & 0 \\ -G & 0 & 2G \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} \frac{V_s}{R_s} \\ -I_s \\ I_s \end{pmatrix}$$



Nodal Analysis, step by step

4- Solve the linear system as you wish!

- Multiplication by the inverse of \mathbf{G}

$$\mathbf{V} = \mathbf{G}^{-1} \mathbf{I}$$

- Cramer's rule

$$V_k = \frac{\det(\mathbf{G}_k)}{\det(\mathbf{G})}$$

\mathbf{G}_k : The matrix formed by replacing the k -th column of \mathbf{G} by \mathbf{I}



Nodal Analysis, step by step


4- Solve the linear system as you wish!

$$\begin{pmatrix} G_s + 2G & -G & -G \\ -G & 2G & 0 \\ -G & 0 & 2G \end{pmatrix} \cdot \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} = \begin{pmatrix} \frac{V_s}{R_s} \\ -I_s \\ I_s \end{pmatrix}$$

$$V_1 = \frac{R}{R + R_s} V_s$$

$$V_2 = \frac{1}{2} \left(\frac{R}{R + R_s} V_s - R I_s \right)$$
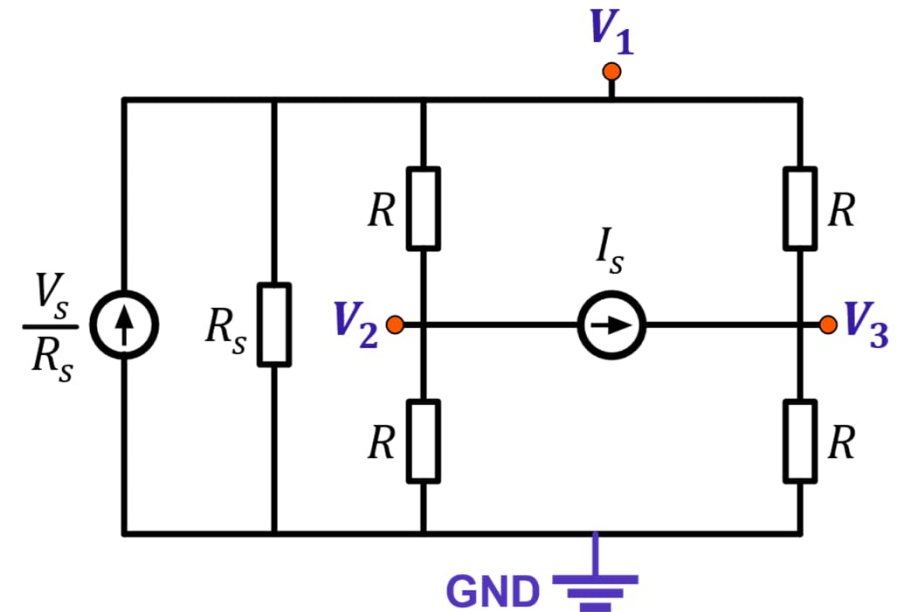
$$V_3 = \frac{1}{2} \left(\frac{R}{R + R_s} V_s + R I_s \right)$$



Pause and Ponder 5

- Solve the previous question using the principle of superposition.

