

Elektronik

Basic Components and Circuit Theory 4

EITA10

Iman Ghotbi

Mars 2025



Today we learn

- Initial and final values
- Step Response of RC circuits
- Maximum operating frequency
- Limitations of circuit theory



First-order RC Circuits

- **Frequency-domain analysis**


- Simple voltage division if we consider impedances:

$$V_C(s) = \frac{Z_C}{Z_C + Z_R} V_S(s) = \frac{\frac{1}{Cs}}{\frac{1}{Cs} + R} V_S(s) = \frac{1}{1 + RCs} V_S(s)$$

- Impulse response ($V_S(s) = 1$):

$$H(s) = \frac{1}{1 + \tau s}$$

The same result

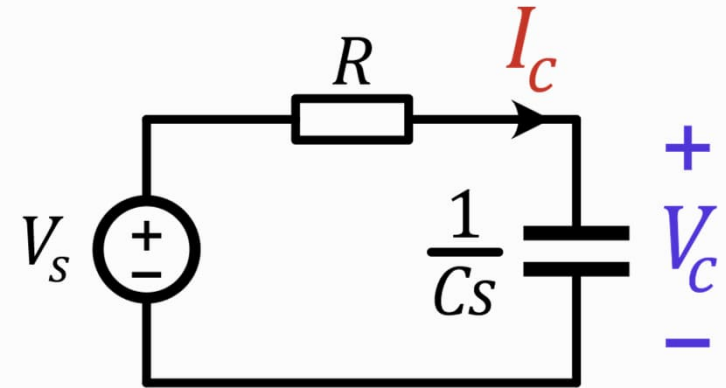


First-order RC Circuits

- Step Response

$$v_c(t) = \left(1 - \exp\left(-\frac{t}{\tau}\right)\right) u(t)$$

Initial value: $v_c(0) = 0$

Final value: $v_c(\infty) = 1$

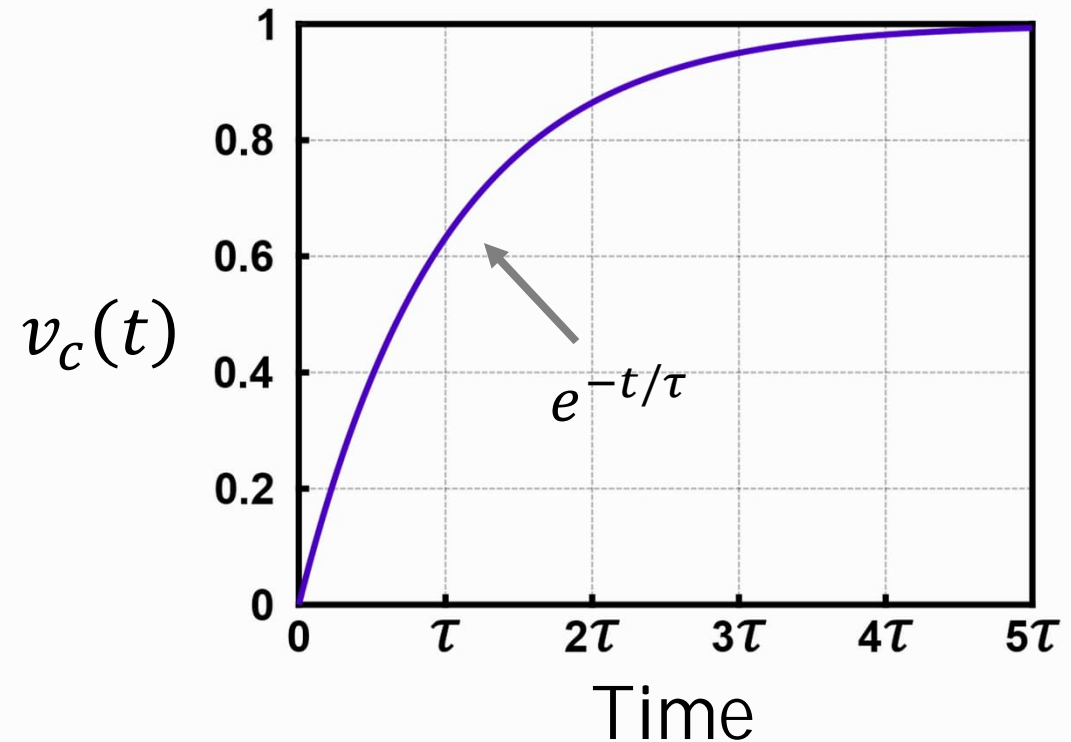

First-order RC Circuits


- Current's Step Response

$$i_c(t) = c \frac{dv_c}{dt}$$

$$i_c(t) = \frac{1}{R} \exp\left(-\frac{t}{\tau}\right) u(t)$$

Initial value: $i_c(0) = \frac{1}{R}$

Final value: $i_c(\infty) = 0$

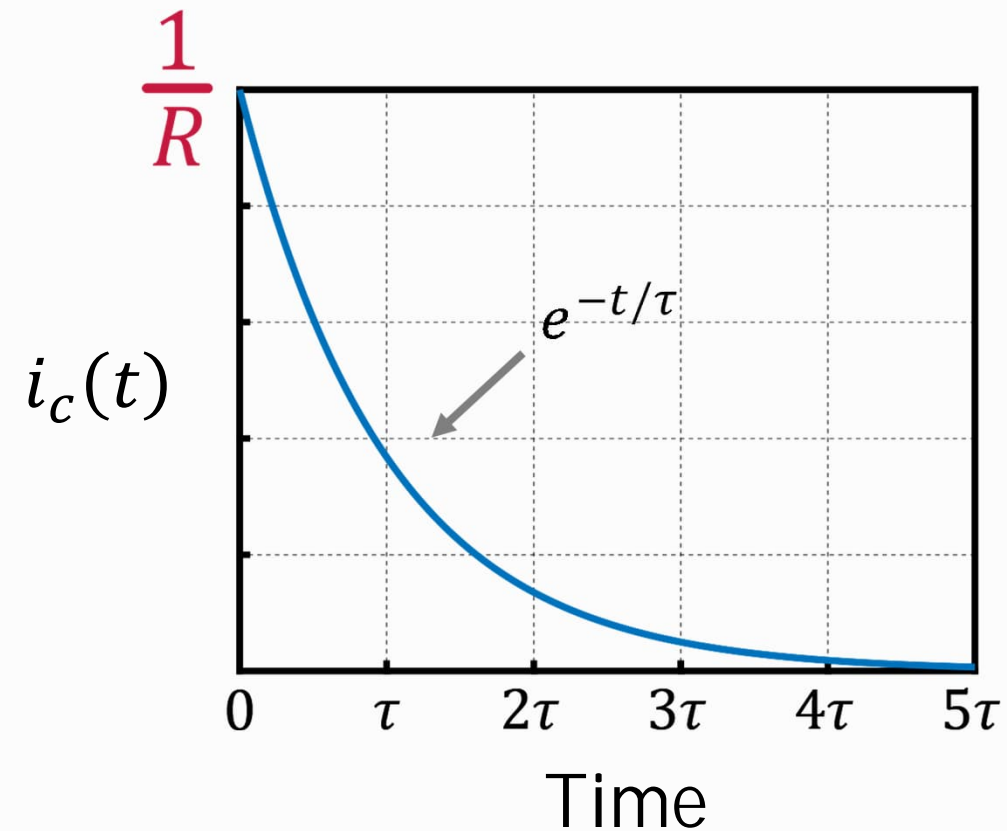

Capacitor's Model when $t \rightarrow 0^+$

- Capacitor's **voltage** must be **continuous**.

$$i_c(t) = C \frac{dv_c}{dt} \Rightarrow \text{if } v_c = \Delta V u(t): i_c(t) \rightarrow \infty$$



Physically
Impossible

$$\Rightarrow v_c(0^+) = v_c(0^-) = V_0$$

- What about current?

$$i_c(0^+) = \frac{V_s - V_0}{R}$$

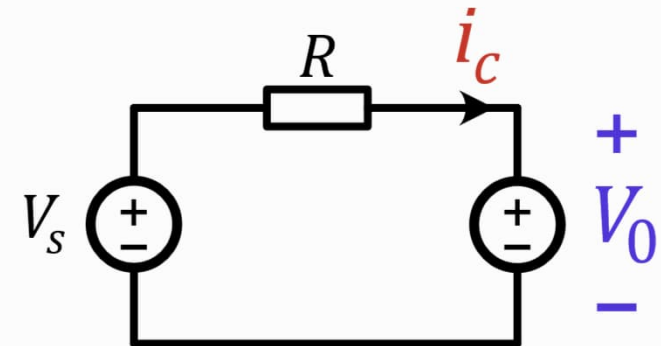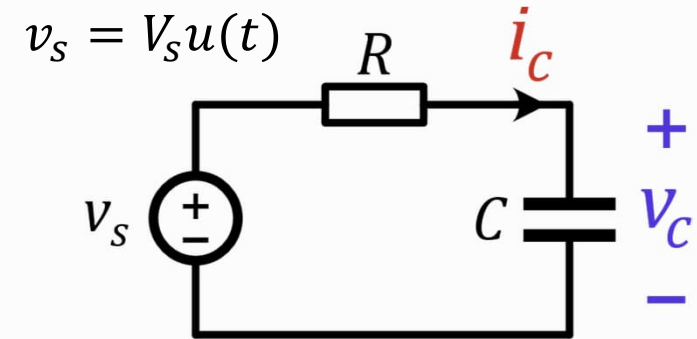Capacitor acts like a **voltage source**, showing **zero impedance**





Capacitor's Model when $t \rightarrow \infty$

- After a sufficiently long time ($t > 5\tau$), the voltage across a capacitor reaches a stable state.
- This duration is called **settling time**.
- **No current** flows into the circuit anymore.


$$\left. \frac{dv_c}{dt} \right|_{t \rightarrow \infty} = 0 \Rightarrow i_c(\infty) = 0, v_c(\infty) = V_s$$

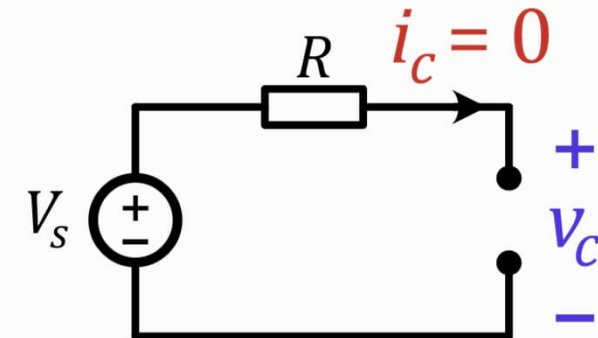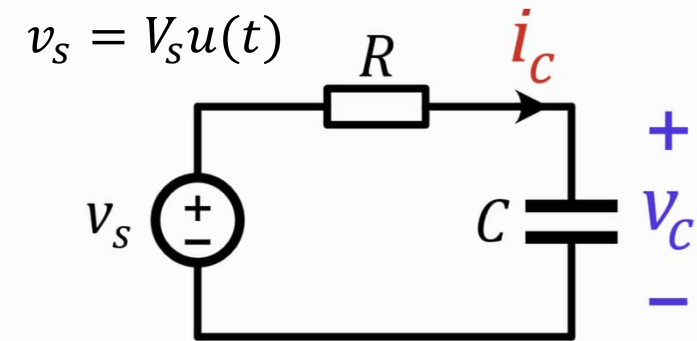Capacitor acts like **an open-circuit**,
showing **infinite impedance**



Step Response of RC Circuits

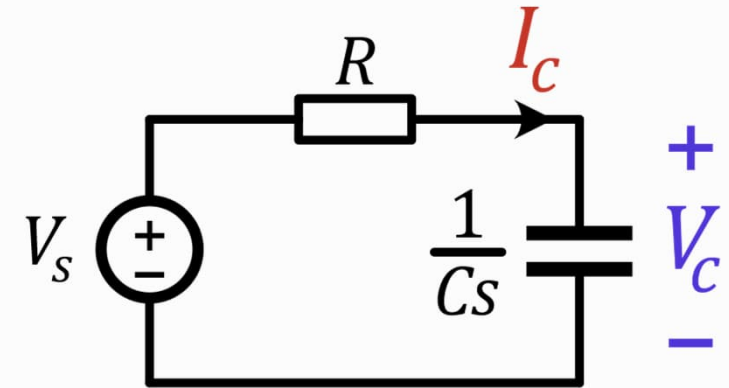- Only three parameters need to be calculated:
 - Time constant ($\tau = RC$)
 - Initial value ($x(0^+)$)
 - Final value ($x(\infty)$)




$$x(t) = x(\infty) + (x(0^+) - x(\infty)) \exp\left(-\frac{t}{\tau}\right)$$

$x(t)$ can be any voltage or current




Example 1

- Find $i_R(t)$.
 - IC: $v_C(0^-) = 0$

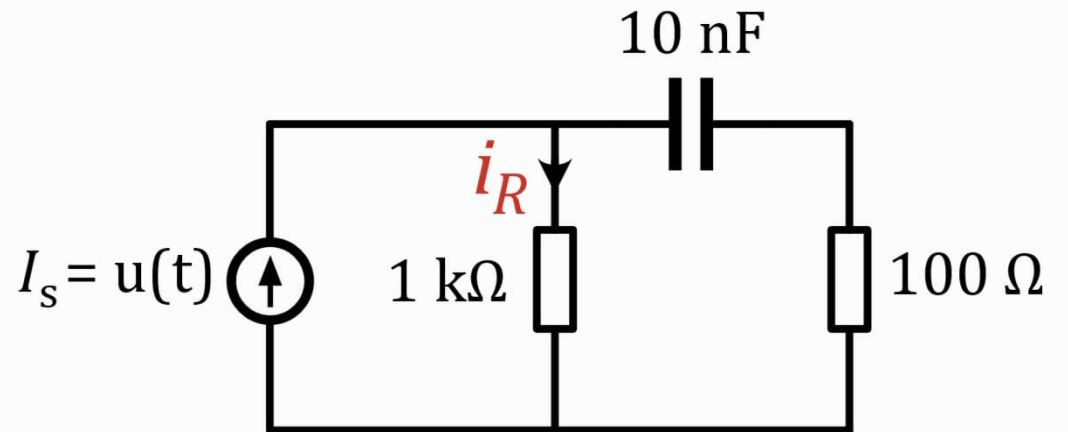

Example 1 – step 1: calculating τ

- We employ **Thevenin's theorem** to find the equivalent resistance seen from the terminals A and B.

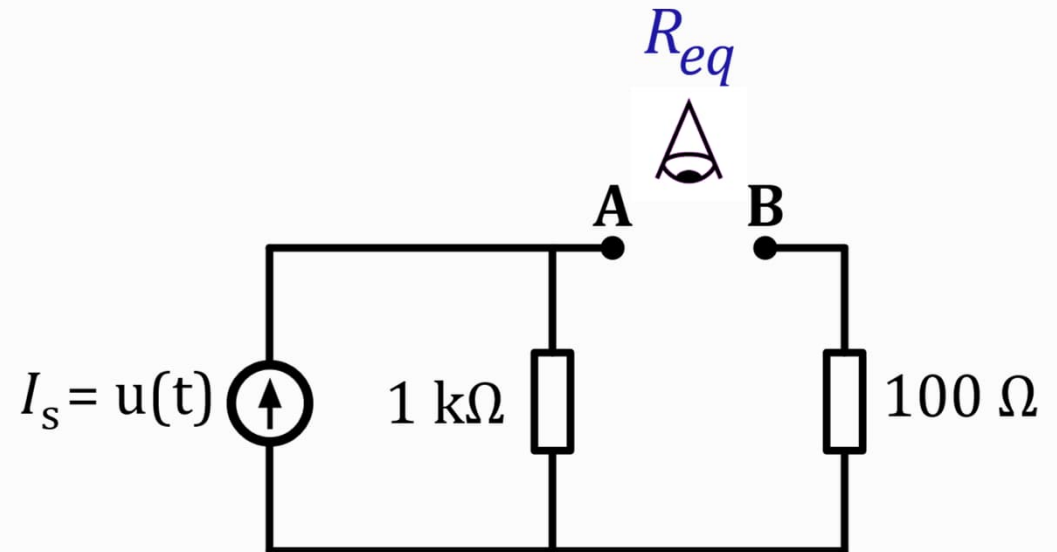


Example 1 – step 1: calculating τ

- We employ **Thevenin's theorem** to find the equivalent resistance seen from the terminals A and B.
- Turn off independent sources.
- Series connection of two resistors:

$$R_{Th} = 1 \text{ k}\Omega + 100 \text{ }\Omega = 1.1 \text{ k}\Omega$$
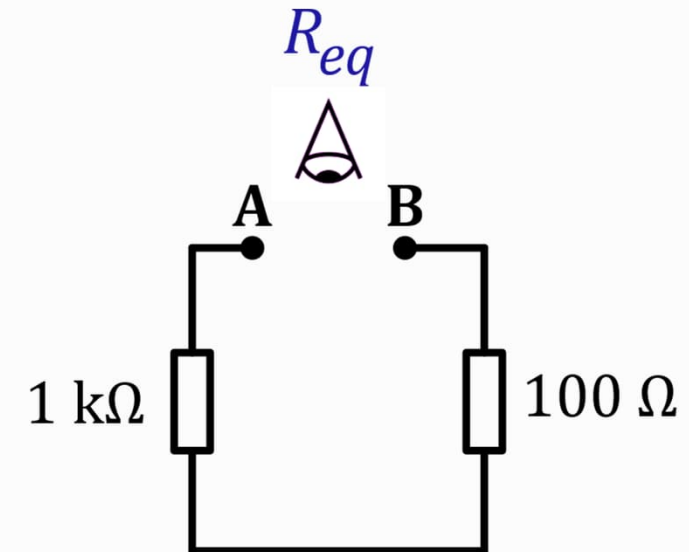
$$\Rightarrow \tau = R_{Th}C = 1.1 \text{ k}\Omega \times 10 \text{ nF} = 11 \text{ }\mu\text{s}$$




$$\tau = 11 \text{ }\mu\text{s}$$



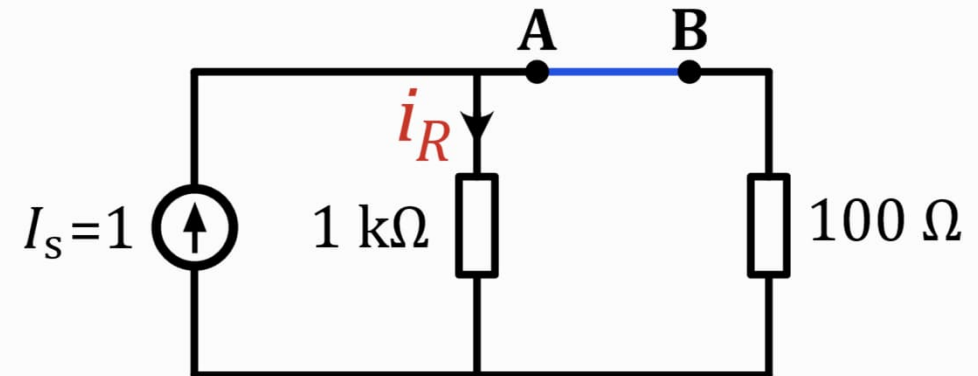Example 1 – step 2: calculating $i_R(0^+)$

- We model the capacitor with a **voltage source** whose value is $v_c(0^-)$.
- In this case, it is turned into short-circuit ($v_c(0^-) = 0$)
- Current division



$$i_R(0^+) = \frac{100}{100 + 1\text{k}} I_s$$



$$i_R(0^+) = \frac{1}{11} \text{ A}$$




Example 1 – step 3: calculating $i_R(\infty)$

- We model the capacitor as an **open-circuit**.
- No current flows into $100\ \Omega$ resistor.

$$i_R(\infty) = I_S = 1$$



$$i_R(\infty) = 1\text{ A}$$

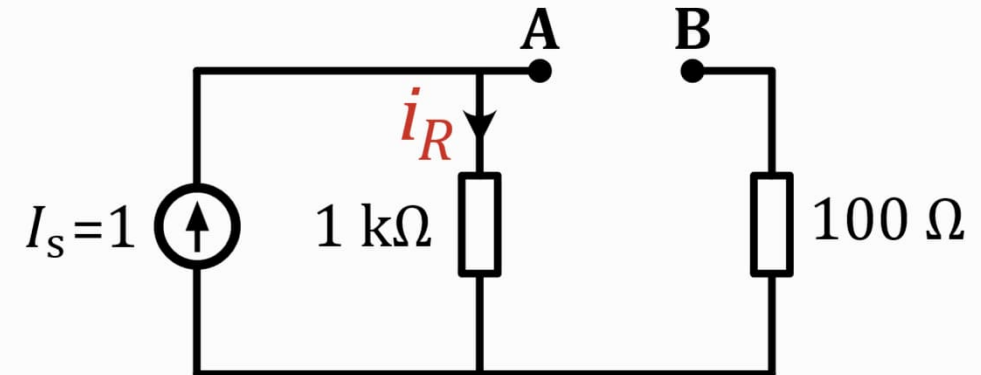

Example 1 – step 4: Conclusion



- Substituting these values in the formula:

$$i_R(t) = x(\infty) + (x(0^+) - x(\infty)) \exp\left(-\frac{t}{\tau}\right)$$

$$i_R(t) = 1 + \left(\frac{1}{11} - 1\right) \exp\left(-\frac{t}{11\mu\text{s}}\right)$$


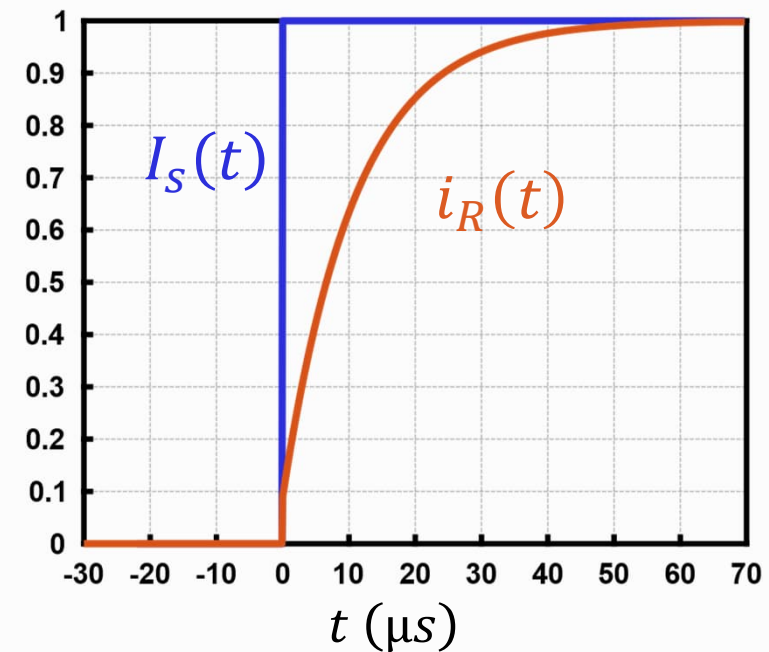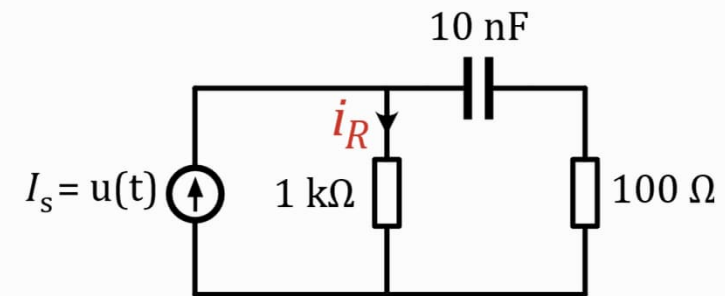
$$i_R(t) = 1 - \frac{10}{11} \exp\left(-\frac{t}{11\mu\text{s}}\right)$$



Pause and Ponder 1



- Plot the response of the circuit when the current source generates a pulse with a duration of 30 μs and an amplitude of 5 V.

$$I_s(t) = 5(u(t) - u(t - 30\mu\text{s}))$$

$$\Rightarrow i_{R,\text{new}}(t) = 5(i_{R,\text{old}}(t) - i_{R,\text{old}}(t - 30\mu\text{s}))$$


$$i_{R,\text{old}}(t) = \left(1 - \frac{10}{11} \exp\left(-\frac{t}{11\mu\text{s}}\right)\right) u(t)$$

$$i_{R,\text{old}}(t - 30\mu\text{s}) = \left(1 - \frac{10}{11} \exp\left(-\frac{t - 30\mu\text{s}}{11\mu\text{s}}\right)\right) u(t - 30\mu\text{s})$$

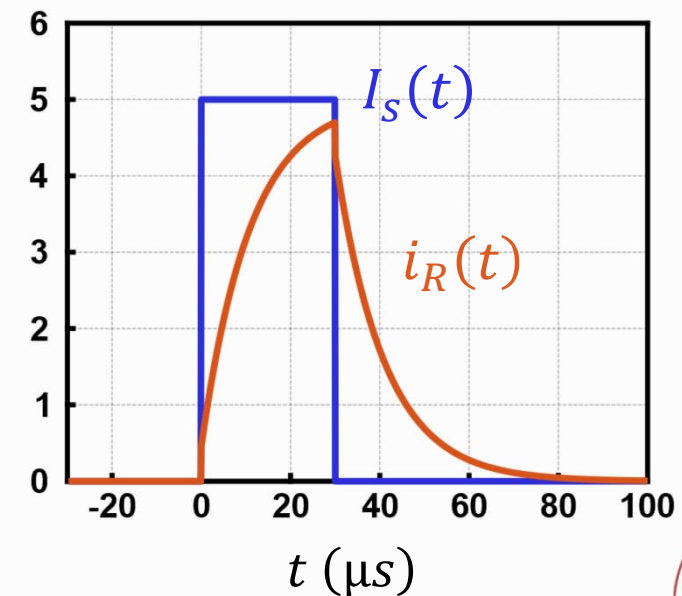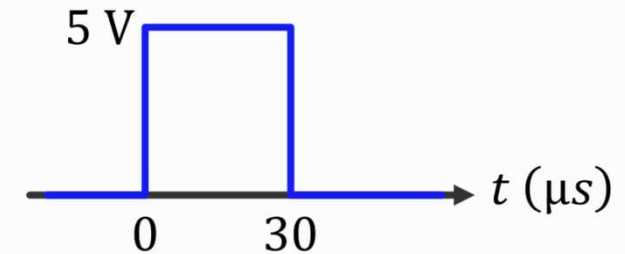

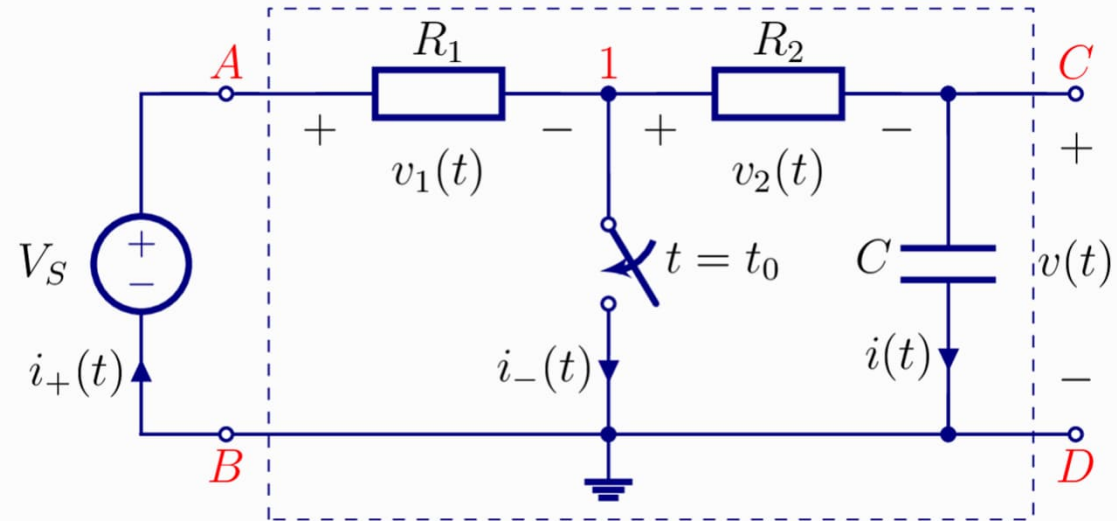Example 2

- Find $v_c(t)$.
 - C has been fully charged before $t = t_0$.
 - At $t = t_0$ we the switch is closed.
 - Source voltage: 5 V



Component	Value
R_1	50 k Ω
R_2	50 k Ω
C	1.4 nF




Example 2 – step 1: calculating τ

- When the switch is closed.


$$R_{Th} = R_2 = 50 \text{ k}\Omega$$

$$\tau_1 = R_2 C = 70 \text{ }\mu\text{s}$$

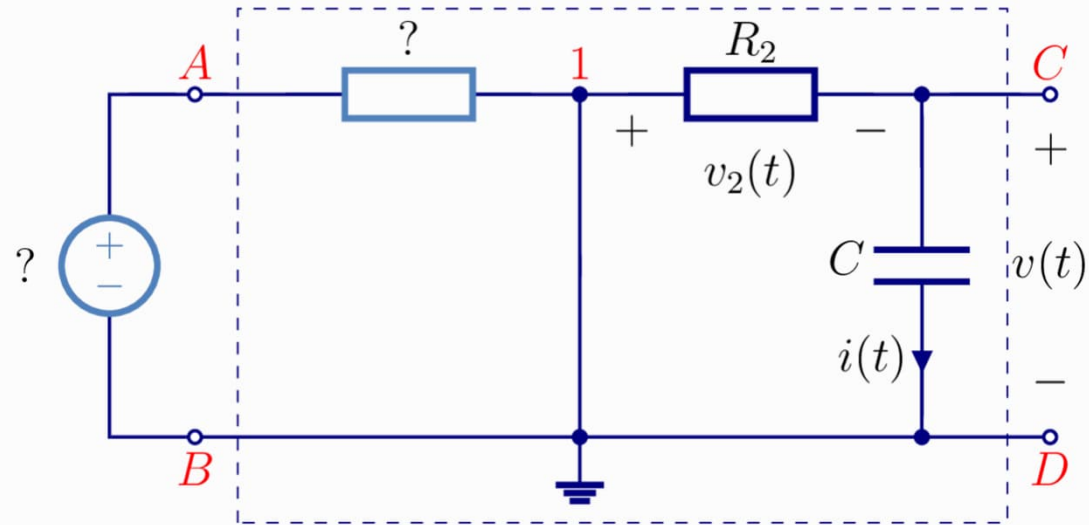

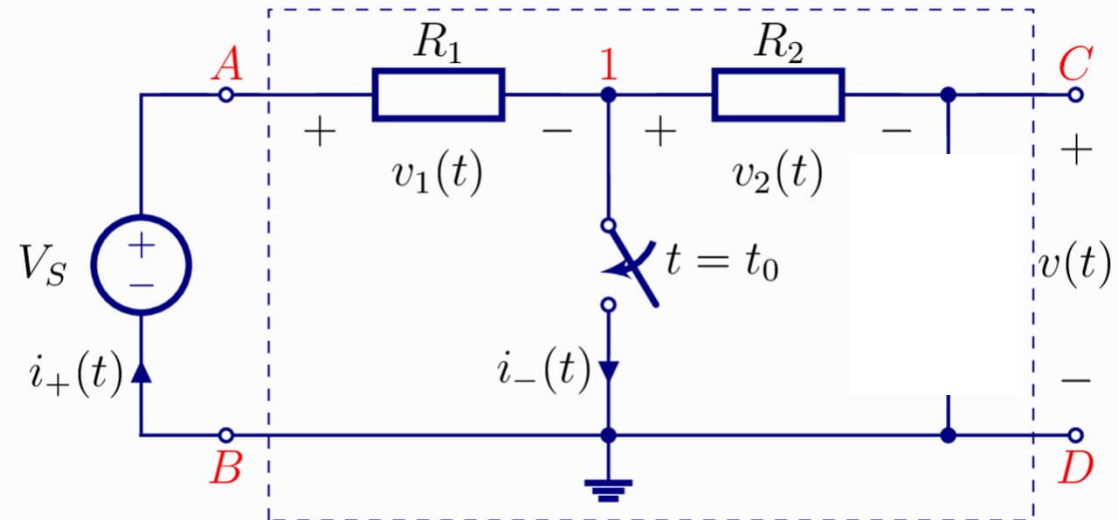Example 2 – step 2: calculating $v_c(t_0^+)$

- $v_c(t)$ must be continuous.
- First, we calculate $v_c(t_0^-)$.
- $v_c(t_0^-)$ is the final value of the previous state ($t < t_0$).
- Then: $v_c(t_0^+) = v_c(t_0^-)$.




$$v_c(t_0^-) = V_S = 5 \text{ V} \Rightarrow v_c(t_0^+) = 5 \text{ V}$$



Example 2 – step 3: calculating $v_c(\infty)$

- In the end, C will be completely discharged through R_2 .


$$v_c(\infty) = 0 \text{ V}$$

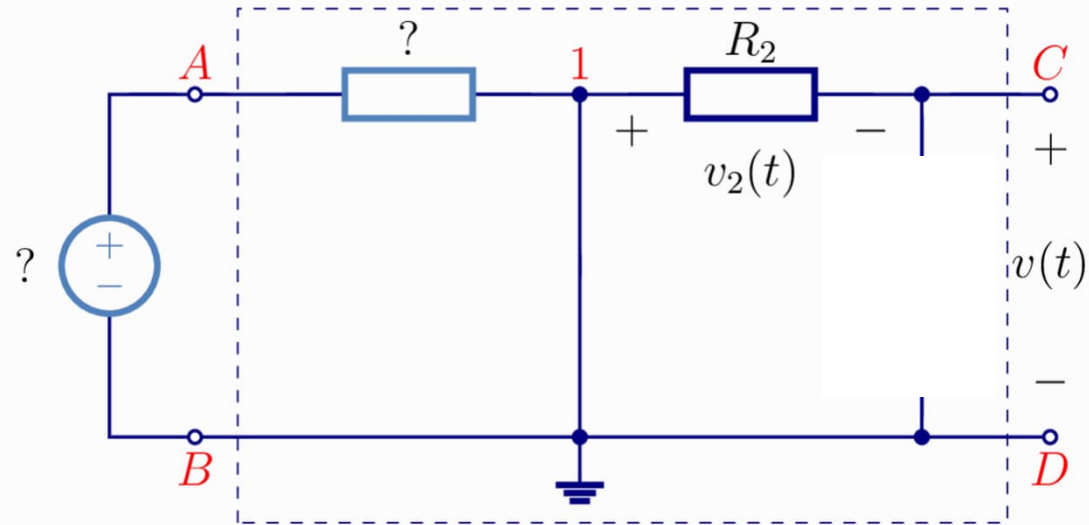

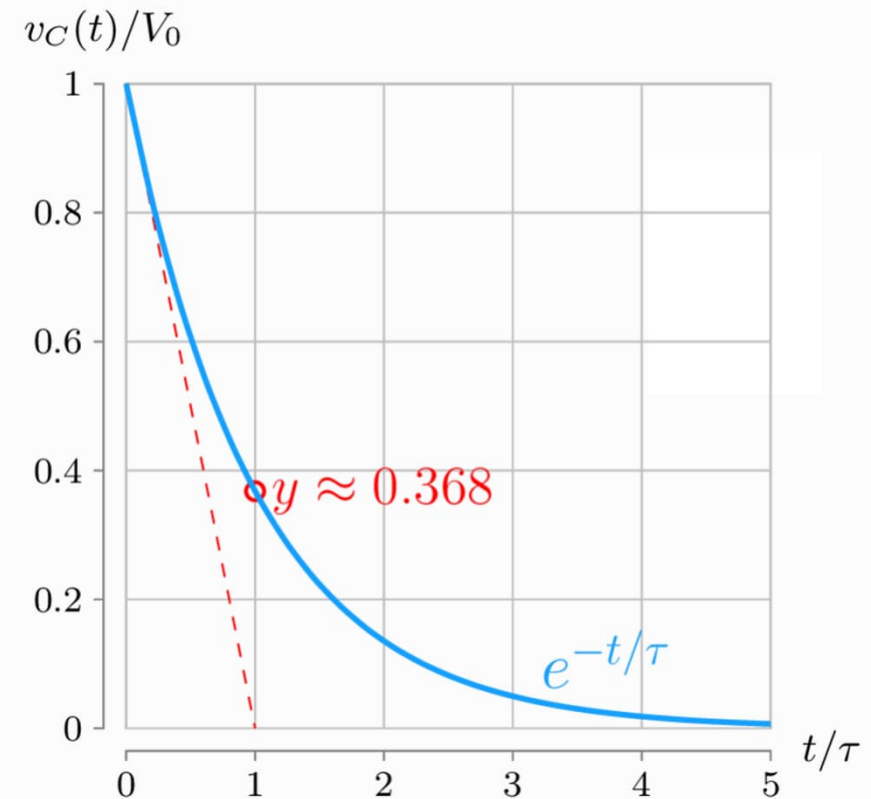Example 2 – step 4: Conclusion


$$v_c(t) = 5 \exp\left(-\frac{t - t_0}{70\mu\text{s}}\right) u(t - t_0)$$

Notice: at $t = t_0 + \tau$ the voltage decreased by **63%**.



What happens if we open the switch again?

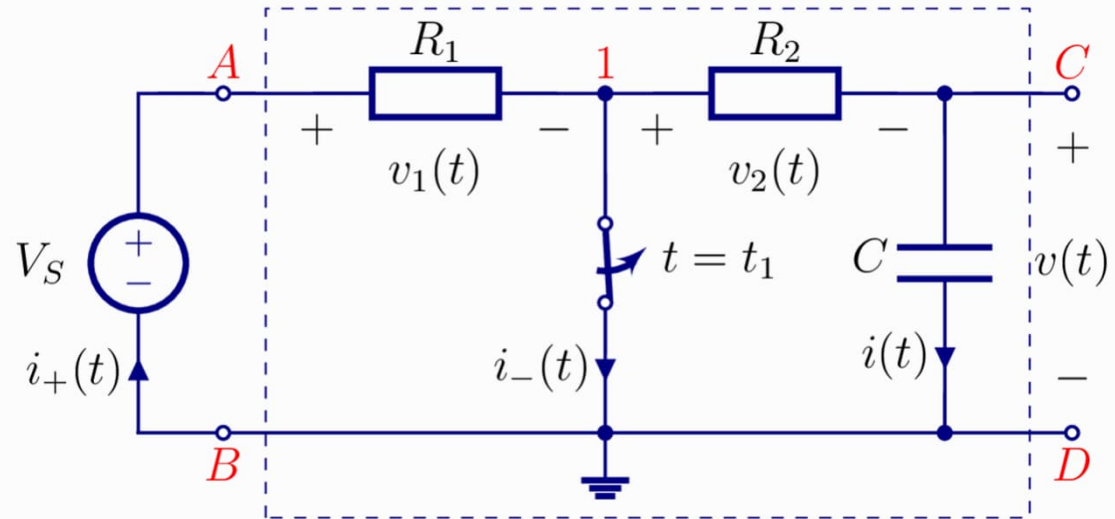- We open the switch later, at $t = t_1$.
- If $t_1 - t_0 \gg \tau_1$, we can assume that the initial value in this state equals the final value of the previous state:



$$v_c(t_1^+) = v_c(t_1^-) = 0 \text{ V}$$

- In the end, C will be charged to $V_S = 5 \text{ V}$.

$$v_c(\infty) = 5 \text{ V}$$




What happens if we open the switch again?

- What about the time constant?

$$R_{Th} = R_1 + R_2 = 100 \text{ k}\Omega$$



$$\tau_1 = R_{Th} C = 140 \text{ }\mu\text{s}$$

Charging happens slower.

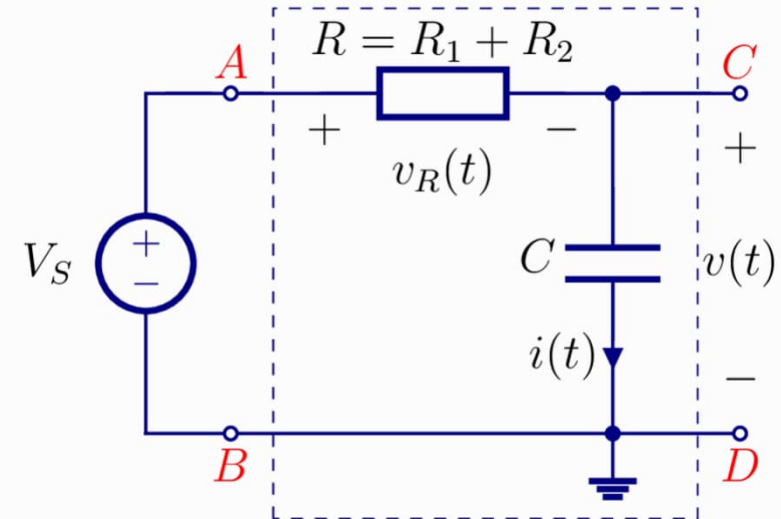


How long should we wait before switching?

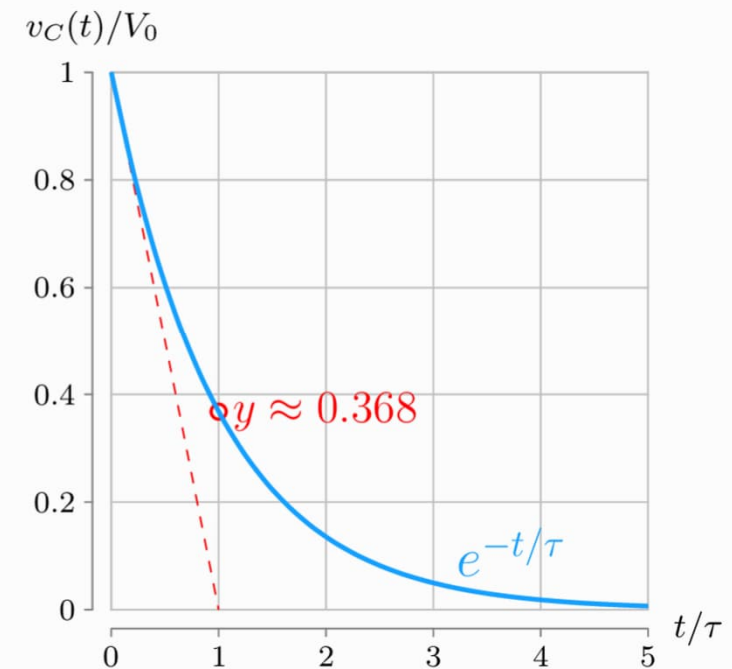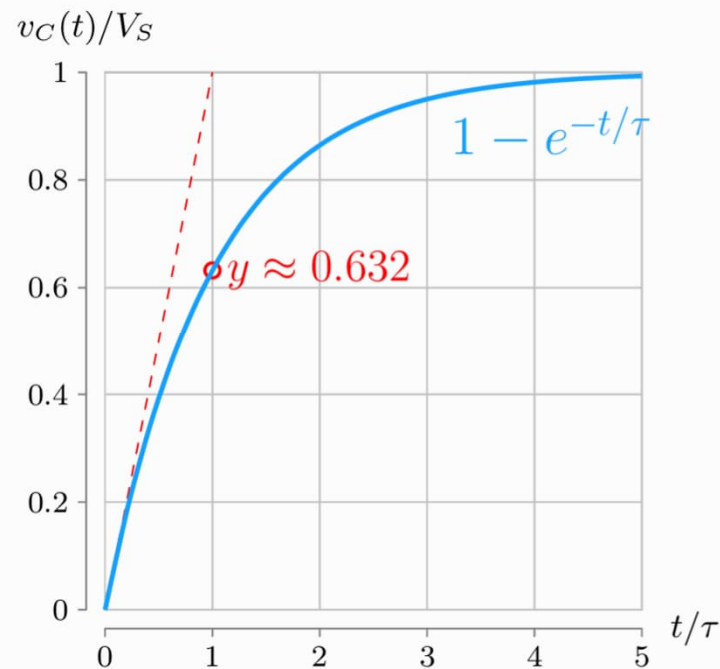- Reaches **63%** of the final value after **1τ** .
- We should wait for at least **5τ** to get to **99%** of the final value.






Maximum Operating Frequency

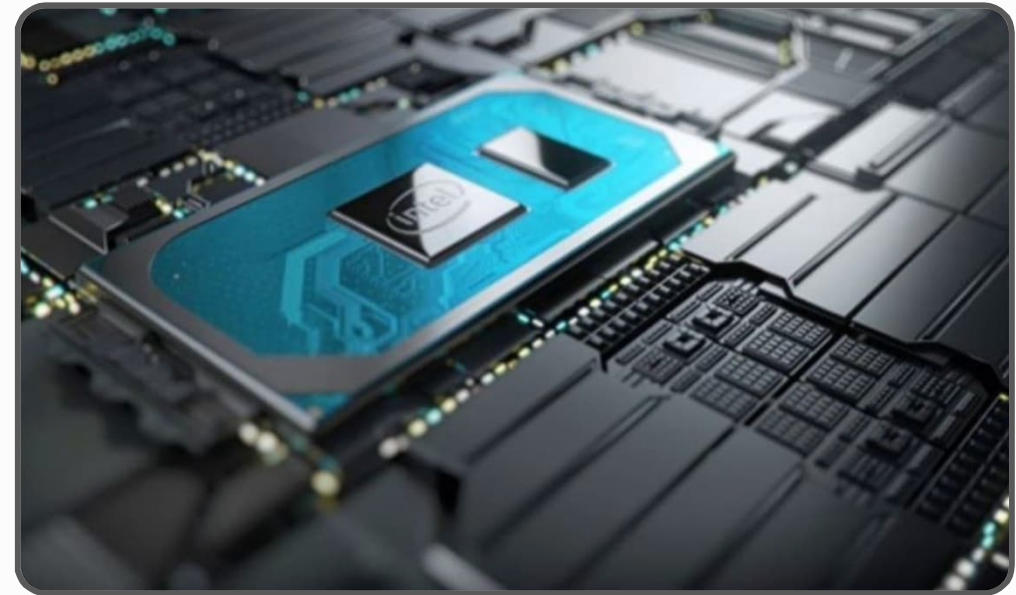- An overly simplified view!
- For MOS transistors (~ 10 nm)
- In the switched-on mode:
 - $V_{dd} \approx 3$ V, $i_d = 0.3$ mA
 - Equivalent to $R_{sw} = 10$ k Ω
 - Capacitance: $C_g \approx 10$ fF
- Time constant: $\tau \approx 100$ ps
- $f_{max} \approx 3$ GHz



Clock Generation, we'll see later

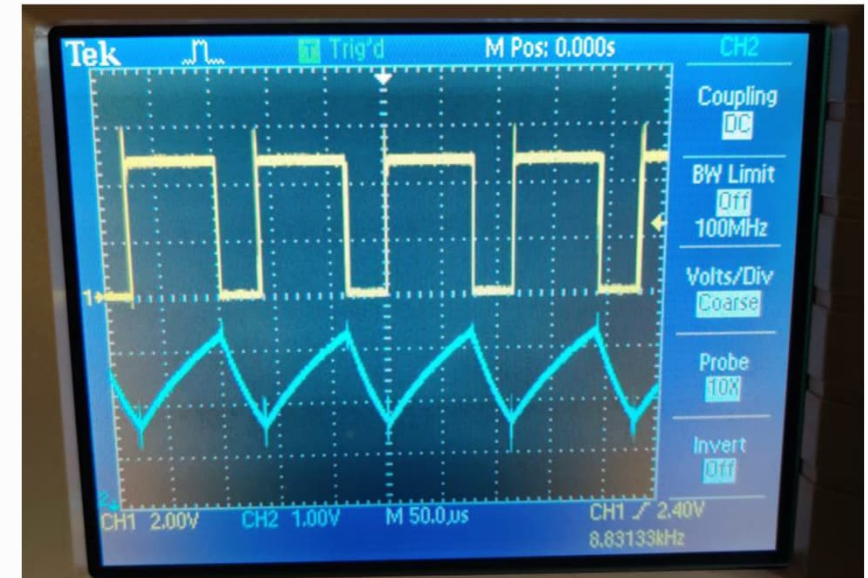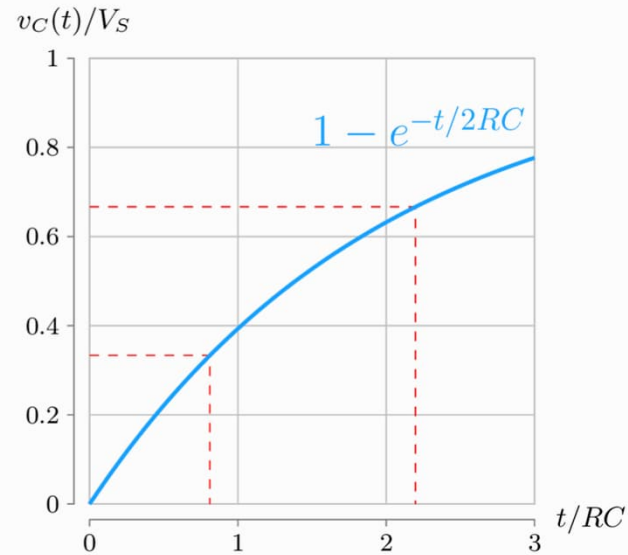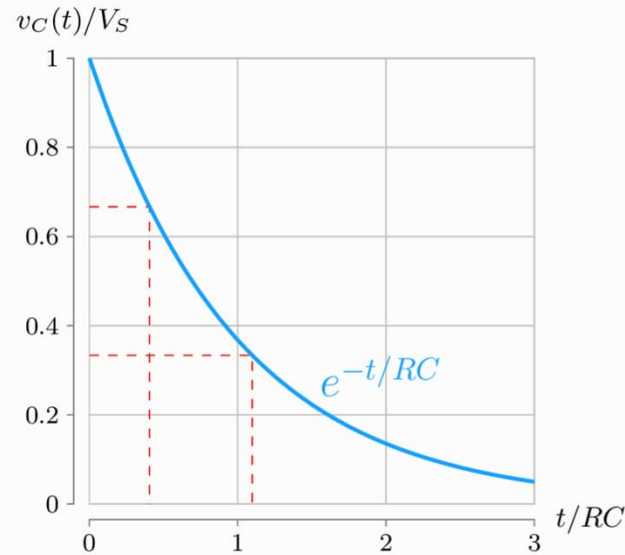

Limitations of Circuit Theory

- **Lumped elements**

- Dimensions of the circuit must be at least ten times lower than the minimum wavelength.

$$\lambda_{min} \approx \frac{c}{f_{max}}$$

c : light speed = 300,000 km/s

Example:

$$f_{max} = 3 \text{ GHz} \Rightarrow \lambda_{min} = 10 \text{ cm} \Rightarrow d_{circuit} < 1 \text{ cm}$$

- **Nonlinearity**
- **Parasitic elements**

